

## THE COMPLEMENTARY FEEDBACK PAIR.

This page last updated: 19 Apr 2000



[to Discrete Design](#)

The simple emitter-follower is lacking both in linearity and load-driving ability. The first shortcoming can be addressed by adding a second transistor to increase the negative feedback factor by increasing the open-loop-gain. This also allows the stage to be configured to give voltage-gain, as the output and feedback point are no longer inherently the same.

This arrangement is usually called the Complementary Feedback Pair (hereafter CFP) though sometimes known as the Szilaki configuration.

### CFP EMITTER-FOLLOWERS.

This circuit can be modified for constant-current or push-pull operation exactly as for the simple emitter-follower. Just plug and play.


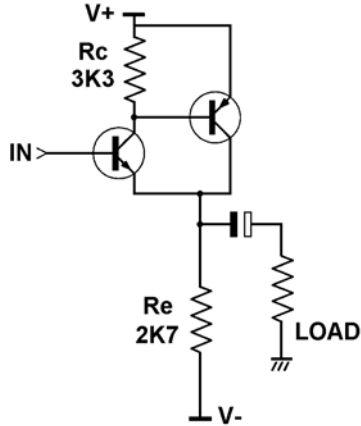


Fig 9: The CFP emitter-follower.

The single transistor is replaced by a pair with 100% voltage feedback to the emitter of the first transistor. The emitter resistor  $R_e$  has been kept at the same value as in the simple emitter-follower to allow meaningful comparisons. The value of  $R_c$  is crucial to good linearity, as it sets the  $I_c$  of the first transistor, and also determines its collector loading. The value of 3K3 shown here is a good compromise.

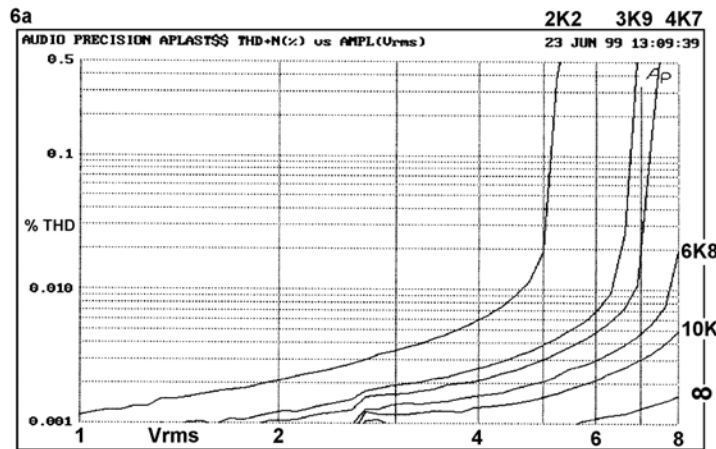

CFP emitter-follower

Fig 10: Distortion and loading effects on the CFP emitter-follower. THD at 6Vrms, 6K8 load is only 0.003% compared with 0.07% for the simple EF.  $R_e$  is 2K7 as before. (6A)

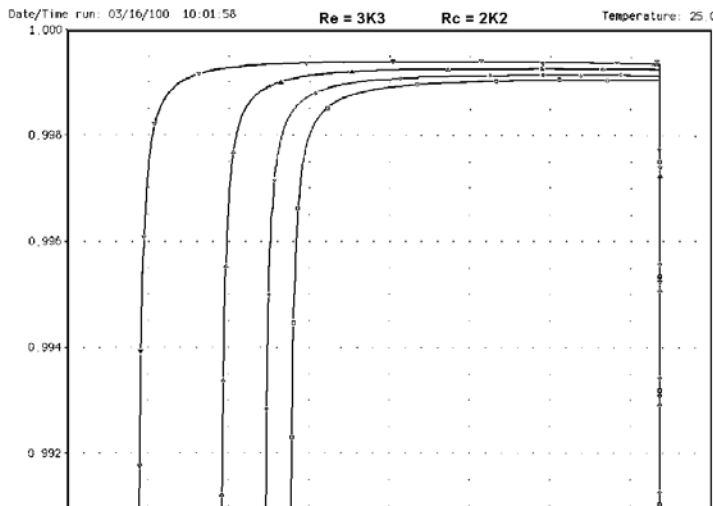


Fig 10a: SPICE simulation of the circuit in Fig 9, for different load resistances.


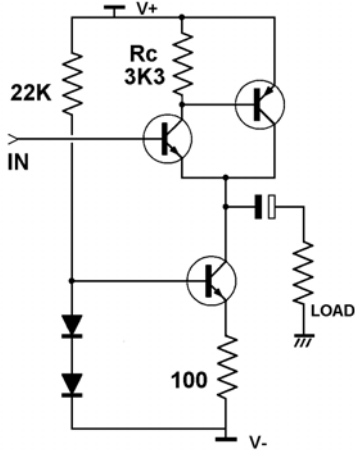


Fig 11: Constant-current CFP follower. Once more the resistive emitter load is replaced by a constant-current source to improve current-sinking.

The 6Vrms,6K8 THD is now too low to measure; it is below 0.0008%. (yes, three zeros after the point- this simple circuitry can be rather effective) See the plot below.

The quiescent current remains at 6mA.

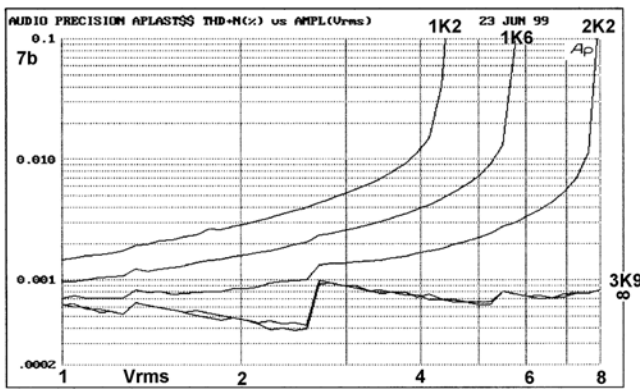

CFP  $R_e = 100 \Omega$

Fig 12: Distortion and loading effects on the CFP emitter-follower with 6 mA current-source. The steps on the lower traces are artefacts caused by the measurement system gain-ranging as it attempts to measure the THD of pure noise. (7B)


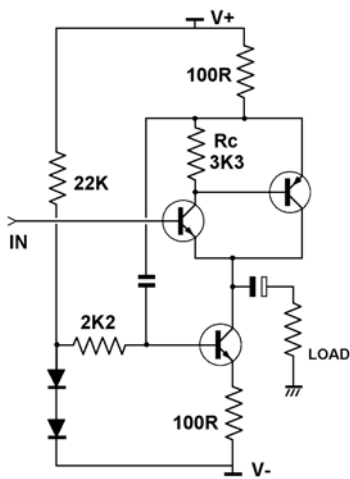


Fig 13: Circuit of a push-pull CFP follower.

This version once more gives twice the load-driving capability for no increase in standing current.

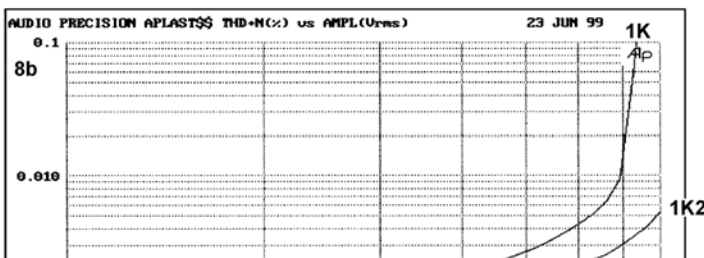

**Fig 14: Distortion and loading effects on the pushpull CFP emitter-follower. The load must be as heavy as 1K6 before measurable distortion is generated. 6 mA quiescent current as usual. Steps on lower traces are artefacts of the measurement system. (8B)**

---