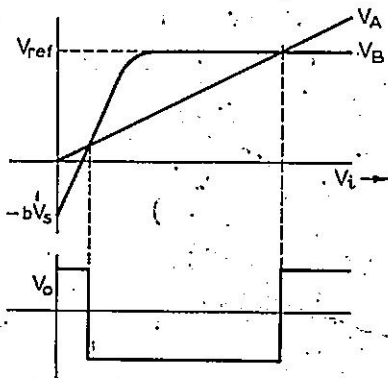


Simple window discriminator

The voltages at the input terminals of the comparator are as shown. V_A is an attenuated form of the input V_i , but V_B is offset by an amount $-bV_S$ ($V_S =$ supply voltage), and rises linearly with



V_i until D_1 becomes reverse biased, when it is clamped to V_{ref} . Thus the V_A and V_B curves cross twice, giving rise to the two switching points. V_B , below the knee, is given by $V_B = V_{in}(1-b) - bV_S$, and above by $V_B = V_{ref}$. Because $V_A = aV_{in}$, the lower switching point occurs at;

$$aV_{in} = (1-b)V_{in} - bV_S$$


i.e. $V_{in} = -bV_S / (a + b - 1)$,
and the upper switching point at;

$$aV_{in} = V_{ref}$$

i.e. $V_{in} = V_{ref}/a$.

By fixing the ratio, the two switching points may be varied independently by adjusting b and V_{ref} for the lower and upper points respectively. As shown, the circuit will work only with positive going input voltages, but by reversing the polarity of D_1 , V_{ref} and $-V_S$, may be made to work with negative going inputs.

M. J. Newman,
Stockton,
Teesside.

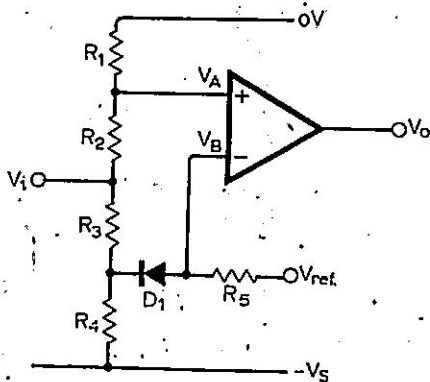

$$\frac{R_1}{R_1 + R_2} = a; \quad \frac{R_3}{R_3 + R_4} = b; \quad R_5 \gg R_3 \parallel R_4$$