



DESIGN NOTES

µModule LED Driver Integrates All Circuitry, Including the Inductor, in a Surface Mount Package – Design Note 445

David Ng

Introduction

Once relegated to the hinterlands of low cost indicator lights, the LED is again in the spotlight of the lighting world. LED lighting is now ubiquitous, from car headlights to USB-powered lava lamps. Car headlights exemplify applications that capitalize on the LED's clear advantages—unwavering high quality light output, tough-as-steel robustness, inherent high efficiency—while a USB lava lamp exemplifies applications where *only* LEDs work. Despite these clear advantages, their requirement for regulated voltage *and* current make LED driver circuits more complex than the venerable light bulb, but some new devices are closing the gap. For instance, the LTM[®]8040 µModule[™] LED driver integrates all the driver circuitry into a single package, allowing designers to refocus their time and effort on the details of lighting design critical to a product's success.

A Superior LED Driver

The LTM8040 is a complete step-down DC/DC switching converter system that can drive up to 1A through a string of LEDs. Its 4V to 36V input voltage range makes it suitable for a wide range of power sources, including 2-cell lithium-ion battery packs, rectified 12VAC and industrial 24V. The LTM8040 features both analog and PWM dimming, allowing a 400:1 dimming range. The built-in 14V output voltage clamp prevents damage in

the case of an accidental open LED string. The default switching frequency of the LTM8040 is 500kHz, but switching frequencies to 2MHz can be set with a resistor from the RT pin to GND.

Easy to Use

The high level of integration in the LTM8040 minimizes external components and simplifies board layout. As shown in Figure 1, all that is necessary to drive an LED string up to 1A is the LTM8040 and an input decoupling capacitor. Even with all this built-in functionality, the LTM8040 itself is small, measuring only 15mm × 9mm × 2.82mm.

Rich Feature Set

The LTM8040 features an ADJ pin for precise LED current amplitude control. The ADJ pin accepts a full-scale input voltage range of 0V to 1.25V, linearly adjusting the output LED current from 0A to 1A. Figure 2 shows the ratiometric response of the output LED current versus the ADJ voltage. The ADJ pin is internally pulled up through a 5.11k precision resistor to an internal 1.25V reference, so the output LED current can also be adjusted by applying a single resistor from ADJ to ground, as shown in Figure 3.

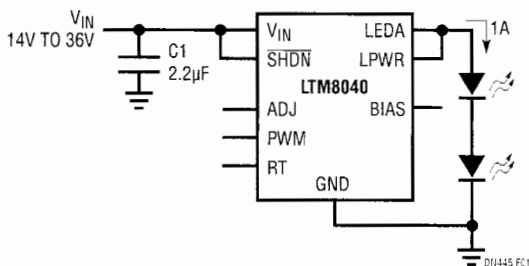


Figure 1. Driving an LED String with the LTM8040 Is Simple—Just Add the Input Capacitor and Connect the LED String

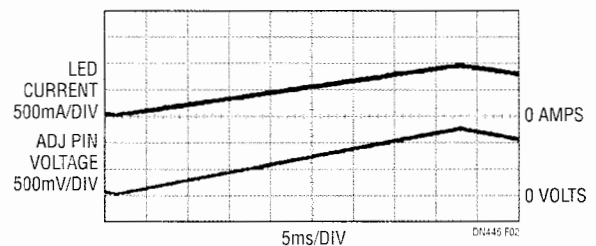


Figure 2. Drive a 0V to 1.25V Voltage into the ADJ Pin to Control the LED Current Amplitude

LT, LT, LTC and LTM are registered trademarks of Linear Technology Corporation. µModule is a trademark of Linear Technology Corporation. All other trademarks are the property of their respective owners.

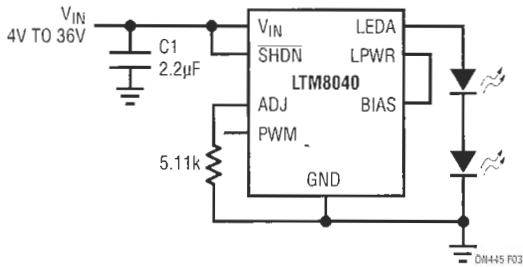


Figure 3. Control the LED Current with a Single Resistor from ADJ to Ground

The PWM control pin allows high dimming ratios. With an external MOSFET in series with the LED string as shown in Figure 4, the LTM8040 can achieve dimming ratios in excess of 400:1. As seen in Figure 5, there is little distortion of the PWM LED current, even at frequencies as low as 10Hz. The 10Hz performance is shown to illustrate the capabilities of the LTM8040—this frequency is too low for practical pulse width modulation, being well within the discrimination range of the human eye.

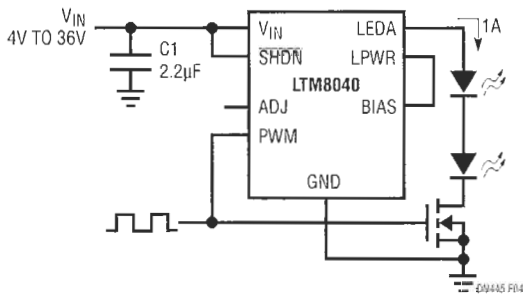


Figure 4. The LTM8040 Can PWM its LED String with an External MOSFET

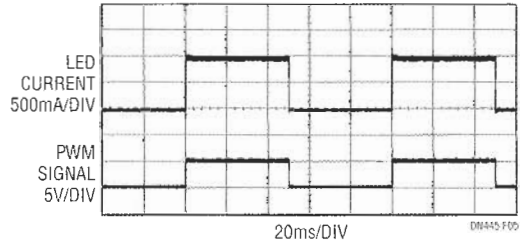


Figure 5. The LTM8040 Can PWM LED Current with Minimal Distortion, Even at Frequencies as Low as 10Hz

The LTM8040 also features a low power shutdown state. When the SHDN pin is active low, the input quiescent current is less than 1µA.

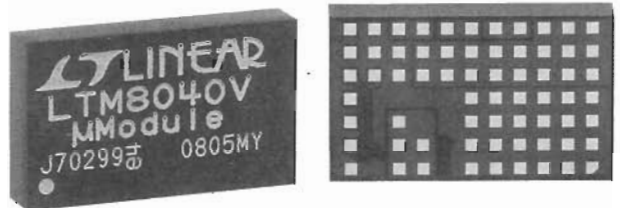


Figure 6. Only 9mm × 15mm × 2.82mm, the LTM8040 LED Driver is a Complete System in an LGA Package

Conclusion

The LTM8040 µModule LED driver makes it easy to drive LEDs. Its high level of integration and rich feature set, including open LED protection, analog and PWM dimming, save significant design time and board space.

Data Sheet Download

www.linear.com, see also www.linear.com/micromodule

For applications help,
call (408) 432-1900, Ext. 2593