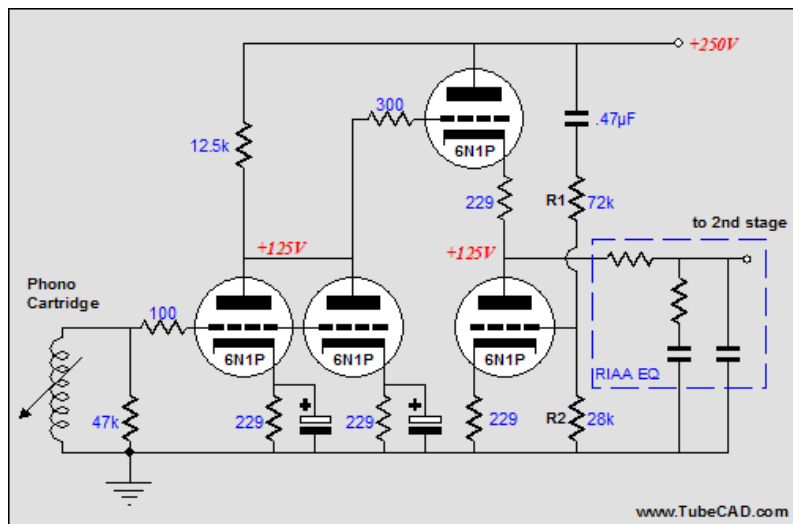




In the schematic above, we see three triodes working in an Aikido amplifier. The input stage still halves the power supply noise at its output and the cathode follower stage still has half of the power supply noise injected to the bottom triode's grid. So, why bother with two triodes for the input stage? The advantage that two triodes hold is that we are not restricted to one triode type.

Usually each triode requires its own specific cathode resistor value to bias up to the desired idle current and to match a fixed plate resistor value, whereas in the balanced totem-pole configuration, we sidestep this need, as any fairly well matched set of triodes will always halve the power supply noise, with the idle current falling where it will and while still retaining the B+ voltage halving. In the test setup I had built for the Aikido amplifier, I was able to plug in 12AT7s, 12AU7, 12AV7s, 12AX7s, 12BH7s, and 5751s. In each case, the circuit worked beautifully, the gain being the only changing variable. Had a single triode been used in the input stage, then each different tube type would require a different cathode resistor value (in some cases, the plate resistor would have to be changed as well).

So, what we gain by using two triodes in the input stage is ease of use and universality. Laudable goals indeed, but there are times when another goal may trump (for example, more gain). In the balanced totem-pole configuration the gain is equal to the amplification factor ( $\mu$ ) divided by 2; whereas when the cathode resistor is bypassed, a grounded-cathode amplifier can deliver a gain much closer to the triode's  $\mu$ . Bypassing the cathode resistor will alter the power supply noise division, so the percentage of power supply noise injected into the cathode follower's bottom triode will correspondingly be altered.




In the schematic above, we see basis of the first half of a tube phone preamplifier. The circuit begins with two 6N1Ps working in parallel into a common plate resistor. Each triode gets its own bypassed cathode resistor, which allows each triode to find its own quiescent idle current. Effectively, the two triodes act as one triode with the same  $\mu$  and twice the transconductance ( $g_m$ ) and half the plate resistance ( $r_p$ ). At the specified plate voltage and idle current, these values become:  $\mu = 36$ ,  $g_m = 7.5 \text{ mA/V}$ , and  $r_p = 4.8k$ . Thus, the 12.5k plate resistor is effectively in series with a 4.8k resistance, with a resulting voltage division of 28%. Therefore, the cathode follower's bottom triode's grid must be presented with 28% of the power supply noise, which 72k and 28k resistors yield easily enough.
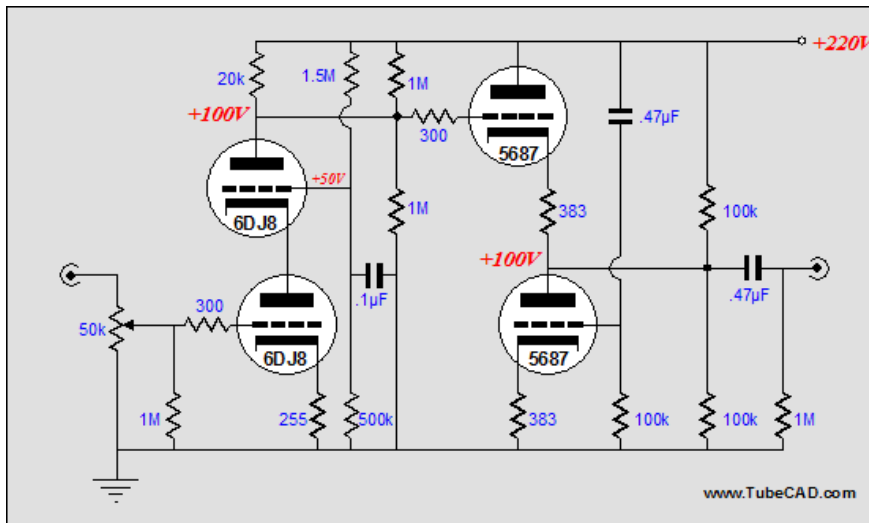
### The cathode follower half of the Aikido amplifier



Having looked into the first half of the Aikido amplifier, let's now move on to the second half: the cathode follower portion. What if attaining the lowest







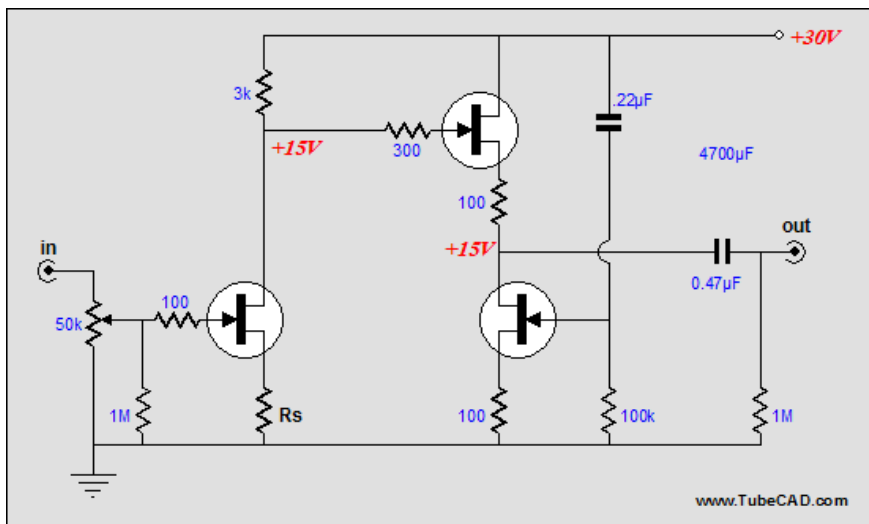
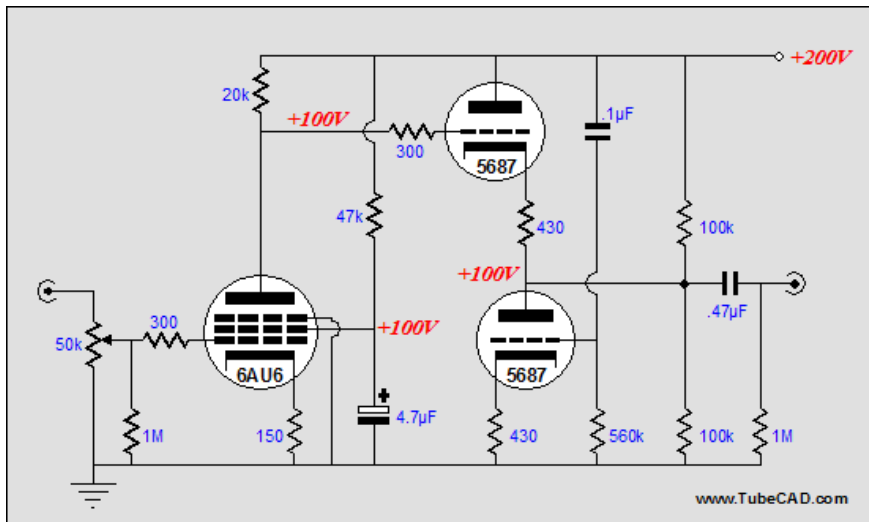
In the circuit below, a pentode has replaced the cascode. Once again, we inject all of the noise into the bottom triode's grid to counter the noise at its plate.




In the schematic above, we see an all-FET preamp. The gain will roughly equal the drain resistor divided by the source resistor,  $R_s$ . No matter what the final gain, however, all of the power supply noise will transfer to the top source-follower FET's gate, so we must offer the bottom FET the same amount of noise. This is easily done by attaching its bypass capacitor to the B+ rail. (This is exactly opposite of what 99% of electronic designers would do, as they always





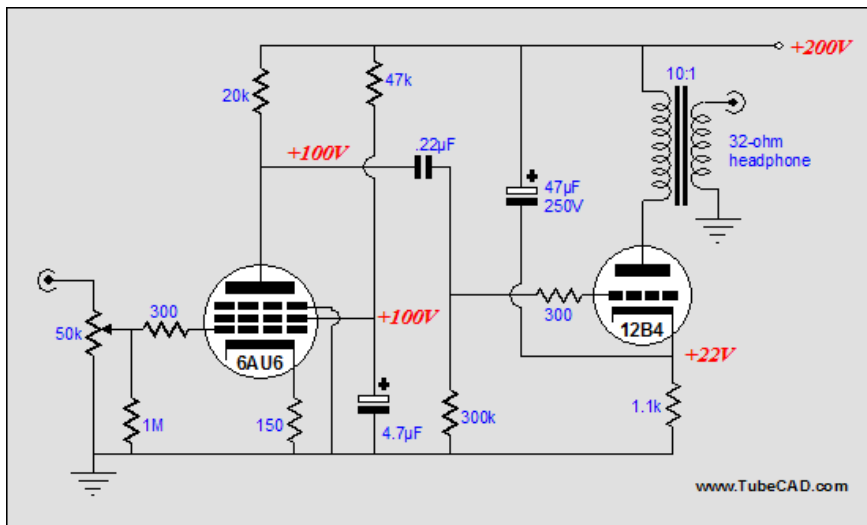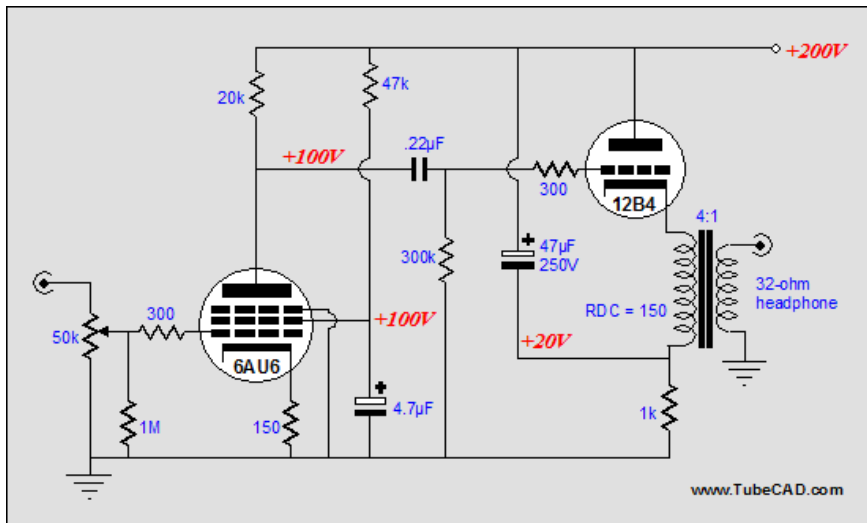

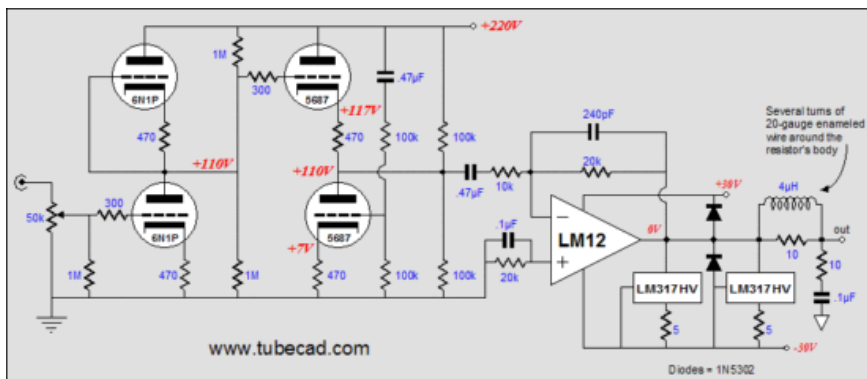In this variation, we see the output stage configured as a grounded-cathode amplifier. This time the 47μF capacitor couples the power supply noise to the output tube's cathode. The result is that the output tube does not "see" the power supply noise about it, as it plate and grid also equally see the same noise.



Click on image to see closeup

Just in case my solid-state e-mail falls off, here is a simple hybrid that uses an LM12 power OpAmp, but with a few twists. Of course, the tube front end counts, but the two LM317s add a nice twist: they are configured as constant-current sources that force the LM12's output stage to work in single-ended Class-A mode for the first watt, with push-pull Class-AB thereafter.



//JRB

<a href="#">&lt; Back</a>	<a href="http://www.tubecad.com">www.tubecad.com</a>	Copyright © 1999-2004 GlassWare	All Rights Reserved	<a href="#">Next &gt;</a>
---------------------------	--	---------------------------------	---------------------	---------------------------