



# A Strobe Flasher for Night Cycling

*Uses a high-voltage xenon flash tube and dc/dc converter.*

**A**LL BICYCLISTS and car drivers are aware of the need for visibility when riding a two-wheeler at night or in fog. However, providing a clear indication of a cyclist's presence can be a real problem. Blinking incandescent lights can be used, but they put out only small amounts of light. The light described in this article uses a xenon tube to generate a bright flash that can be seen from a great distance—but is not intense enough to destroy a driver's night vision. Simple circuitry allows the project to be built at low cost, in a lightweight, compact package that can be secured to the bicycle or the rider's belt.

**Principles of Operation.** The light-producing element is a sealed glass tube containing two electrodes and filled with the inert gas, xenon. When a high voltage is applied to the tube, the gas ionizes. That is, some of the electrons are stripped from the xenon atoms. When the electrons and xenon ions recombine, the energy that caused them to separate is given up as light. If many atoms are ionized, the light output is intense.

Xenon flash lamps are usually operated in a pulsed mode. The intensity of their flashes gives good visibility, and their short duration keeps the average power applied to the tube low. How-

ever, the flash tubes require high voltages. In this circuit, a dc-to-dc converter supplies this high voltage, drawing power from two AA batteries. A capacitor stores charge which is needed for the large instantaneous flash current. To initiate ionization in the tube, a potential difference of about 4000 volts is required. This is developed by a trigger coil, or pulse transformer, which steps up the converter output.

**About the Circuit.** Transistor *Q1*, transformer *T1*, and their associated components comprise an oscillator which is the heart of the dc-to-dc con-

verter. When power is first applied, collector current builds up until the ferrite core of *T1* saturates. At this point, base drive is removed from *Q1*, the transistor cuts off, and flux in the core decays. Then the cycle repeats itself again.


On the other side of *T1*, high voltage pulses developed across the secondary are rectified by *D1*, and charge *C2* to +250 volts. The voltage divider composed of *R2*, *R3*, and *R4* charges *C3* to 90 volts and *C4* to 200 volts. The time constants associated with these capacitors are small, so the voltages across *C3* and *C4* can be assumed to be proportional to that across *C2*.

When the potential across *C3* reaches approximately 90 volts, neon lamp *I1* fires and discharges *C3* through the gate of *SCR1*. This causes *SCR1* to turn on, and the charge stored in *C4* is dumped into the primary of *T2*, the trigger coil. Because of *T2*'s high step-up ratio, this surge of current induces a potential difference of several thousand volts across the secondary. In turn, the flashtube fires, creating a bright flash of light as the charge stored in *C2* flows through the tube. When *C2*'s charge is depleted, the tube stops conducting and goes dark. Then the rectified pulses from *D1* start to charge up the capacitors, and the cycle begins again.

The flasher requires only two or three volts to function. Two penlight (AA) cells make a lightweight power source, but since current drain is 250 to 300 mA, carbon zinc cells should be used only if the flasher is intended as a back-up safety device in extreme circumstances. However, two alkaline AA cells should provide about six hours of intermittent operation. If the flasher is to be used frequently, rechargeable nickel-cadmium batteries should be installed. They will give about two hours' use to a charge. (Of course, rechargeable or nonrechargeable C or D cells can be used if more extensive use is contemplated.)

Most of the components can be obtained from any electronic parts store, including flash tube *FT1* and trigger coil *T2*. However, the converter transformer *T1* must be wound on a Ferroxcube 2616-F1D bobbin and uses two Ferroxcube 2616-PLOO-3C8 pot core halves. These parts are available from some industrial distributors, and a mail-order source is included in the parts list.

**Construction.** The flasher can be

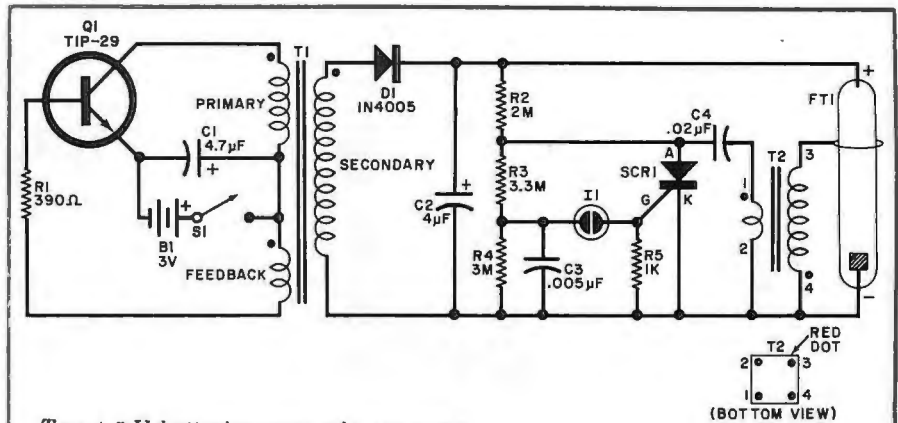

Two 1.5-V batteries power the converter which drives the flashtube and SCR trigger circuit.

### PARTS LIST

B1—Two 1.5-volt cells in series (see text)  
 C1—4.7- $\mu$ F, 10-V electrolytic capacitor  
 C2—4- $\mu$ F, 450-V electrolytic capacitor  
 C3—0.005- $\mu$ F, 500-V disc ceramic capacitor  
 C4—0.02- $\mu$ F, 500-V disc ceramic capacitor  
 D1—1N4005 diode  
 FT1—Xenon flash tube (Radio Shack 272-1145 or equivalent)  
 I1—NE-2 neon bulb  
 Q1—TIP-29, HEP S5000 npn plastic power transistor or equivalent  
 The following are 1/4-watt, 10% tolerance resistors:  
 R1—390 ohms  
 R2—2 megohms  
 R3—3.3 megohms

R4—3 megohms  
 R5—1000 ohms  
 S1—SPST switch  
 SCR1—400-volt silicon controlled rectifier (Radio Shack 276-1000 or equivalent)  
 T1—see text  
 T2—4000-volt trigger coil (Radio Shack 272-1146 or equivalent)  
 Misc.—Printed circuit or perforated board, solder, hookup wire, No. 34 enamelled wire, No. 28 enamelled wire, machine hardware, circuit board spacers, suitable enclosure, battery holder, standoff insulator, silicone cement, solder, etc.  
 Note—The Ferroxcube 2616-F1D bobbin and two 2616-PLOO-3C8 ferrite pot core halves are available for \$3.00 (first class postage paid) from Elna Ferrite Laboratories, Inc., Box 395, Woodstock, NY 12498.

built on a printed circuit or perforated board, and housed in any enclosure of sufficient size. The prototype was built in a small plastic box with a transparent top which protects the flash tube without obscuring its light output.

No matter which arrangement is chosen, the first step in constructing the flasher is to assemble *T1*. It is wound on a nylon bobbin that will be inserted into a two-piece ferrite pot core. Begin with the secondary. Allow a few inches of No. 34 enamelled wire to extend from a slot in the bobbin, and attach a "flag" of masking tape to the end of the wire. Mark the tape with an "S." This will allow you to keep track of the start of the secondary winding, which is essential to proper phasing. Secure the wire to the bobbin with a piece of electrical tape, and then wind 350 turns, keeping each layer even. When you have finished, cover the winding with electrical tape, and leave a few inches of wire free to serve as a connecting lead for the "finish" end of the secondary.

The primary will be wound next, using No. 28 enamelled wire. Use a masking tape flag marked "P" to identify the start of the winding, and wind 16 turns in the same direction as you

did for the secondary. When the primary is completely wound, cover it with a layer of electrical tape. As before, leave a few inches of wire free at both ends of the primary. Finally, wind the five-turn feedback winding in the same direction as the other two. Use No. 28 enamelled wire, identify the start of the winding with a tape flag marked "F," and cover the completed bobbin with a layer of electrical tape. Again, leave a few inches of lead length on each side of the winding.

Insert the bobbin between the two pot core halves, and mount the transformer on the project board using #6-32 machine hardware. The ferrite core is very brittle, so the mounting hardware should be no more than finger tight. Use a dab of silicone cement to secure the nut to the board.

The flashtube should be mounted so that it can be seen and is somewhat protected from shock. The author mounted his flashtube on the circuit board using its leads and a standoff insulator. Note that the electrode composed of wire mesh is the cathode. Trigger transformer *T2* should be positioned near the flashtube. The rest of the components can be mounted in any convenient

manner. It is wise to leave the transformer leads long, as a mistake in the direction of a winding, or improperly identifying the start of a winding, will require a phasing change involving the reversal of one or more windings.

### **Checkout and Troubleshooting.**

When you have completed building the project, double check all wiring, and then turn the unit on. The flashtube should flash about once each second, and an audible whistle should be heard near *T1* as the dc-to-dc converter oscillates.

If no whistle is heard, measure the battery voltage and current with a high-impedance multimeter. If no current is being drawn from the battery, check the wiring to *T1*, *Q1*, *R1*, the battery, and switch *S1*. If current is being drawn, try reversing either the primary or feedback winding of *T1*, but *not both!*

The converter might oscillate but the flashtube won't flash. In that case, measure the voltage across *C2*. Although current is limited, the capacitor's voltage can give you an unpleasant shock, so be careful! A reading of 250 to 300 volts is normal. But if the voltage is below this level, disconnect *R2* and the anode of *FT1* from the positive plate of *C2*. If the voltage is now correct, the problem is located in the trigger circuit for the flashtube. If the voltage is low but not zero, try reversing the secondary winding of *T1*. Zero voltage points to incorrect wiring or a defective *D1* or *C2* component.

When the voltage across *C2* is correct but there is no flash, the trigger circuit must be examined. Measure the voltage between the anode and cathode of *SCR1*. You should obtain a reading of 200 volts or so. If you do, short these two points with a jumper. The tube should flash as you do this. If it doesn't, either it or the trigger coil is defective. Other possibilities are a faulty SCR or trigger component (*I1*, etc.) or incorrect wiring of that part of the circuit that generates the trigger.

**Final Thoughts.** If desired, small leather straps can be secured to the flasher enclosure to serve as belt loops. The unit is small enough to be mounted either on the bicycle or on the cyclist's arm or leg. It can also be taken along for hikes on dark country roads. You will probably find many other applications for this handy little bicycle flasher. 