



BUILD AN

Electrolytic Restorer

PREVENT HIGH-VOLTAGE CAPACITOR BREAKDOWN

BY GEORGE J. FLAMONDON

WHEN a high-voltage electrolytic capacitor has been unused for too long a time, it is customarily looked upon as a possible troublemaker. Too often, when power is applied to such units, the dielectric punctures, destroying the capacitor and probably the associated circuit. Unfortunately, many people have some of these capacitors in their junk boxes (they were quite common in power supplies for vacuum-tube circuits), but hesitate to use them. Since they are fairly expensive, it behooves the electronics experimenter or service man to salvage such

capacitors by restoring the dielectric so that there is no chance of its breaking down when put to use.

However, before finding out how to restore an electrolytic, let's be sure we know the exact nature of the trouble.


What Is an Electrolytic Capacitor? An electrolytic capacitor usually consists of two flexible sheets of aluminum foil separated by gauze impregnated with an electrolyte. Leads are connected to each foil section. The foil connected to the positive lead has an


oxide coating which serves as the capacitor's dielectric. It is the thickness of this coating that determines the working voltage of the capacitor.

While the capacitor is being used, the oxide coating is preserved by chemical processes resulting from the voltage impressed across the terminals. Unfortunately, when it


is in storage, time and ambient heat take their toll and the oxide deteriorates. When the full working voltage is applied to a capacitor whose oxide is weak, the latter breaks down and a short circuit is placed across the circuit.

Reforming the Dielectric. The dielectric

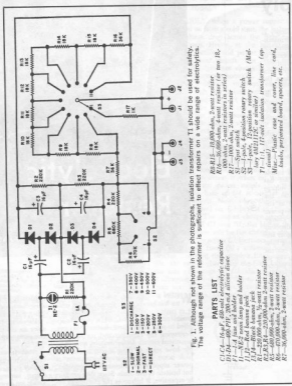

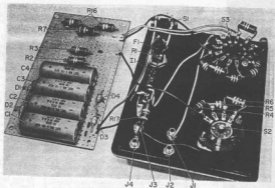

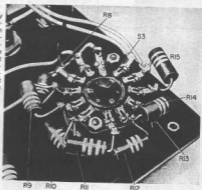Perf board construction may be used with operating controls and jacks mounted on front panel of selected cabinet. A TV-type cheater connector is used to make the power connection. Mount perf board on suitable spacers and be sure that components on board do not make electrical contact with any front-panel elements.



of a suspect capacitor can be reformed by connecting a low dc voltage across the capacitor and slowly increasing the voltage until the rated value is reached. This must be done over a long period of time to allow the oxide to reform properly.

The "Electrolytic Restorer" described here does this job automatically, and requires only

an occasional look at a dc voltmeter to check progress. The cost of the project is about \$14 if all parts are bought new.

Construction. The prototype shown in the photos was housed in a conventional plastic case although any type of arrangement will suffice. The schematic of the circuit is shown

THEORY OF CIRCUIT DESIGN

Diodes *D1* through *D4* and capacitors *C1* through *C4* form a full-wave voltage quadruplar rectifier with a dc output of approximately 600 volts. Resistors *R7* through *R16* form a voltage divider network and *S3* selects the desired voltage and applies it to the parallel-connected positive output jacks *J1* and *J2*. The negative side of the power supply is connected through a switch-selected resistor network consisting of *R4* through *R6* to the parallel-connected negative jacks *J3* and *J4*. The use of *S2* determines the forming rate. The **RESET** position permits the unit to be used as a high-voltage, low-current power supply. This position can be eliminated if desired.

The **RESISTANCE** position of *S3* places *R17* across the output to discharge the formed capacitor, while resistors *R2* and *R3* keep a small load on the power supply and discharge the power supply capacitors.

During the forming process, the capacitor's resistance is low so most of the voltage is dropped across the limiting resistor. As the oxide coating in the capacitor is re-formed, less current flows through the capacitor, causing the voltage across it to increase. When this voltage equals the preset voltage on *S3*, the reformation is complete.

in Fig. 1. Exact placement of parts is not given since dimensions are not critical and the control locations can be changed depending on personal preferences.


Most of the circuit can be assembled on

perforated board. The front panel controls and jacks are mounted directly on the case cover, making sure that all leads are long enough to reach the electronics board. For safety, a 1:1 ac line isolation transformer should be used, though this is not shown in the prototype.


Operation. The electrolytic capacitor to be reformed is connected to the output jacks, making sure that the polarities are observed. The positive side of the capacitor is connected to either *J1* or *J2* and the negative side to either *J3* or *J4*. The dc voltmeter for checking the reforming action is connected to the remaining two jacks. Make sure that the polarity and voltage range are correct. The voltmeter can be disconnected and reconnected at any time without affecting the operation.

Place *S3* in the **RESISTANCE** position, plug the unit in, and turn on the power. Neon indicator lamp *I1* should glow. Set the desired forming rate on *S2* and then rotate *S3* to the working voltage of the capacitor. If the capacitor is unformed, the voltmeter will indicate a much lower voltage than that set on *S3*.

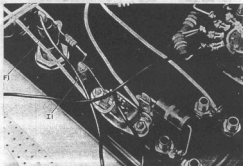Note that the voltmeter indication starts to increase quickly at first, then slows down as the dielectric forms. The rate of increase is determined by the condition of the capacitor and the setting of *S2*. When the slow setting



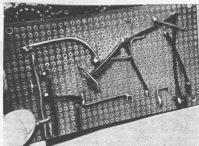Be careful when drilling holes in the plastic front panel as it will chip easily. Neon indicator lamp is cemented in the hole, other components use hardware.



Insulated wiring is used to make interconnections. If metal case is used, make sure spacers keep connections from touching case.

is used, the operation takes longer but the oxide formed will be of better quality. The opposite is true for the **FAST** setting. Use the **NORMAL** position for most cases.

When the voltage across the capacitor is approximately equal to the set on **S3**, put the switch on **DISCHARGE** and remove the capacitor. No harm will be done if the capacitor is left connected longer than required, so it is not necessary to check progress constantly.

To use the unit as a high-voltage, low-cur-

rent power supply, set the forming rate switch (**S2**) to **RECTIFY**. A current of 4 mA may be drawn continuously, and somewhat higher currents for a short period of time. (A load current of 10 mA causes a dissipation of 3 watts in the divider resistors.)

The Electrolytic Restorer can also be used for a quick go-no-go check of voltmeters. Comparison of voltage switch settings and voltmeter readings will reveal any gross inaccuracies. ♦



The finished front panel should be labeled as shown here. A coating of transparent plastic spray keeps lettering from getting smeared.