

PC-BASED SCROLLING MESSAGE DISPLAY

■ SURESH KUMAR

Controlling electronic devices from a PC is fun. Here is a scrolling message display that makes use of the PC's parallel port. The message typed from the keyboard of the PC is displayed on the light-emitting diodes arranged as 5×7 dot-matrix display in moving message format.

LED-based scrolling message displays are increasingly being used at railway stations, public places, colleges, universities, hospitals, general stores, etc for disseminating information. However, most displays lack in storage capacity and cannot display a large number of characters at a time.

This PC-based LED scrolling message display has the following features:

1. The message to be displayed is stored in a file and the message length to be displayed is limited only by free memory space on the hard disk of the computer.
2. The number of characters displayed at a time can be as high as 30.
3. The message stored in the file can be changed using any text editor including Notepad.
4. The running speed of the message displayed can be increased or decreased by pressing a few keys.

Here, the circuit is designed for displaying English characters on a 35 (5×7) LED dot-matrix display.

The PC's parallel port (LPT port) is used to output the display code and the clock signal for the scrolling message display.

The parallel port is terminated into a 25-pin D-type female connector at the back of the PC. IBM PCs usually come with one or two LPT ports. Each parallel port is actually made up of

PARTS LIST

Semiconductors:

IC1	- 7805C 5V regulator
IC2-IC8	- 74174 hex D-type flip-flop
D1-D4	- 1N4007 rectifier diode
LED1-LED42	- Red LED

Resistors (all 1/4-watt, ±5% carbon):

R1- R42	- 150-ohm
---------	-----------

Capacitors:

C1	- 470µF, 16V electrolytic
----	---------------------------

Miscellaneous:

X1	- 230V AC primary to 7.5V, 1A secondary transformer
----	---

three ports, namely, data port, status port and control port. Here, only data port is used for this scrolling message display.

Pins 2 through 9 form the 8-bit data output port. This is purely a write-only port, which means it can only output data. The base address of the first parallel port (LPT1) is '378H' or '888' (decimal).

Parallel-input parallel-output (PIPO) registers are used to shift the signal from right to left. The clock pulse and code signal are generated by the computer program and output from the parallel port (base address 0×378). Theoretically, we can add infinite number of PIPO registers but the maximum number of registers is actually limited to the current triggering value of the clock pulse. To add a large number of PIPO registers, amplify the clock pulse prior to connecting it to the PIPO ICs.

Circuit description

Fig. 1 shows the circuit for the scrolling message display. IC 74174 has been used as PIPO register, which comprises high-speed, hex D-type flip-flops. It is used as a 6-bit edge-triggered storage register. The data on the inputs of the flip-flop is transferred for storage during high-to-low transition of clock. Data lines D0 through D5 of the paral-

lel port are connected to the input pins of the first flip-flop (IC2). The output of IC2 is fed to the next flip-flop IC input as well as LED. Data line D6 is fed to IC8, while data line D7 is connected to the clock inputs of IC2 through IC8. Clock pins of all the flip-flop ICs are connected together. Master reset pin 1 of all the flip-flops is connected to Vcc. Pins 18 through 25 of the parallel port are grounded. As data present on lines D0 through D6 shifts from the first stage to the next stage, and so on, the message appears as scrolling on the dot-matrix LED display.

The present circuit supports a display made of 42 LEDs comprising seven rows and six columns. Up to 30 such units can be added with no change in the circuit. However, to add these units, you need to amplify the clock pulse output. Note that each character is displayed in a matrix of 5 columns and 7 rows (explained later), hence the sixth-column LEDs form part of the next character (column 1).

Fig. 2 shows the power supply circuit. The AC mains is stepped down by transformer X1 to deliver a secondary output of 7.5V AC at 1A. The transformer output is rectified by a full-wave bridge rectifier comprising diodes D1 through D4, filtered by capacitor C1, then regulated by IC 7805C (IC1) to provide regulated 5V DC to the circuit.

An actual-size, single-side PCB for the circuits in Figs 1 and 2 is shown in Fig. 5 and its component layout in Fig. 6.

EFY note. Commercially 7×5 dot-matrix displays with discrete LEDs may not be easily available in the market, therefore a perforated board with holes for the LED leads may be used. The layout of such a board is shown in Fig. 7. The holes are used for passing the LED leads.

 


Fig. 2: Power supply

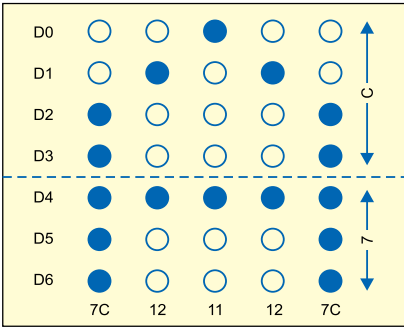


Fig. 3: Design of character 'A'

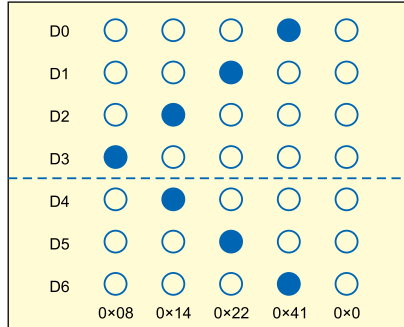


Fig. 4: Design of character '<'

'~', '@', '#', '\$', '%', '^', '(', ')', '{', '}', and ;'. It has been developed for displaying alphabets ('A' through 'Z'), digits ('0' through '9') and some special characters like ', ', '!', ' ', '-', '+', and '_'.

Other special characters can be added as follows: Suppose you want to display character 'A.' Draw 'A' on the 5x7 LED display as shown in Fig. 3. First, '7CH' data is available at the input of IC2 and the first flip-flop of IC8. When a clock pulse is received, this data (7CH) is output by IC2 and the first flip-flop of IC8 and new data '12H' arrives at the input pin of IC2 and the first flip-flop of IC8. The output data of IC2 and the first

 


Fig. 7: Perforated board for 5x7 LEDs

 


Fig. 5: Actual-size, single-side PCB for the LED-based scrolling message display including power supply

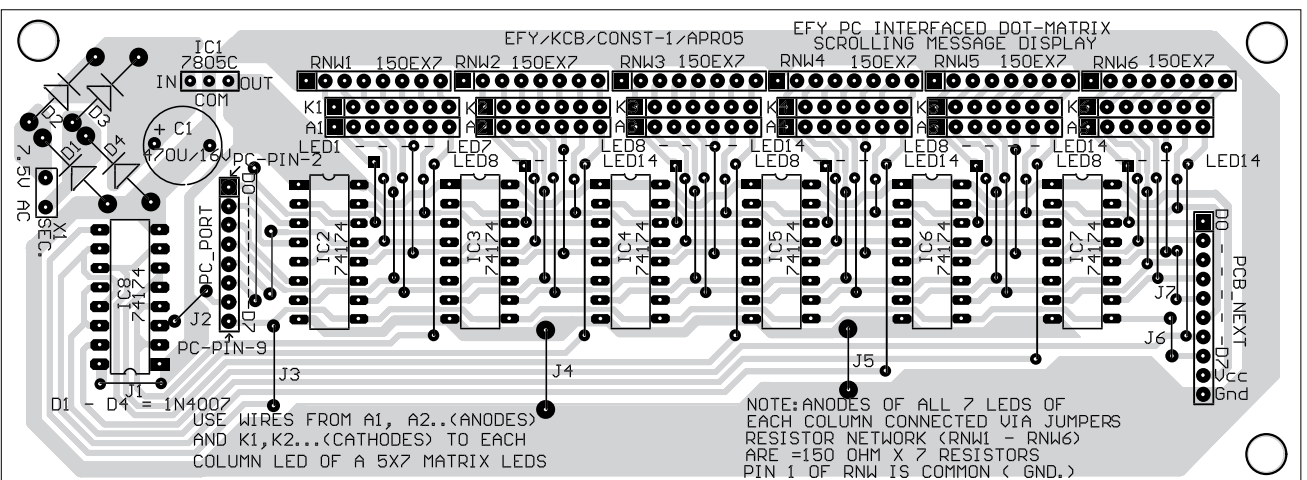


Fig. 6: Component layout for the PCB

<pre> r1[2]=0x40;str1[3]=0x40;str1[4]=0x3F; break; case 'v': case 'V': str1[0]=0x1F;str1[1]=0x20; str1[2]=0x40;str1[3]=0x20;str1[4]=0x1F; break; case 'w': case 'W': str1[0]=0x7F;str1[1]=0x20; str1[2]=0x10;str1[3]=0x20;str1[4]=0x7F; break; case 'x': case 'X': str1[0]=0x63;str1[1]=0x14; str1[2]=0x08;str1[3]=0x14;str1[4]=0x63; break; case 'y': case 'Y': str1[0]=0x03;str1[1]=0x04; str1[2]=0x78;str1[3]=0x04;str1[4]=0x03; break; case 'z': case 'Z': str1[0]=0x03;str1[1]=0x04; str1[2]=0x08;str1[3]=0x11;str1[4]=0x61; break; case '0': str1[0]=0x1C;str1[1]=0x22 ;str1[2]=0x41; str1[3]=0x22;str1[4]=0x1C; break; case '1': str1[0]=0x40;str1[1]=0x40; str1[2]=0x7F;str1[3]=0x42;str1[4]=0x44; break; case '2': str1[0]=0x46;str1[1]=0x49; str1[2]=0x51;str1[3]=0x61;str1[4]=0x42; break; case '3': </pre>	<pre> str1[0]=0x31;str1[1]=0x4B; st r1[2]=0x45;str1[3]=0x49;str1[4]=0x21; break; case '4': str1[0]=0x10;str1[1]=0x7F; st r1[2]=0x12;str1[3]=0x14;str1[4]=0x18; break; case '5': str1[0]=0x31;str1[1]=0x49; st r1[2]=0x49;str1[3]=0x49;str1[4]=0x27; break; case '6': str1[0]=0x32;str1[1]=0x49; st r1[2]=0x49;str1[3]=0x51;str1[4]=0x3A; break; case '7': str1[0]=0x07;str1[1]=0x79; st r1[2]=0x01;str1[3]=0x01;str1[4]=0x01; break; case '8': str1[0]=0x36;str1[1]=0x49; st r1[2]=0x49;str1[3]=0x49;str1[4]=0x36; break; case '9': str1[0]=0x3E;str1[1]=0x49; st r1[2]=0x49;str1[3]=0x49;str1[4]=0x26; break; case '.': str1[0]=0x60;str1[1]=0x60; st r1[2]=0x00;str1[3]=0x00;str1[4]=0x00; break; case ':': str1[0]=0x00;str1[1]=0x00; st r1[2]=0x00;str1[3]=0x00;str1[4]=0x00; break; case '!': str1[0]=0x67;str1[1]=0x7F; st r1[2]=0x00;str1[3]=0x00;str1[4]=0x00; break; case '-': </pre>	<pre> str1[0]=0x08;str1[1]=0x08; st r1[2]=0x08;str1[3]=0x08;str1[4]=0x08; break; case '+': str1[0]=0x08;str1[1]=0x08; st r1[2]=0x3E;str1[3]=0x08;str1[4]=0x08; break; case ' ': str1[0]=0x40;str1[1]=0x40;st r1[2]=0x40; str1[3]=0x40;str1[4]=0x40; break; //////// ADD YOUR CODES HERE//////// default: str1[0]=0x0;str1[1]=0x0;str1 [2]=0x0; str1[3]=0x0;str1[4]=0x0; break; } } void setcode() { int i,k; for(i=0,k=0;i<10;i+=2,k++) { str2[i]=str1[k]; str2[i+1]=str1[k]+128; } str2[i]=0; str2[i+1]=128; } void sendcode() { int i; for(i=0;i<12;i++) { outportb(0x0378,str2[i]); delay(DELAY); } } } </pre>
--	--	---