



THOMAS E. BLACK

YOU SLIP THE FLOPPY IN YOUR A: drive, copy the files to your hard disk—and discover that you forgot the latest update to the report you worked on last night at home. What do you do? Make the trip back home, possibly wasting hours in the process? Not if you have Ring-Thing. In that case, you just dial home, boot your PC, and download the file directly to your office. Ring-Thing is also useful for consultants and anyone who needs occasional remote access to a PC, but who doesn't want to leave his or her PC on all the time, risking intrusion by hackers.

Ring-Thing acts as an interface between your phone line and an AC power strip, as

shown in Fig. 1. When Ring-Thing recognizes a set number or pattern of ring signals, it turns on a relay that applies 117 VAC to whatever is plugged into the power strip. After the phone connection terminates, Ring-Thing waits 5–6 minutes and then removes power from the power strip. Ring-Thing can control IBM compatibles, Macintoshes, Amigas—even non-computer equipment. And a special software module allows special tricks with an IBM compatible PC.

An on-board 68HC705 microcontroller provides simple operation and sophisticated features, summarized in Table 1.

You can order a complete kit of parts for about \$80, and partial kits containing hard-to-

find parts, commercial-quality double-sided PC boards, and software. The RE-BBS (516-293-2283, 1200/2400, 8N1) also carries the software; look for file RINGTHING.EXE, a self-extracting archive that contains C++ source and object code for the optional IBM control module, and a Motorola format hex file containing the object code for the microcontroller. Firmware source code is not available.

Operating modes and controls

Ring-Thing has two jumper-selected modes of operation: Ring Counting and Ring Pattern.

Ring Counting (Standard Mode) After one or ten rings (jumper selectable), Ring-Thing

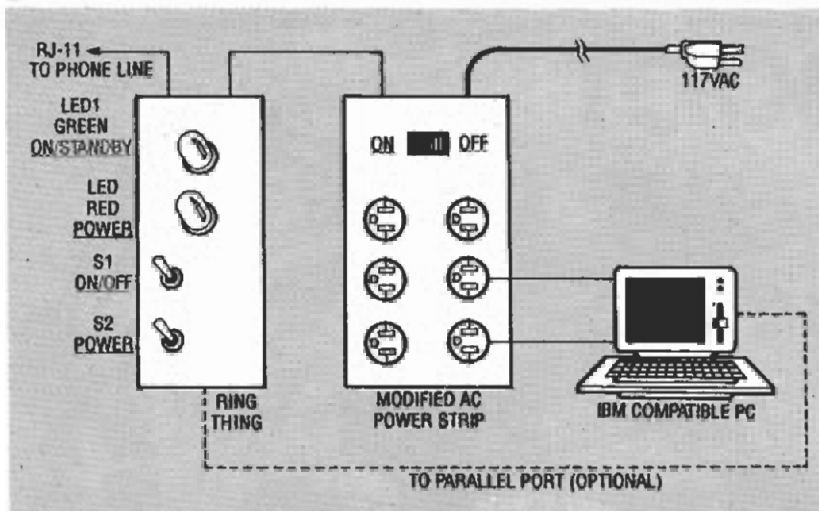


FIG. 1—RING-THING ALLOWS THE REMOTE CONTROL of any AC-powered device via standard telephone lines. An optional PC interface allows computer-controlled power-downs.

TABLE 1—RING-THING FEATURES

- Microprocessor-based design for user-friendly operation
- Compatible with all computer equipment
- Compatible with all standard business and home telephone lines
- Modular two-piece design for convenient mounting
- Automatically controls computer equipment power during modem or PC fax connection
- Provides security for computer modems
- Provides convenient manual on/off power control for computer equipment
- Computer-controlled power-down mode

MAIN BOARD PARTS LIST

All resistors are 1/4-watt, 5%, except as noted	
R1, R22—470 ohms	IC8—LM2931T-5.0, low-dropout regulator
R2, R7, R8, R10, R11, R12, R13, R21—100,000 ohms	BR1—W005 or RB151, 50-volt, 1-amp diode bridge
R3, R4—47,000 ohms	D1, D4—1N4148 or 1N914, switching diode
R5—22 ohms	D2, D3, D5, D6, D10, D11, D12—1N4003, 200-volt, 1-amp rectifier diode
R6, R17—10,000 ohms	LED1—T1-3/4 green LED
R9, R14—470,000 ohms	LED2—T1-3/4 red LED
R15—1000 ohms	MOV1—130-volt, 11-15 Joule surge suppressor
R23—1000 ohms, 1/2 watt	Q1—PN2222, general-purpose transistor
Capacitors	
C1, C2, C4, C5, C10, C11, C12, C13, C15—0.1 μ F, 50 volts, monolithic, radial	Other Components
C3, C6, C16, C18—10 μ F, 16 volts, electrolytic, radial	JU1, JU2—2-pin header with shorting block
C7, C8—27pF, 100 volts, COG ceramic (see text)	XTAL1—4.00-MHz quartz crystal, HC18 - HC49 pkg, or 4.00-MHz resonator (see text)
C9, C14—0.01 μ F, 100 volts, polyester, radial	SPKR1—8-16 ohms speaker, 1-2"
C17—470 μ F, 25 volts, electrolytic, axial	S1, S2—switch, SPST, NO, momentary, pushbutton, panel mount
Semiconductors	
IC1—MC68HC705K1, 8-bit CMOS microcontroller	Modular telephone cord, 6 feet
IC2—LM358N, low-power dual op-amp	Four-conductor cable, 22 AWG, 6 feet
IC6—74HCT14, CMOS hex inverter	IC Sockets, enclosure, screws, circuit board, etc.
IC7—CD4001, CMOS quad NOR gate	

applies AC power to the power strip. When the computer boots, the modem (or Fax) seizes the phone line to allow remote communications. One

ring is best for Fax transmissions, ten for modem communications.

Ring Pattern (Shared Mode)

Similar to Ring Counting mode,

except that AC power is enabled only if the caller allows the phone to ring 1-3 times, hangs up, and then calls back within 45 seconds. Pattern mode provides additional security over Counting mode; it also allows you to share one phone line among several devices, for example, by setting an answering or Fax machine to answer on the fourth ring.

Call duration of both modes is indefinite. As long as your modem or Fax adapter continues to seize the line, Ring-Thing will apply power. Five minutes after your device relinquishes the line, Ring-Thing removes power. The delay allows you to reestablish the connection if the phone call terminates accidentally.

Two front-panel pushbutton switches control Ring-Thing's operation: ON/STANDBY and POWER ON/OFF. They operate as follows.

ON/STANDBY enables remote control, indicated by an illuminated green LED, which also blinks when the phone line is in use.

POWER ON/OFF functions in place of the ON/OFF switch on the AC power strip to control power to all equipment plugged into the strip. Rather than fumble for the main switch on your power strip, you now simply tap this button to turn on your equipment. As a safety feature, you must push and hold the button momentarily to turn your equipment on or off. The adjacent red LED illuminates when the computer has been turned on manually. The LED blinks slowly if power was enabled by the phone ring mode; a faster blink rate indicates that power will shut off automatically within two minutes.

Remote control

Activating the system for remote control by a PC takes five simple steps.

1. Set your modem (or Fax board) to answer on 1-4 rings. See your board's documentation for instructions on how to do that.

2. Set up your computer so that your favorite modem (or Fax)

communications program executes automatically after the computer boots.

3. Plug Ring-Thing into the same telephone jack that your modem (or Fax board) uses. You can use the jack on the back of your modem (or Fax) usually labeled "Line."

4. Plug your computer, monitor, and other peripherals into Ring-Thing's AC power strip. Leave the power switches of the Ring-Thing's power strip and all the computer equipment in the on positions.

5. Plug in the Ring-Thing and enable Ring Detection by pressing ON/STANDBY.

At this point, Ring-Thing is armed and ready for action.

Optional power down

Have you ever started a program that you knew wouldn't finish for hours—like printing the OS/2 documentation files? Just start the program and let Ring-Thing power your PC down when it's through. This feature does not involve the tele-

phone system at all. What it does is allow a PC user to turn the computer's power off from within DOS.

By connecting Ring-Thing to a spare LPT port, you can use RT.EXE to send a power-off command. The command can be issued directly from the keyboard, or indirectly via a DOS batch file. Sixty seconds later, whatever is connected to the Ring-Thing will be turned off. The delay allows the computer to perform other batch operations (e.g., parking the hard drive). Power-down mode works with both ring-detection modes.

To send the power-down command while connected to LPT2, type the following: RT /LPT2 /OFF, followed by the ENTER key. You will hear a one-minute warning beep, and the red LED will flash. After one minute, the PC will shut off. To cancel power-down mode, merely tap S2.

Circuit overview

Ring-Thing consists of two

main functional units: the AC power strip and the control unit, as shown in Fig. 2. The power strip contains the AC sockets whose power is controlled, the control relay, and a 12-VAC transformer. The control unit contains the microcontroller and seven functional areas: a ring-detect circuit; LED drivers; a 12-volt power supply; speaker, LED, and parallel-port drivers; and switch and jumper inputs. Note that the control unit has three separate ground circuits: analog for the ring detector, digital for the microcontroller and functional units, and a separate relay ground. All the grounds come together at the power supply. Now let's look at each section of the circuit in more detail.

Detailed circuit description

AC Power Strip Ring-Thing uses a standard AC Power Strip, but modifies the wiring so that the output of the strip's ON/OFF switch also passes through the relay contacts, as shown in Fig.

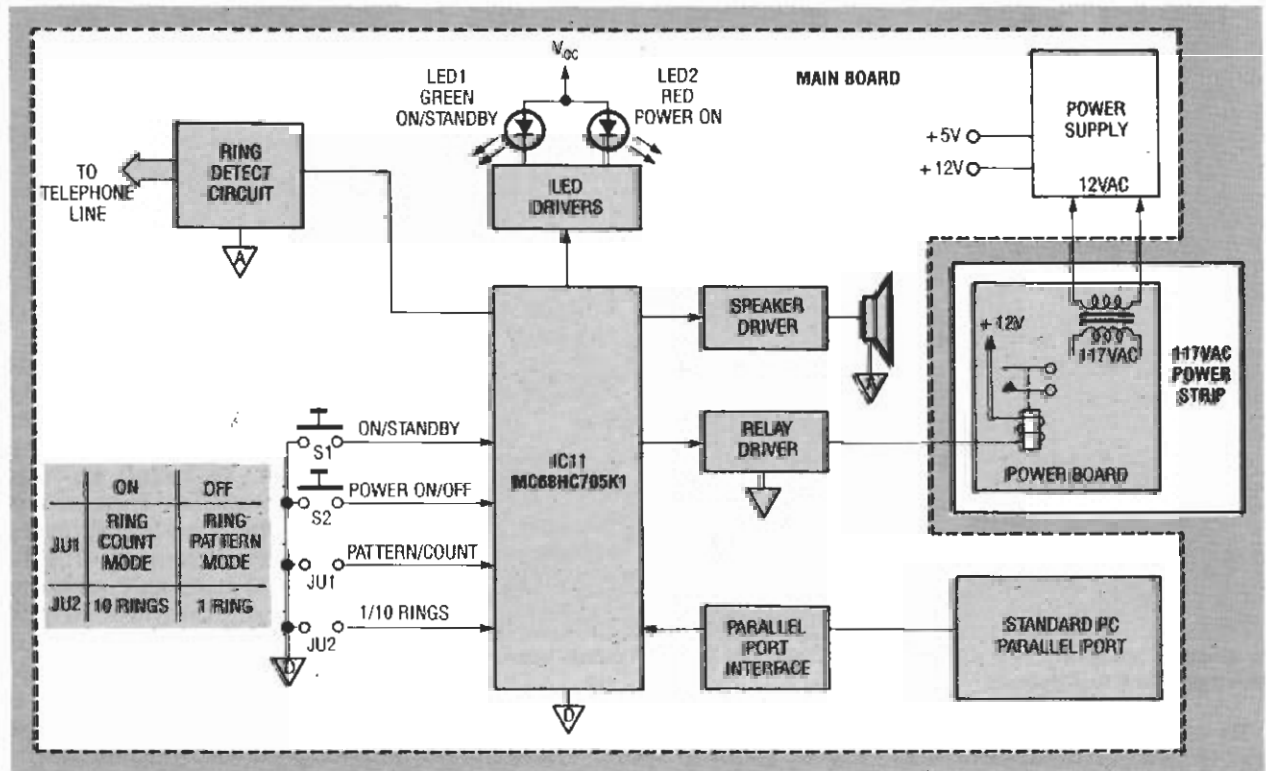


FIG. 2—RING-THING'S INTELLIGENCE is provided by an 8-bit microcontroller, the MC68HC705K1, that reads switch, jumper, and ring-detect inputs, and drives LED's, a speaker, a relay, and (optionally) a parallel-port interface. Note the three separate ground circuits.

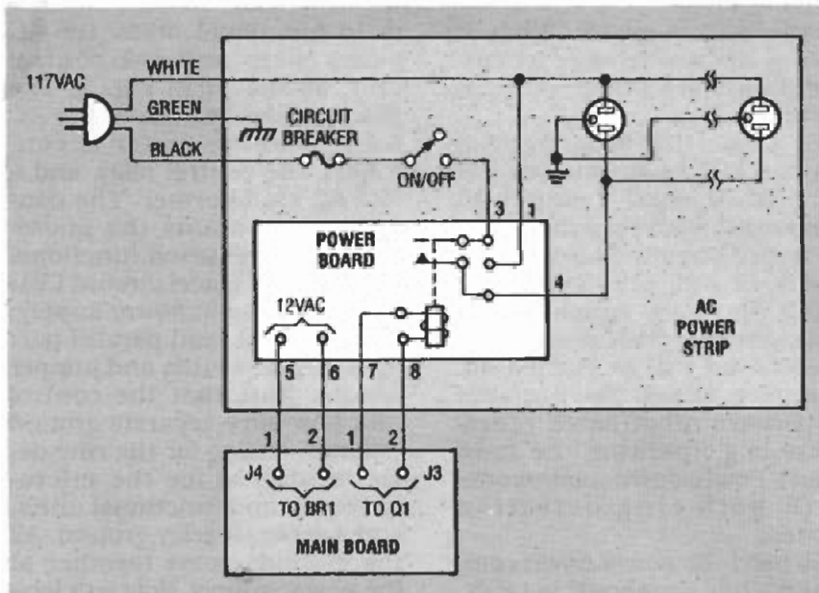


FIG. 3—THE AC POWER STRIP contains a 12-volt transformer and a 12-volt relay mounted on a separate circuit board. Wire the relay's contacts in series with the power strip's on/off switch.

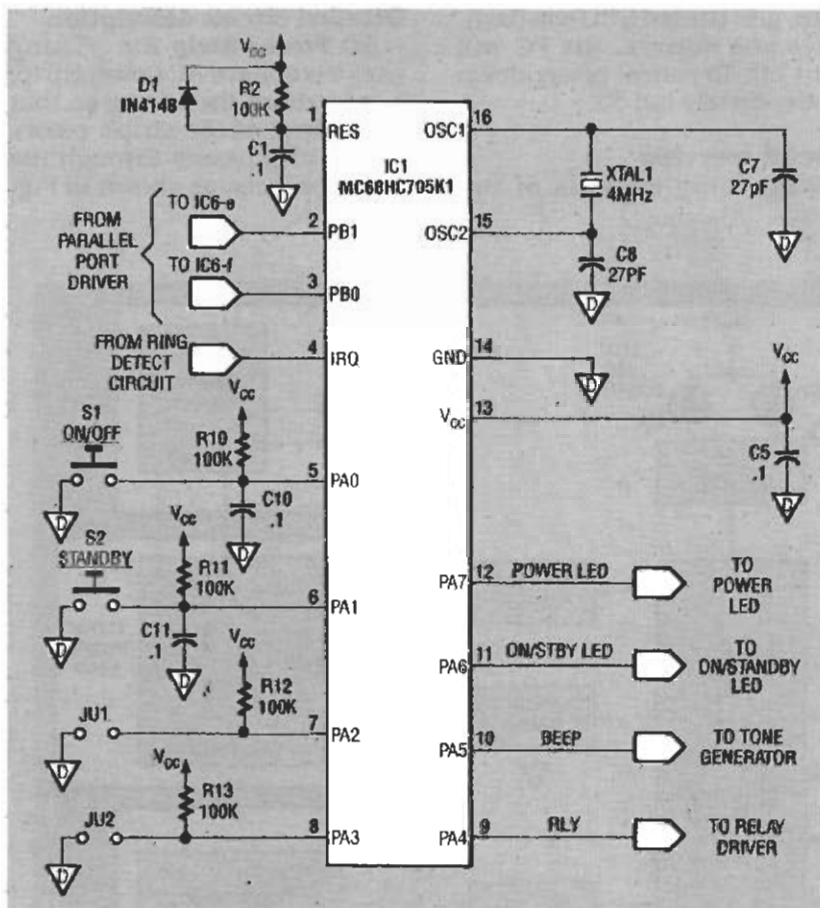


FIG. 4—MICROCONTROLLER AND INPUT SECTIONS of the main circuit board has seven inputs and four outputs.

3. To obtain power from the strip, the switch must be on and the relay must be energized. The power board (including the relay and power transformer) was designed to fit inside the

recommended power strip with little room to spare. There may be interference problems if you use other components.

Microcontroller Ring-Thing's intelligence is provided

POWER BOARD PARTS

RY1—Relay, SPST, 12V Coil, Guardian 1715-1A-12D
 T1—120VAC to 12VAC, 120 mA Transformer, Mouser 41PG120
 PC board, plastic strain reliefs, plastic spacers (#4 × 1/4"), 4-40 × 1/2" machine screws with nuts, 14 AWG stranded wire

OPTIONAL PC POWER-DOWN PARTS

IC3, IC4, IC5—PS2502-1 NEC Optoisolator
 D7, D8, D9—1N4148 or 1N914 signal diode
 R16, R18, R19, R20—2200 ohms
 5-conductor cable (22 AWG, 6 feet), DB25 25 Pin Male (Pin) Connector and Hood, control software

ADDITIONAL PARTS NOT SUPPLIED IN KIT

B1—9-volt NiCd battery, Duracell NC1604 or equiv.
 Multi-outlet AC power strip (see text) with 6-amp 3AG fuse and holder

ORDERING INFORMATION

The following parts are available from Digital Products Company, Attn: Thomas E. Black, 134 Windstar Circle, Folsom, CA 95630, 24 hr phone/FAX: (916) 985-7219. Ring-Thing Kit: (All components, programmed microcontroller, enclosure, PC board set, documentation, less PC power-down feature): \$79.95. PC power-down kit (parts, DB25 cable, software): \$9.95. Basic kit (PC board set, microcontroller, transformer, relay, software, documentation): \$59.95. PC board set (#RT001): \$24.95. Programmed MC68HC705K1 microcontroller: \$14.50. Six-outlet metal power strip with fuse kit: \$16.00. Rechargeable battery, 9-volt size, NiCd: \$7.00. Documentation package with schematic: \$4.75. PC software, 5" disk only, includes RT.EXE source: \$7.50. All orders add \$4.50 S&H (\$9.50 to Canada). CA residents add applicable sales tax. U.S. funds only. MasterCard, Visa accepted. Prices subject to change.

by IC1, a low-cost, 8-bit MC68HC705K1 made by Motorola. The microcontroller contains a central processing unit (CPU), as found in your desktop computer. However, it also incorporates 32 bytes of random-access memory (RAM), 504 bytes of read-only memory (ROM), 10 digital input/output lines, timer-based interrupt support, and external-interrupt support. In other words, it's a complete computer housed in a single IC—a 16-pin IC at that!

Of course the microcontroller needs software to operate; software is stored permanently in the internal ROM. Because the

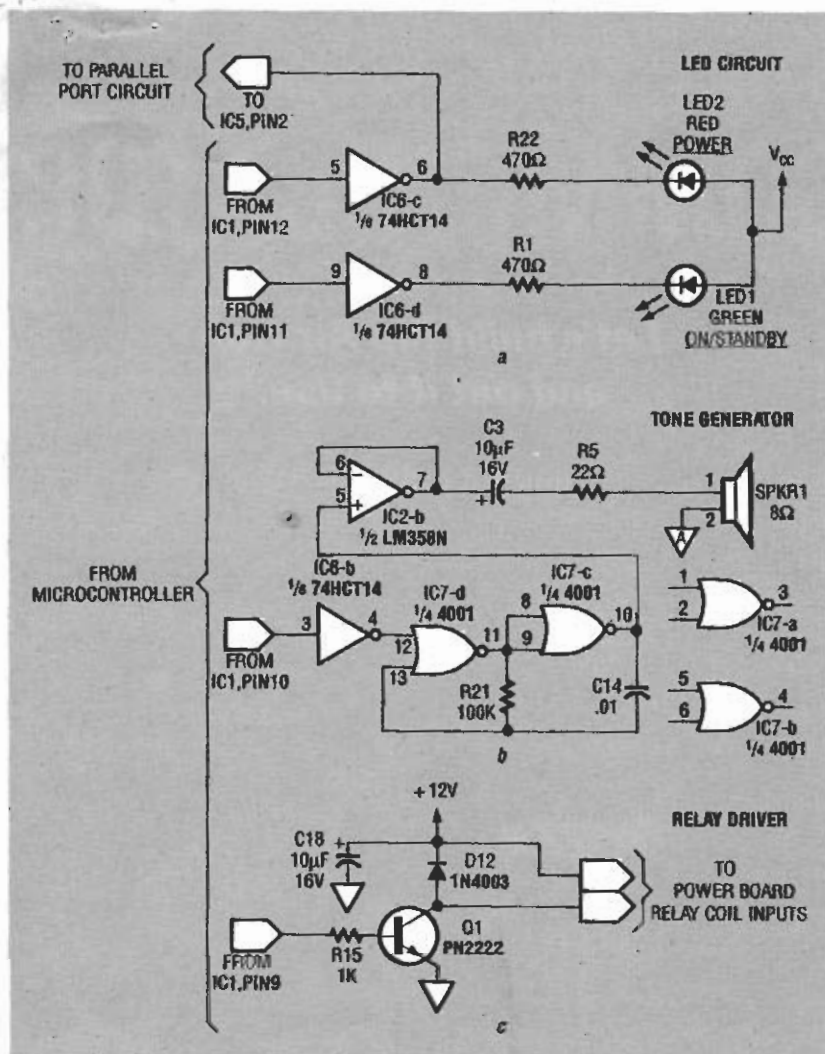


FIG. 5—SEPARATE MICROCONTROLLER OUTPUTS drive the LED (a), tone generator (b), and relay (c) outputs.

TABLE 2—LED STATUS INDICATION

AC power fail	On/Standby and Power-on LED's flashing rapidly
Ring detect on	On/Standby LED on
Phone ringing	On/Standby LED flashing rapidly
Phone line in use	On/Standby LED blinking slowly
Manual AC power	Power-on LED On
Ring invoked power	Power-on LED blinking slowly
AC power timeout	Power-on LED flashing rapidly (two-minute warning).

TABLE 3—RING-THING AUDIBLE ALERTS

Short beep	Power On/Off button pushed
Short modulated beep	On/Standby button pushed
Chirp sound	Phone ringing
Slow beep	AC power auto-turn off (one minute warning)

software is nonvolatile—it remains even when power is removed—it is called *firmware*. The firmware uses all 504 bytes of program ROM to implement a sophisticated real-time operat-

ing system. Major events (e.g., ring detection, tone generation, and LED and relay control) are interrupt driven, so all features work together seamlessly. The firmware uses the timer-based

interrupt to schedule tasks that need to be performed, and the external interrupt to monitor telephone-line activity. The firmware uses RAM for storing temporary data (e.g., current ring count, remaining time, and beep duration). Although there are only 32 bytes of RAM, it's more than enough for our application.

Firmware source code is not available; however, the author has made the object code available in S-record format. It is contained in the file RT.S19, available from the RE-BBS as part of RINGTHNG.EXE, and from the author directly, as mentioned in the Parts List. Because a special programmer is required, preprogrammed microcontrollers are available separately (see Parts List).

Figure 4 shows the microcontroller and switch/jumper input sections. Components C1, D1, and R2 provide a power-on reset function for IC1; C7, C8, and XTAL1 provide a steady 4-MHz clock.

Of the ten digital I/O lines, four (PA0-PA3) monitor the switches and configuration jumpers, two (PB0, PB1) monitor the PC's parallel port, and the remainder (PA4-PA7) drive the LED, tone generator, and relay circuits.

The PA0 and PA1 microcontroller inputs monitor the ON/STANDBY and POWER ON/OFF switches (S1 and S2, respectively). Although the switches are momentary-contact, normally-open switches, the software "debounces" them to emulate toggle switches.

The PA2 and PA3 inputs read the condition of JU1 and JU2. If JU1 is installed, then Ring-Thing operates in Ring Counting mode; if JU1 is not installed, then Ring Pattern mode.

If JU1 is installed (i.e., the user selected ring-counting mode), then JU2 determines the number of rings before applying power. If JU2 is installed, Ring-Thing waits 10 rings before answering; if JU2 is not installed, 1 ring.

Now let's look at the output circuits, shown in Fig. 5.

continued on page 85

BOOT YOUR PC REMOTELY

continued from page 59


Figure 5-a shows the LED circuit. Inverters IC6-c and IC6-d drive the LED's to provide the necessary sink current. (Note that IC6-c also connects to the parallel-port driver circuit, in which it drives an optoisolator.) The LED's provide several types of status information, summarized in Table 2.

Figure 5-b shows the tone-generator circuit, which is driven by PA5 of the microcontroller. The tone generator is a simple monostable multivibrator; R21 and C14 form an RC time constant circuit that causes IC7 to oscillate at about 1 kHz. Op-amp IC2-b then drives the speaker. The microcontroller can create different sounds by modulating the beep frequency. During normal operation, you will hear the sounds listed in Table 3.

Figure 5-c shows the relay-driver circuit. Transistor Q1 turns on whenever PA4 goes high; diode D12 protects transistor Q1 from voltage spikes that could occur when the coil is de-energized.

Next time

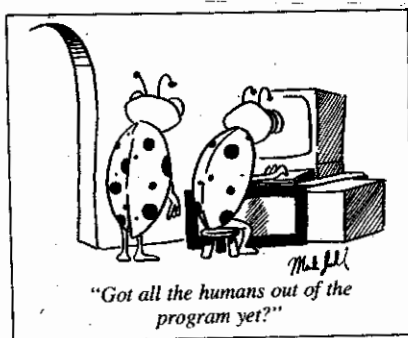We're out of space in this article. Next time we'll complete the circuit description and go on to build a Ring-Thing. Meanwhile, you might want to order parts and software. See you then! R-E



September 1993, Electronics Now

79



January 1993, Electronics Now

85