

Digital-I/O circuit adapts to many interface voltages

Steve Hageman, Windsor, CA

To test products in my R&D lab, I build many universal data-acquisition systems that connect to a PC or another controller through RS-232 links or LANs. These small systems typically include multiple ADC, DAC, and digital-I/O channels to control various hardware functions during

product design and development. Over the years, I have established a simplified analog-interface standard that spans a 0 to 5V range. On the digital side, many of the newer logic families no longer tolerate 5V inputs and have rendered 5V-only digital-I/O ports obsolescent.

To solve the problem, I designed a flexible digital-interface circuit around a MAX7301 I/O expander from Maxim Integrated Products (www.maxim-integrated.com) and a programmable linear-voltage regulator comprising a MAX1658 adjustable linear-voltage regulator under the control of a MAX5400 256-position, digitally programmable potentiometer. This circuit provides a programmable interface matching the logic levels of ICs that require 2.5, 3, 3.3, and 5V power supplies.

Two SPIs (serial-peripheral inter-

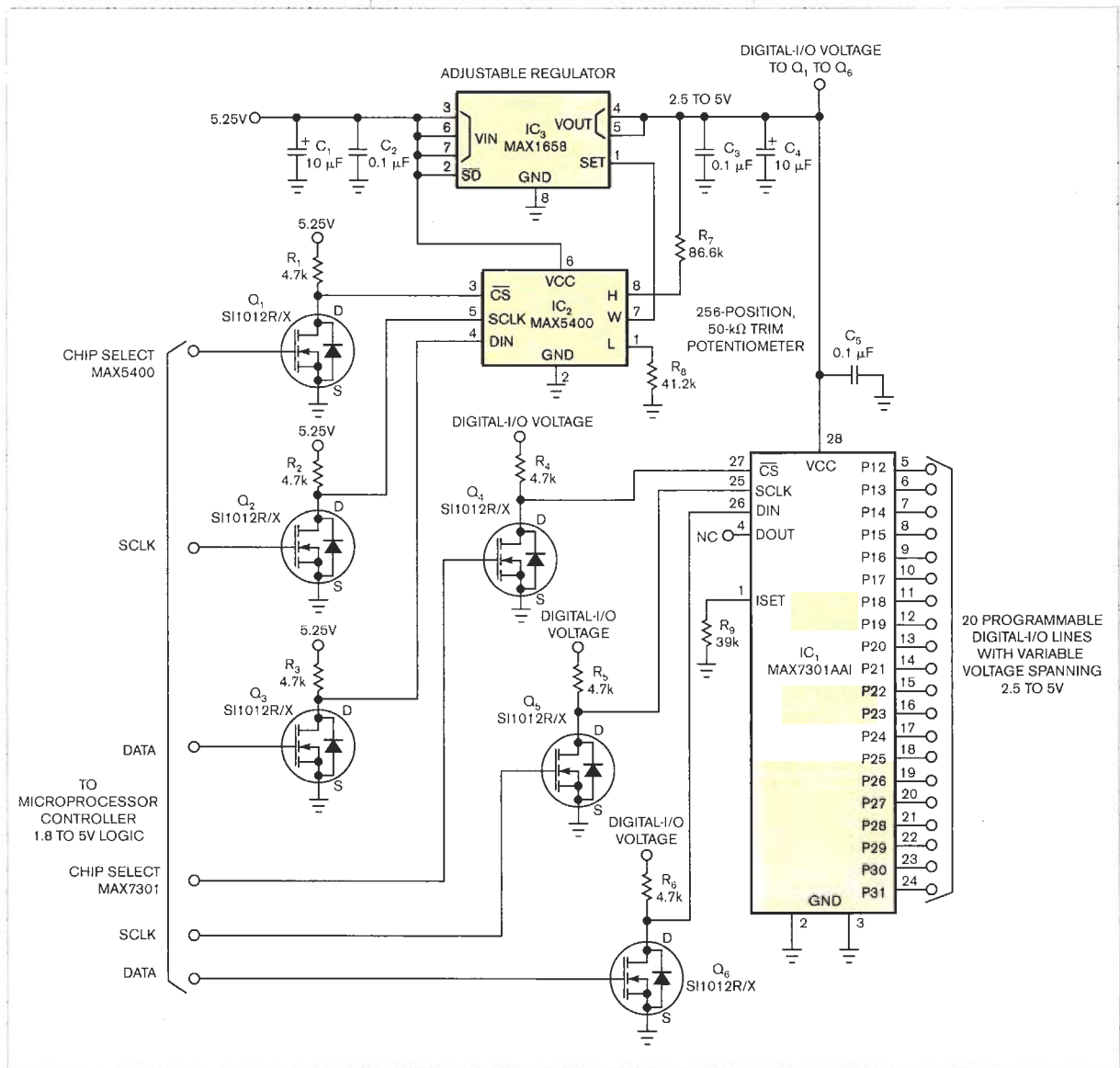


Figure 1 A programmable power supply sets voltage thresholds for a universal digital-I/O device.

faces) control all 20 of the MAX7301AAI's input and output pins and voltage thresholds (Figure 1). Unlike some SPI-port expanders that include weak, resistor-only pullups, the MAX7301, IC₁, features true, active-pullup, "totem-pole" outputs that can source higher currents. When powered by the SPI-programmable linear regulator, the MAX7301's outputs can deliver logic levels of 2.5 to 5V. The programming interfaces for both devices comprise two three-wire (plus ground) SPI connections that use only six of the controller's signal lines.

Six Vishay (www.vishay.com) Si-1012R low-gate-voltage-threshold N-channel MOSFETs, Q₁ through Q₆, isolate the controllers' fixed-output-voltage levels from IC₁'s variable-input-threshold voltages. Although any of several IC-level-translator ICs work equally well, the inexpensive MOSFET buffers occupy small footprints on the interface's PCB (printed-circuit board). For operation at serial-interface clock

UNLIKE SOME SPI-PORT EXPANDERS THAT INCLUDE WEAK, RESISTOR-ONLY PULLUPS, THE MAX7301, IC₁, FEATURES TRUE ACTIVE-PULLUP, "TOTEM-POLE" OUTPUTS THAT CAN SOURCE HIGHER CURRENTS.


rates approaching IC₁'s 26-MHz maximum, optimize the values of resistors R₁ through R₆ to provide adequate rise times at the selected clock rate. These values are adequate for operation at the 1-MHz SPI clock rate that a low-power microcontroller produces.

To alter the circuit's output-voltage level, IC₂, a 256-step Maxim MAX5400 digital potentiometer, con-

trols IC₃, a Maxim MAX1658 adjustable-voltage linear regulator. Writing all zeros to IC₂ sets IC₃'s output voltage to slightly more than 5V, and writing all ones (255 decimal) to IC₂ reduces IC₃'s output voltage to slightly less than 2.5V. To compensate for component tolerances, the circuit provides enough voltage overrange to cover the full 2.5 to 5V range. Writing 128 (decimal) to IC₂ should produce a nominal 3.25V output. Measure IC₃'s actual output voltage and subtract it from the nominal voltage to produce an offset count for calibration correction.

In operation, the host controller sets IC₃'s regulated output voltage through IC₂ and determines the maximum voltages of IC₁'s logic inputs and outputs. Next, the controller configures IC₁'s inputs and outputs as necessary for the interface task at hand. The MAX7301's standard CMOS logic-threshold voltages of 0.3 to 0.7 times its supply voltage for low and high inputs, respectively, interface with other CMOS parts. **EDN**

AS1923 - Quad Voltage Supervisor

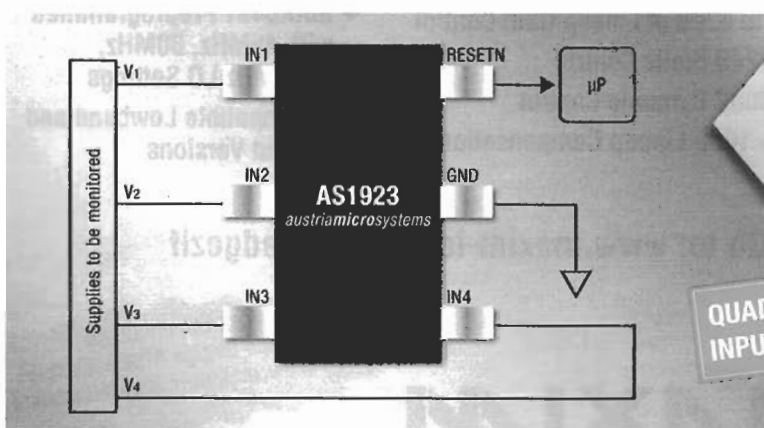

- ▶ 1.0 to 5.5V Supply Voltage
- ▶ Quad Sense - Single Reset
- ▶ Adjustable or Fixed Thresholds
- ▶ Small SOT23 package

QUAD INPUT

The AS1923 allows to pull a single reset if one of its four supervised inputs goes below a certain threshold.

Ideal for multi-supply applications where small size and performance are critical as in FPGA and DSP based intelligent instruments and any critical CPU monitoring.

Part No.	Thresholds (16 variants)				Supply V	Supply Current µA (typ)	Package
	V(1)	V(2)	V(3)	V(4)			
AS1923	5, Adj	3.0, 3.3	2.5, 1.8, Adj	-5, 1.8, Adj	1.0 to 5.5	55	SOT23-6

Get more technical info on austriamicrosystems complete portfolio of High Performance Analog solutions at www.austriamicrosystems.com

West Coast (408) 345-1790 East Coast (919) 676-5292
Order samples at <https://shop.austriamicrosystems.com>

austriamicrosystems
a leap ahead