

# CMOS DACs act as digitally controlled voltage dividers

John Wynne and Liam Riordan, Analog Devices, Limerick, Ireland

➔ Digital potentiometers, such as Analog Devices' ([www.analog.com](http://www.analog.com)) AD5160, make excellent digitally controlled voltage dividers in applications in which 8-bit resolution is acceptable. This Design Idea shows how to use a CMOS DAC as a voltage divider in applications requiring higher resolution.

Millions of CMOS R2R (resistor/two-resistor)-ladder DACs have found use in attenuator applications in which an external op amp acting as a current-to-voltage converter forces one current-output terminal to a virtual ground. The reference input to the DAC can be ac or dc as long as the op amp can produce the desired output voltage. A phase inversion is normal between input and output, so the circuit requires dual power supplies.

Figure 1 shows a way to rewire this simple circuit to avoid the phase inver-

sion and to operate with a single supply. In this configuration, the DAC acts as a digitally programmable resistor, and the DAC's code changes the effective resistance between the input voltage and the  $I_{OUT1}$  output-current terminal of the DAC. Figure 2 shows a practical implementation using one-

half of an Analog Devices AD5415 dual 12-bit current-output DAC operating as a voltage divider. This figure omits the DAC's control lines for clarity. Op amp  $A_1$  forces the voltage on the  $I_{OUT2A}$  output-current terminal to follow the voltage on the  $I_{OUT1A}$  output-current terminal. This approach prevents a voltage differential from developing between these two bus lines, which would result in the application of different gate-source voltages across the internal DAC switches and a deterioration in the DAC linearity.

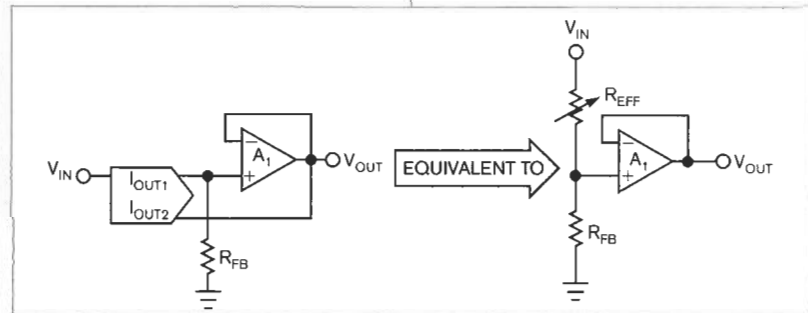


Figure 1 This simple circuit avoids a phase inversion and operates with a single supply. In this configuration, the DAC acts as a digitally programmable resistor.

Wire the split-feedback resistors,  $R_{FB}$  and  $R_1$ , to produce a composite-feedback resistor equal in value to the DAC's ladder impedance,  $R$ . For this arrangement the circuit-transfer function is  $V_{OUT}/V_{IN} = (R)/(R_{EFF} + R)$ , where  $R_{EFF}$  is the effective DAC resistance that is under digital control. Its value is  $R(2^n)/N$ , where  $n$  is the resolution of the DAC and  $N$  is the binary equivalent of the digital-input code. Substituting the second equation

into the first and assuming zero DAC gain error, the circuit-transfer function for a 12-bit DAC reduces to  $V_{OUT}/V_{IN} = 1/(1 + 4096/N)$ . With all switches off, the effective impedance between the reference voltage and the  $I_{OUT1A}$  terminal is infinite, so the output voltage starts at 0V when you load zeros into the DAC. The output voltage increases linearly with increasing

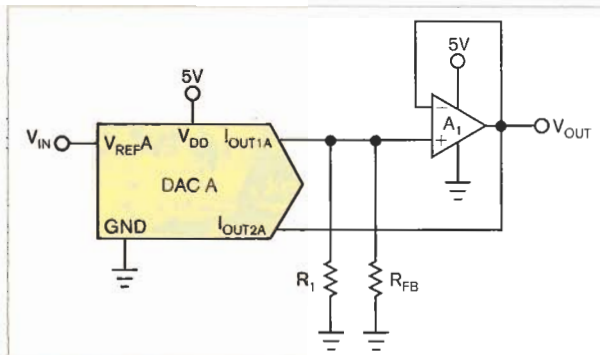


Figure 2 This practical implementation of the circuit in Figure 1 uses one-half of a 12-bit-current-output AD5415 dual DAC that operates as a voltage divider.

code, ideally to approximately half the input with all ones applied to the DAC.

The threshold voltage of the DAC's internal N-channel-CMOS switches limits the maximum value of the output voltage, so not all configurations can achieve the full code range. The switch-gate voltage remains at the  $V_{DD}$  voltage, and the switch-source volt-


age rises with the voltage on  $I_{OUT1A}$ . As this voltage increases, the on-resistance of the switches becomes large and indeterminate, leading to a flattening of the output voltage and the cessation of the circuit as a predictable voltage divider. For proper operation, the  $V_{DD}$  voltage must be a few volts higher than the maximum output voltage—that is, half the input voltage. Otherwise, the input voltage must be less than two times the  $V_{DD}$  voltage minus 3V. With a

$V_{DD}$  voltage of 5V, the AD5415 operates linearly to approximately a 3.33V output but then flattens. If a wider output-voltage range is necessary, you could use Analog Devices' AD7541A, which uses a 15V power supply, in place of the AD5415. This substitution extends the usable output-signal range to approximately 7V.<sup>EDN</sup>

## a leap ahead in DC/DC-converters
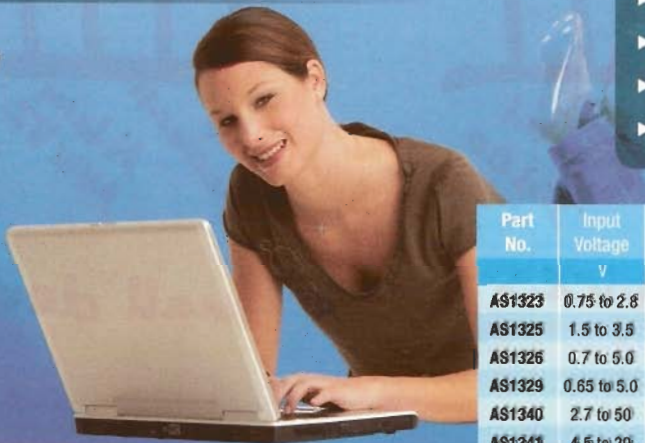
### Perfect for battery powered devices

- ▶ Small size
- ▶ Highest efficiency
- ▶ Adjustable output voltages
- ▶ Supporting all battery types



### AS1341

- ▶ 20V Maximum Input Voltage
- ▶ 600mA @ 5V from 12V Input
- ▶ 96% Efficiency
- ▶ 1.25V Minimum Output Voltage
- ▶ 12µA Low Quiescent Supply Current

Part No.	Input Voltage V	Output Voltage V	Output Current mA	Efficiency %	Package
AS1323	0.75 to 2.8	2.7	100	85	TSOT23-5
AS1325	1.5 to 3.5	3.3	300	96	SOT23-6
AS1326	0.7 to 5.0	3.3, 2.5 to 5.0	650	96	TDFN-10
AS1329	0.65 to 5.0	2.5 to 5.0	315	95	TSOT23-6
AS1340	2.7 to 50	2.7 to 50	100	90	3x3 TDFN-8
AS1341	4.5 to 20	1.25 to $V_{IN}$	600	96	3x3 TDFN-8

Free samples online at **ICdirect**  
<https://shop.austriamicrosystems.com>

**ae** austriamicrosystems

a leap ahead in analog

West Coast (408) 345-1790 · East Coast (919) 676-5292  
[www.austriamicrosystems.com](http://www.austriamicrosystems.com)