

# Scheme provides high-side current sensing for white-LED drivers

Dimitry Goder, Sipex Corp, San Jose, CA

**W**HITE LEDs FIND WIDE use in back-lighting color-LCD screens in most portable devices, such as cellular phones, PDAs,

and MP3 players. Multiple LEDs often connect in series to ensure that the same current flows through every LED. To forward-bias these LEDs, a voltage of 10 to 16V comes from an inductor-based boost regulator, such as an SP6690. However, white LEDs are behind the display, whereas boost regulators are on the main pc

board, and it is important to minimize the number of interconnects. You can obtain the best results if you implement high-side and differential-current sensing. In this case, the boost regulator's output looks like a high-voltage true current source. Of course, LEDs need to connect to ground at some point, but it is unimportant where they connect. For example, the display itself can locally pick up ground. This approach allows you to ef-

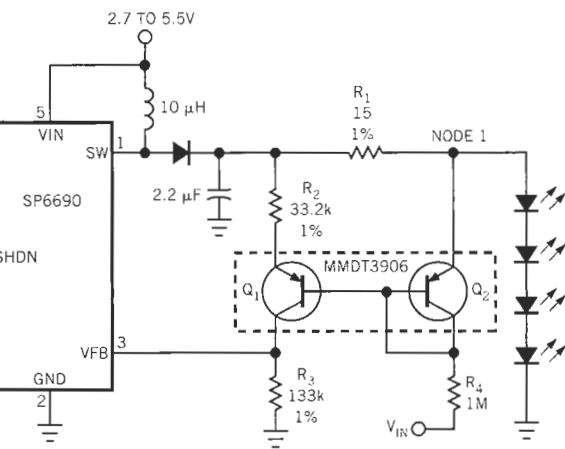


Figure 1

This circuit provides high-side current sensing for driving a string of white LEDs.

fect a "single"-wire connection. The simple circuit in **Figure 1** shows the implementation of the idea.

$R_1$  acts as a current-sense resistor. The diode-connected  $Q_2$  level-shifts the voltage at Node 1 and applies it to the base of  $Q_1$ . These transistors come in one package and provide closely matched  $V_{BE}$  voltage when they operate at the same current. Because the  $V_{BE}$  values match, the emitter of  $Q_1$  is at the same voltage as

Node 1. As a result, the voltage across resistor  $R_2$  matches the drop across  $R_1$  and produces  $Q_1$  emitter current that equals  $V_{R1}/R_2$ . This current flows to  $Q_1$ 's collector and creates a voltage drop across  $R_3$ . The boost-regulator SP6690 regulates the voltage across  $R_3$  at 1.22V, the IC's internal reference voltage.  $R_4$  provides current bias for  $Q_2$ . The value of  $R_4$  allows the  $Q_1$  and  $Q_2$  collector currents to match. You calculate the

value of  $R_1$  as follows:  $R_1 = R_3 \times (V_{OUT} - V_{IN} - V_{BE}) / 1.22$ , where  $V_{OUT}$  is the combined LED forward voltage. The output current is  $I_{OUT} = 0.3A / R_1$ . The circuit in **Figure 1** sets  $I_{OUT}$  at 20 mA, but you can adjust it by using a different  $R_1$  value. Note that you could return  $R_4$  to ground, but it instead connects to  $V_{IN}$ . This connection removes quiescent current through the resistor and  $Q_1/Q_2$  when the SP6690 is in shutdown mode. □