

Infrared light-beam relay

Interested in capturing spectacular wildlife shots like the one on our front cover? You can, by building this new infrared relay unit. It uses only two CMOS ICs plus a few transistors, and can also be used as a shop entry monitor, an "invisible" burglar alarm, or even as a target game.

by RON DE JONG

Light beam relay systems are popular for many applications but most suffer the disadvantage of using a visible light beam. These circuits are invariably quite limited in range, are critical to set up and adjust, and can be falsely triggered by changing ambient light conditions. Indeed, most simple light beam relay systems are virtually useless in bright sunlight and are suitable only for fixed installations indoors.

All these problems are overcome in the circuit presented here. It uses a modulated beam of infrared light for greatly improved range and sensitivity, and will operate reliably in conditions ranging from total darkness to bright sunlight without adjustment. Other advantages include insensitivity to changing ambient light levels and the invisible nature of the beam itself (important in burglar alarm applications).

One of our photographers was quick to realise that the unit could be used as a camera trip for photographing wildlife.

The receiver and transmitter are both battery powered so the relay and camera unit can be quickly set up and left unattended. If a bird or other animal interrupts the infrared beam, the relay triggers a motor-driven camera and flash and the camera winds on ready for the next unsuspecting subject. The results, as you can judge by our front cover and some of the other photographs in this article can be spectacular.

The invisibility of the infrared beam also makes the relay ideal for use as a burglar alarm. The relay could be positioned across an appropriate doorway or even across a whole room so that when the invisible beam is broken by an intruder, an alarm is activated. Since the unit is battery-powered, it is completely portable and easy to set up in any location. Alternatively, the unit can be powered from a 9V DC plugpack and

the batteries used as a back up.

Conventional applications such as a shop entry indicator are also possible, or it could be used to automatically open and close doors. In the industrial field, an infrared relay can be used for counting objects on conveyor lines etc.

We also found that with a slight modification we could make the relay operate as a simple target game. In this case, the infrared source can be fitted inside a toy gun. When the gun is aimed directly at the sensor and the trigger pressed, a buzzer in the receiver sounds to indicate a "good shot".

Physically, the infrared relay consists of a transmitter and a separate receiver, both of which are housed in small plastic zippy boxes. Each unit is powered by its own 9V battery (Eveready 216 or similar) and these should provide about 50 hours continuous operation. Battery life can be increased by using alkaline cells if desired.

An open-collector transistor is used at the output of the receiver and can be used to activate an internal buzzer, a relay, or other low power devices. For



Taken from colour slides, these b&w reproductions do not do justice to the actual results. Note that the series is NOT in sequence.

photographic work, the open-collector output can be used to directly trigger most motor-driven cameras.

The range of the relay – ie the maximum distance between transmitter and receiver – is about five metres in sunlight. No lenses are used and no adjustment of sensitivity is required – just point the transmitter in the general direction of the receiver and you're in business. If greater range is desired, the transmitter current can be increased (more on this later).

HOW IT WORKS

Looking now at the circuit diagrams for the transmitter and receiver we can see that two CMOS ICs and six transistors are used. The circuit is more complex than the usual light beam relay – which typically includes a light bulb, a lens and a phototransistor – but then it has quite a few more features.

The source of light in the transmitter is an infrared LED and rather than merely providing a continuous source of light, it is flashed on and off at 10kHz. This is done so that the receiver can selectively amplify the signal from the transmitter and completely reject ambient light. The result is a high degree of sensitivity without any need of adjustment and it also allows us to use quite low current drive through the transmitting LED.

A standard three-inverter CMOS oscillator is used in the transmitter and consists of gates IC1a,b,c from a 4011 quad NAND package. The frequency of the oscillator is determined by the 4.7k Ω resistor and .0068 μ F capacitor and is nominally 10kHz. Gate IC1d permanent-

ly enables the oscillator, since its output is always high.

Some readers may be wondering why IC1d has been included in the circuit. Why not simply connect pin 2 directly to the positive supply rail? The reason is simply that the transmitter printed circuit board pattern is exactly the same as that used in a previous project (Infrared

The completed infrared relay receiver together with its companion transmitter (right). Both units are compact, battery powered and portable.

Remote Volume Control, October 1979). The circuit configuration, however, is slightly different and leaving IC1d in circuit happens to be the easiest way of adapting the board for its present application.

Either way, it makes no difference to circuit operation.

The CMOS oscillator drives an output stage consisting of a BC547 transistor (Q1) and two infrared light emitting diodes. The infrared diodes used are

quire the greater range, otherwise the relay may not trip reliably close in due to reflections caused by the high light output.

Infrared light generated by the LEDs is picked up at the receiver by a special infrared photodiode. This is also a Philips device type number BPW50, and is


specifically designed to match the CQY89A LED. The BPW50 also has an integral infrared filter that almost completely rejects visible light.

Referring to the circuit diagram of the receiver, the photodiode is connected with its cathode to the +9V rail via an RC decoupling network, while the anode is connected via a 470k Ω resistor to ground. In operation the photodiode acts as a current source, ie it generates a current proportional to the incident light. This current signal is converted to a voltage signal by the 470k Ω resistor.

Clearly the larger the resistor value is series with the photodiode the greater

Philips type CQY89A. They are plastic-pack devices and are similar in appearance to the familiar red LED except that the plastic encapsulation is a deep violet colour.

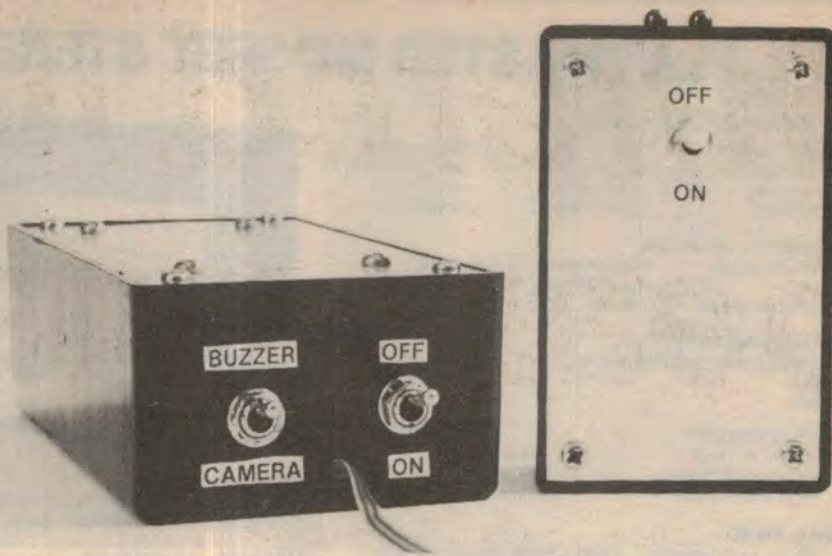Current drive through the two LEDs is limited by the 680 Ω resistor. If greater range is required, this resistor may be reduced to a minimum value of 150 Ω with a consequent adverse effect on current consumption. Do not reduce the value of the resistor unless you do re-





The completed target game transmitter inside a plastic gun. Although the PCB layout differs from the overlay, the two are electrically identical.

.068 μ F capacitor will charge up via the 100k Ω pull up resistor to the transition voltage of the CMOS gate. IC1d's output will then suddenly switch low, disabling the oscillator. The total period for which the oscillator is enabled is set by the time constant of the .068 μ F capacitor and 100k Ω resistor, ie about 7ms.

The 1 μ F tantalum capacitor is included to provide switch debouncing.

Whenever the trigger button is pressed therefore, a brief 7ms 10kHz pulse of infrared light is emitted. This will normally trigger the receiver, regardless of the direction in which the transmitter is pointed. Clearly this is unsuitable for a target game so when the transmitter is installed in a suitable plastic housing, say a toy gun or rifle, the light output from the infrared LED

has to be collimated or restricted to a narrow beam.

While the beam could be collimated with a lens, a far simpler solution is to use two or more opaque discs with holes drilled in their centres. If the LED and discs are lined up and spaced at say 4cm intervals, and if the holes are sufficiently small, quite a narrow beam results. A single disc made of aluminium foil with a small pin hole also gave good results.

Note that very little of the LED's output is actually used and this is why it is pulsed on so hard.

The case used for the transmitter is up to the constructor but as a guide we have included a photograph of one unit we built. We used a discarded gun from a TV game and found it quite easy to adapt to its new role.

PARTS LIST

RECEIVER

- 1 PC board, code 81ir4, 97 x 46mm
- 1 zippy box, 130 x 68 x 41mm
- 2 miniature SPDT toggle switches
- 1 Solid state buzzer
- 1 large LED & mounting bezel
- 1 9V battery, Eveready 216 or equivalent
- 1 battery clip to suit
- 1 74C14 CMOS Schmitt trigger IC
- 1 2N5485N channel JFET
- 3 BC549 NPN transistors
- 1 BC337 or BC547 NPN transistor
- 1 BPW50 infrared photodiode
- 3 1N4148 diodes
- 1 OA91 diode (optional for battery back up)

RESISTORS: (1/4W, 5%)

- 3 x 1M Ω , 1 x 470k Ω , 2 x 100k Ω , 1 x 68k Ω , 1 x 47k Ω , 1 x 15k Ω , 2 x 10k Ω , 1 x 2.7k Ω , 2 x 330 Ω , 1 x 150 Ω , 1 x 100 Ω , 1 x 47 Ω

CAPACITORS

- 2 100 μ F 16VW PC electrolytics
- 1 47 μ F 16VW PC electrolytic
- 1 10 μ F 16VW PC electrolytic
- 2 0.1 μ F 25VW tantalum
- 1 .01 μ F greencap
- 2 .0068 μ F greencap
- 1 .0022 μ F greencap
- 1 .001 μ F greencap

RELAY TRANSMITTER

- 1 PC board, code 81rc4c, 61 x 42mm
- 1 zippy box, 83 x 54 x 28mm
- 1 SPDT miniature toggle switch
- 1 9V battery, Eveready 216, or alkaline equivalent
- 1 battery clip to suit
- 1 4011 CMOS quad NAND gate
- 1 BC337 or BC547 NPN transistor
- 2 CQY89A infrared LEDs
- 1 10 μ F 16VW electrolytic capacitor
- 1 .0068 μ F greencap capacitor


RESISTORS (1/2W, 5%)

- 1 x 100k Ω , 1 x 10k Ω , 1 x 4.7k Ω , 1 x 680 Ω

TARGET GAME TRANSMITTER

- 1 PC board, code 81rc4c, 61 x 42mm
- 1 suitable plastic gun (see text)
- 1 momentary contact pushbutton
- 1 9V battery, Eveready 216 or alkaline equivalent
- 1 battery clip to suit
- 1 4011 CMOS quad NAND gate
- 1 BD263 NPN Darlington transistor
- 1 CQY89A infrared LED
- 1 1000 μ F 10VW axial lead electrolytic capacitor
- 1 1 μ F 16VW tantalum capacitor
- 1 .068 μ F greencap capacitor
- 1 .0068 μ F greencap
- RESISTORS (1/4W, 5%)
- 2 x 100k Ω , 2 x 10k Ω , 1 x 4.7k Ω , 1 x 22 Ω .

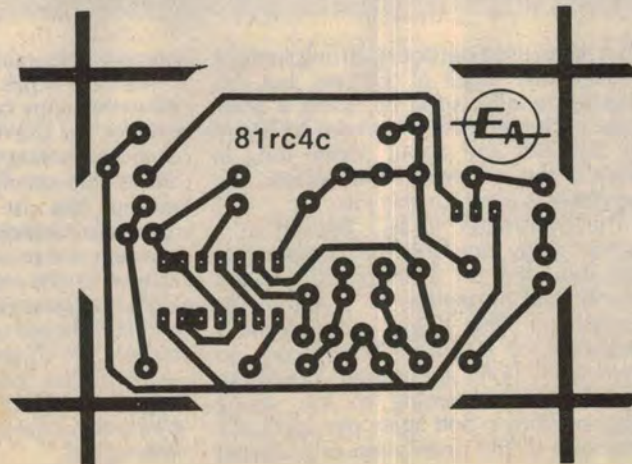Actual size artwork for the transmitter PCB. The same board is used for both the relay transmitter and the target game transmitter.





THE SETUP! (left): this retouched photograph shows the setup used by Sungravure photographer Bob Donaldson to capture the superb shot on our front cover. The transmitter and receiver units are mounted on wooden beams, and arranged so that the Infrared Relay is triggered as a bird comes in to land at a food table (centre foreground)!

Photographic details are as follows: Camera — 35mm Leica R3 SLR fitted with motor drive (essential) and a


250mm lens; Flash rate — 1/2,500s (high speed necessary to freeze wing motion); Film — Kodak EPR ASA64; Aperture — F8.

In practice, the relay units are moved closer together than shown here — just outside the picture area — so that the subject will be correctly centred. The camera is mounted about 1 metre from the subject while two flash units with variable power ratio controls are used, one on either side of the camera.

that the earth track on the PCB goes to one of the mounting holes so that when the board is mounted the lid is earthed. This is to provide some measure of shielding.

Now drill holes in the box for the on/off and buzzer/camera switches S1 and S2, as well as an exit hole for the camera lead. Alternatively use a DIN socket to mate with a suitable camera lead. Drill a 10mm hole for the light beam to enter the receiver, positioning it so that the centre of the hole lines up with the centre of the BPW50 photodiode.

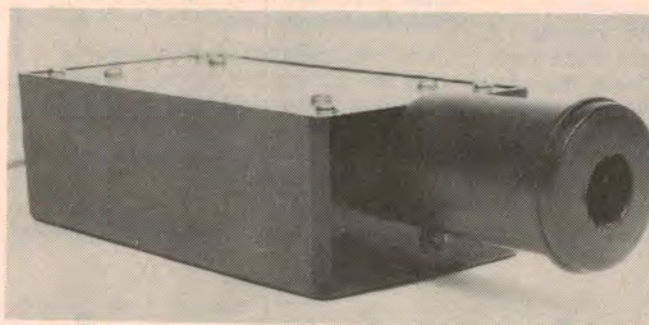When the unit is fully assembled the photodiode should be recessed about 20mm from the light beam entry hole. This does not reduce the range of the unit but is intended to prevent direct light from falling on the BPW50 and thus reducing its sensitivity. We still found



A plastic film canister makes an ideal light-tube for the receiver.

that when used outdoors, strong sunlight reduces the range of the unit, but this can be readily cured by fitting a small tube of non-reflective material 20-30mm in diameter and about 50mm long in front of the receiver. A black plastic film canister is ideal for this job.

The transmitter is also housed in a plastic zippy box and the components are mounted on a single PCB coded 81rc4c and measuring 61 x 42mm. As mentioned, this board was originally designed for a remote control unit so quite a few holes are unused. Mount the components according to the wiring diagram shown and again pay particular attention to the orientation of polarised

components, including the infrared LEDs.

The only holes which need to be drilled in the zippy box are two holes at one end for the CQY89A infrared LEDs and a single mounting hole on the aluminium lid for the on/off switch. This done, the wiring can be completed and the transmitter/receiver combination tested.

Switch the receiver on and switch the output to the internal buzzer and LED. With the transmitter off, both the buzzer and LED should turn on. Now switch the transmitter on and aim it at the receiver — the buzzer should stop. Finally, check that the buzzer/LED combination is activated whenever the beam is interrupted.

We estimate that the current cost of parts for this project is approximately

\$40

including sales tax.