# **IR-related ASCII Schematics**

Contents:

- 1. Infra Red Remote Transponder
- <u>2. Cheap 40KHz clock</u>
- <u>3. A very STABLE 40khz generator</u>
- 4. Minimizing SUN's noise in IR reception
- <u>5. Build an Infrared night scope</u>
- 6. Decoding IR Remote Controls
- 7. IR 'slotted switch' sensor

[Document Version: 1.00] [Last Updated: 12/12/96]

#### 1. Infra Red Remote Transponder


From: squish@endor.uucp (Shishin Yamada)


[...] I built a remote-transponder, which lets me send signals from a small receiver into closed (opaque door) cabinets, and around corners, etc. Anyways, the cheif problem is just stray environmental noise with any slowly changing amplitude modulated IR signal (lots of 60 Hz noise, and sunlight noise). Most IR remotes work around a 40KHz carrier, so that they can just pulse this digitally, and just bandpass filter it at the receiving end. This boosts the range of unfocused IR remotes to tens of feet (around 20-30 feet). Adding two IR Leds helps alot, by sending out more IR signals.

Anyways, the following is a cutout from the group sci.electronics. Most of which had been posted in the past month (I guess many news-servers might not go back one month, so I re-posted. Hope nobody minds). There is included transmitter and receiver modules. Personally, I find the Sharp IR Receiver module (avaiable at Radio Shack) to be the easiest darn thing to use. You just pop in +5V and ground, and you get the demodulated signal out (a high/low version of whatever was riding on the 40KHz IR signal). It comes with simple application notes. Hope this info helps you out.

Oh, lastly, if you're looking for ANALOG transmitters, I would look into Radio-Electronics recently for posts about their "Air-Hop" voice transmitter, or into Forrest Mims III "Circuit Cookbook." They both show how to do FM modulation onto IR (much, much better than AM).

#### IR DETECTOR CIRCUIT

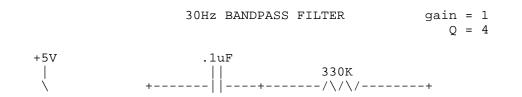

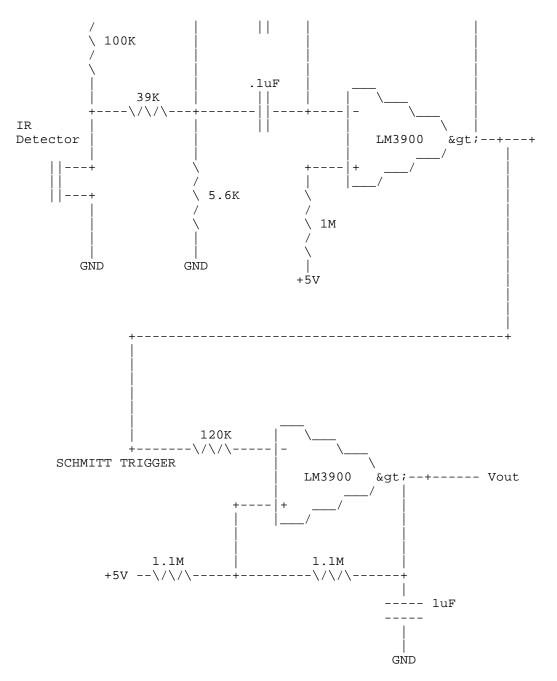


#### Notes

- The LM3900 is a quad unipolar op-amp IC. Vcc of this chip must be on +5V DC.
- I found that the 100K pull-up resistor on the IR detector provided the optimum sensor performance. Any increase or decrease in the resistance caused a decrease in the signal quality from the IR detector.
- The 0.1uF capacitors that are part of the filter eliminate the effects of DC light, such as direct sunlight, something that causes an unfiltered IR passive detector to become swamped.
- The H->L and L->H threshold voltages in the Schmitt trigger can be changed by adjusting the 120K and 1.1M resistors.
- The 1uF capacitor was added to eliminate voltage spikes at the H->L and L->H trasitions.

 Vout is a TTL/CMOS level signal that outputs a logical high 30 times/second when an object has gotten within 6-12 inches of the IR detector.

#### IR EMITTER CIRCUIT

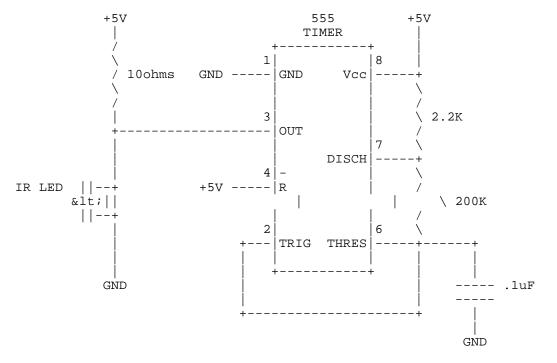


Notes:


- Adding more IR LED's will increase the range of the IR detector.
- The signal on pin 3 of the 555 is 30Hz and has a duty cycle of 50%
- Due to the very small pull-up resistor the 555 sinks about 109mA. The specs say the 555 can sink up to 225mA so it's well below the danger level.
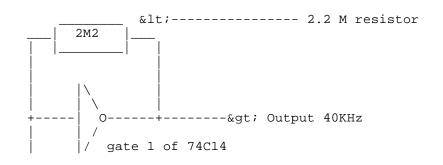
### 2. Cheap 40KHz clock

(From Sebastian Filzek)

Use a 40KHz Xtal and a 74C14 schmitt trigger:



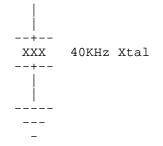

This circuit has worked for me in many applications. (it might be an idea to buffer the signal befor using it. (There are still 5 unused gates in the 'C14.. :-)

### 3. A very STABLE 40khz generator


(From Rodney Radford)

A circuit that I have used before is based on the CD4060 (14stage binary counter) and a 640Khz ceramic resonator. The CD4060 is basically an oscillator and a ripple counter to divide the 640khz down to something more usable.

Here is the pinout of the CD4060 (frequencies are assuming a 640khz input signal into pins 10/11/12 - circuit shown below):

		$+ - \setminus / - +$		
160hz	1		16	Vcc
80hz	2		15	625hz
40hz	3		14	2.5khz
10khz	4		13	125hz
20khz	5		12	$\setminus$
5khz	б	i i	11	> see sub-circuit below
40khz	7	i i	10	/
GND	8	ÍÍ	9	NC
		++		

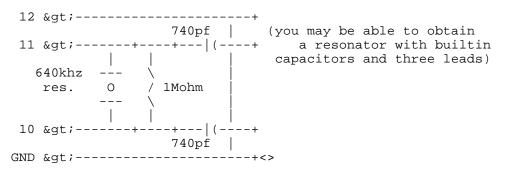Sub-circuit for a 640khz ceramic resonator:



A nice part about this circuit is that it delivers a STABLE 40khz signal, as well as delivering several other frequencies that can be used to modulate the 40khz carrier. For example, the person that designed this circuit (Ken Boone, member of Triangle Amateur Robotics) used it


to build several beacons in his yard to serve as navigation points for a robotic lawnmower. By diode-OR'ing the results of the 40khz carrier and one of the lower frequencies (such as the 125Hz) line to drive a ring of IR-LEDs, he could locate the beacon and tell which, of several, beacons he had found.

This circuit has proven to be VERY stable, and is fairly inexpensive (about \$1.50 for the CD4060 and 640Khz ceramic resonator).
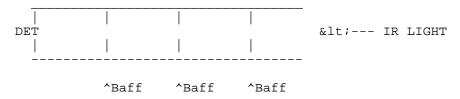
### 4. Minimizing SUN's noise in IR reception

```
(From jrm@gnv.ifas.ufl.edu)
```

A 'baffle' is a perforated disk or disks spaced inside your 'shade tube'. The idea is to trap all reflections, leaving only the light coming in on the exact axis of the tube to strike the IR Detector.



Off-axis light, 'noise', will be caught by the baffles and dissipated through reflection between the baffles. Paint the inside of your tube black ... in fact, check into what paints/coatings are 'black' to IR wavelenghts. Just because a paint **LOOKS** black does not mean it won't reflect IR.

Check into an astronomy or optics group to get the formula for the ideal spacing of the baffles and how big a hole should be in them. Getting this right will improve your system performance.

# 5. Build an Infrared night scope

```
(From -=-= Wes =-=-)
```

Building a night scope is easy if you have the heart of it which is the image intensifier part. I would recommend using the PVS-5 module which uses 'MCP' or Micro Channel Plate technology. This is a U.S. 2nd generation device and is rated at 15,000 times light gain. The resolution is one of the best on the market. It was used in Desert Storm and released to the surplus market about 2 1/2 years ago. However, it can't be exported out of the U.S. :-( The device can be found for between \$350 to \$700 depending on the quality you want in terms how new it is or if it used. I will list a couple of vendors at the end.

I have built several of these scopes with and without targeting lasers. The laser will kill your battery in no time and I recommend not using one for normal use as the PVS-5 has excellent response without it (unless you want to scare the crap out of someone in total darkness running around your yard. Just put a laser dot on his forehead and let him figure out where it came from and what is at the end of it....like a 30.30 :-) Anyway, you will need the following:

- 10" length of 1 3/4" PVC plastic pipe (thinwall)
- 6" length of 3/4" PVC pipe and end caps (thinwall)
- 1-35mm lens with shutter
- 1- eyepiece (see text)
- 1- lens mount (I use Minolta lens adaptors and lenses which I pick up at pawn shops dirt cheap)
- 1- 3/4" washer
- 1- small spring
- 1- micro pushbutton switch
- 1- 3 volt lithium battery (I use the DL123A which Radio Shaft...ahhh..Shack sells for \$7.99)
- 1- tube of silicon rubber (black)
- And of course, one PVS-5 MCP module

When you receive your module do not pull on the power wires or they will break off inside of the power supply and you now have a several hundred dollar paper weight! Do no handle the front screen if possible. If you do, wipe it clean with a optical lens cleaner. **DO NOT TWEEK THE TWO POTS IN THE POWER SUPPLY!!** These pots adjust the ABC (Automatic Brightness Control) and AGC (Automatic Gain Control). If the pots are set too high, a flashover will occur in the Micro Channel Plates and burn out one or more which means that part of the display is dead. This is noticed by a black spot on the display when the PVS-5 is turned on. With that out of the way, lets continue...

Using fine sandpaper or cheesecloth, smooth out the inside surface of the larger PVC pipe. Test fit the PVS-5 module by sliding it into the PVC pipe. It should fit snug but not tight. Continue sanding until the fit is snug. Next, remove the module and wipe down the inside of the pipe. Spray the inside flat black and let it dry. Once its dry, mount the front lens mount to the PVC pipe and mount the lens. Slide the PVS-5 into the other end and slide it to about 2">from the lens. Focus the lens to infinity and close the shutter all the way so that only a pinhole is open. Point it towards an object 10 feet or better away. Apply 3 volts to the PVS-5 and slide it back and forth until the clearest image can be seen on the display screen. Move the housing with the silicon rubber. **DO NOT GET IT ON THE DISPLAY OR THE FRONT SCREEN!** In case you are wondering why you can use the PVS-5 in normal lighting (like a shop or lab) its because of the automatic brightness function. The PVS-5 was designed to eliminate blooming problems with muzzle flash and bright light sources such as gun fire and explosions. Just don't open the shutter all the way (though it wouldn't hurt it).

After the silicon rubber is cured, we now start on the 'fun' (ugh !) part. This is time consuming (about an hour) and requires a little patience. The eyepiece that I use is a 35mm lens that is 'reversed' I.E. you look through the front of it rather than the back. The reason I do this is to eliminate the pincushion effect of the PVS-5's concave screen. But you can use anything that will magnify the image (even a 8X jeweler's eye loupe which I used on my first one with

'passable' results). Anyway, if you choose to use a 35mm lens like I did, then we have to rework the lens. First unscrew the whole body of the lens. Most will have a small screw stop that won't allow you to unscrew it completely unless the screw is removed. Once the lens is separated from the shutter and rear optic, clean the grease off of the threads. Next, try a fit test into the PVC housing. If the lens is too tight, grind the threads down until the lens fits snug, but not overly tight. Next, drill a small hole 1/2" from the rear of the PVS-5 at the top to pass the power wires through. Now, put the lens onto the PVC and press it as far in as it will go. Now apply power to the PVS-5. The image will be blurred. Here is the fun part. Remove power and the lens and using a hacksaw or bandsaw, cut 1/2" off of the PVC pipe and try it again. Continue doing this until it 'starts' to come into focus. Once it starts to come into focus, saw the PVC in 1/8" sections. Continue until the display is crystal clear. This has to be done whether you use a 35mm lens or not. Whatever you choose, the housing has to be cut to focus the eyepiece correctly. At this point, you need to remove the eyepiece, front lens mount and front lens. Cover the front and rear of the housing with paper and masking tape. Now you can spray paint the housing whatever color you choose. I do mine in flat satin black and they come out great ! Set it aside to dry. After its dry, remove the paper and masking tape. Blow out any particles. Insure that the PVS-5 is secure with silicon rubber. Touch up any scrapes of the flat black paint on the inner surface to eliminate reflections. Clean the front and back of the PVS-5 with optical lens cleaner. Re-assemble the front lens mount and front lens. Insert eyepiece. Drill two 1/16" hole about 1/2" from the rear of the housing on either side of the evepiece. Secure the evepiece with two small 2-56 screws. Apply power and insure all is well so far.

Now for the battery holder. This is what the 3/4" PVC pipe and end caps are for. Put an end cap on one end and place it on the main housing so that the front end cap is against the front lens mount. Measure back from the eyepiece about 3/4" and put a mark on the small PVC pipe. Cut the pipe on the mark and place the other end cap on the small pipe. Put the whole thing on the main housing and check the fit. If it is to close to the eyepiece, mark and cut it where it is at a suitable distance. Next, mark exactly where the wires are coming out of the housing on the bottom of the battery holder pipe and drill a small hole there so that the wires go straight into the battery holder. Next, drill a hole for the pushbutton about 1/2" from the end of the front end cap. Remove both caps and set aside for now. Measure 1 1/2" from the rear of the battery holder and place a mark here. Now saw with a hacksaw about 3/4 of the way through the battery holder to form a slot. Grind the washer so it fits flush into the slot (I.E. the round top is even with the round top of the battery holder). Next nip a small slot out of the side of the washer so that the ground wire can pass through it. Insert the washer into the slot and insure it is flush then epoxy it into place by putting a dab of epoxy **OPPOSITE** the slotted side inside of the battery holder. Next, take a small piece of insulated hookup wire and strip one end. Form a loop that will let a 4-40 screw pass through it and solder the loop. Next place a 4-40 flat head screw into the hole in the center of the washer with the head pointing towards the battery. Place the loop of the wire on the other side and secure it with a 4-40 nut. Solder the other end to one side of the pushbutton switch. Connect the positive wire from the PVS-5 to the other side of the switch. Route the ground wire from the PVS-5 through the slot in the washer and out the back of the housing. Next we make the rear battery connection by using a spring secured into the rear end cap. I used a spring from a 'D' cell battery holder and secured it into place with a 2-56 screw and nut. I also soldered the ground wire to the spring after I determined the length so that the cap would just come off and let the battery slide free. But use your ingenuity on this. Install the battery with the positive side pointing towards the front of the scope and put on the rear end cape. Press the button and viola, check for a working

scope.

Finally (whew) install the front end cap and secure the battery housing to the main housing with a bead of silicon rubber along both sides of the battery housing. Smooth the silicone down so it looks like it was made like that. Let the silicon dry. Next, paint the housing whatever color you want. Again, I used flat satin black.

DO not point your scope at the sun or other really bright light source. Even though the scope has automatic gain control, a bright IR source could burn the MCP.

One reason for using the lens adaptor was so that a telephoto lens could be used or just a standard 35mm lens. Also, the 35mm eyepiece lens makes it nice for mounting to other devices like a camera (with a 80mm extension) with the threaded lens front. I have built maybe 14 of these and they are great scopes. Far better than the Russian stuff in terms of resolution and clarity. Below is the vendors for the MCP modules:

MWK Industries 1269 W. Pomona Corona, CA 91720 1-800-356-7714 1-909-278-0563 Cost: \$395 item number NIGTU2 (ask for Martin)

Meredith Instruments P.O. Box 1724 5035 N. 55th Ave. #5 Glendale, AZ 85301 1-800-722-0392 1-602-934-9387

Have fun with it and let me know how it goes :-) (particularly if you get some foxy lady that likes nude moonbathing and you get some nice 8 x 11's :-) My e-mail is <u>wellison@kuhub.cc.ukans.edu</u>.

And if you need an IR filter for that spotlight so you can use it to 'help out' the above project, here's a little something:

(From William J. Beaty)

The large amounts of IR plastic filter sheet are no longer available, but here's a hint.

Go to a theatrical lighting supplier and buy two filter gels, one for "congo blue" and one for primary red. Overlap them and you get black. However, these dyes are transparent to IR. Lay them between thin plexi for a big filter sheet. They aren't entirely black, you can see the sun through them. for darker filtering, overlap more sheets. The standard sheet is 18" x 24" (I think) and costs \$3 to \$5.

and (From John De Armond)


Edmund Scientific sells surplus sniperscope illuminator IR filters for about \$20. This is a glass filter that can stand the heat of a large lamp.

## 6. Decoding IR Remote Controls


(From Juergen Putzger)

The origin of this posting was the question what to do with an old TV. I suggested to use the infrared remote control as an input keyboard for a microcontroller board and mentioned a piece of code I had written for the 8052 microcontroller. I was asked by some people to share my information about remote controls, so here it is:

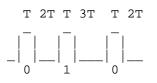
There are at least two international standards which are used by remote controls to encode the commands, the RC5 and RECS 80 code. The RECS 80 code uses pulse length modulation. Each bit to be transmitted is encoded by a high level of the duration T followed by a low level of duration 2T representing a logical '0' or 3T representing a logical '1'.



Notice that a '1' takes more time to be transmitted than a '0'. The RC 5 code instead has a uniform duration of all bits. A transition in the middle of the time interval assigned to each bit encodes the logical value. A '0' is encoded by a high to low transition and a '1' by a low to high transition. Therefore we need additional transitions at the beginning of each bit to set the proper start level if a series of equal bits is sent. We don't need this additional transition if the next bit has a different value. This is also called a 'biphase' code.

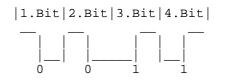


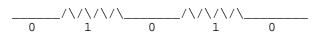Instead of being fed direct into the IR emitter, most remote controls modulate a 20-30 kHz carrier with this signal. A logic one is represented by a burst of oscillations.



The reason is, that you can use a filter tuned to the carrier frequency to distinguish the signal from noise in the ambient light. Fluorescent lamps are the main source of such noise. Photodiodes behind an optical filter which transmits infrared light but blocks visible light are used as detectors. The signal from the photodiode is fed through a filter tuned to the carrier fequency and then amplified. The amplified signal is demodulated just like the carrier is

demodulated in any AM radio receiver.

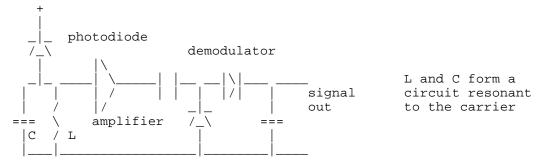

It can be a lot of pain to design a sensitive receiver that does'nt start to oscillate. It is also necessary to have some automatic gain control to avoid overload of the amplifier at close distance to the emitter. It is easier to use some integrated circuit that does all of the job. The best i have ever seen (and used) is the SFH505A manufactured by SIEMENS (no, I don't work for this company). It looks like one of this three legged voltage regulators and uses a single 5V supply. It incorporates an optical filter, the photodiode, a filter tuned to about 30 kHz, the amplifier with automatic gain control and the demodulator.

If you don't know which code your remote control is transmitting you can identify it by viewing the output of your receiver with an oscilloscope. The RECS 80 code uses high pulses of uniform length while the low pulses differ in length. If there are high and low pulses of two different lengths it might be RC5 code. Note that your receiver may invert the levels.

How are commands like volume control or channel selction encoded? In the case of the RC5 code there is an international standard. Every command is encoded by 14 bits. The first two bits S are startbits to allow the receiver to adjust the automatic gain control and to synchronize. Next a bit T follows, that toggles with every new keystroke. Next is the address A of the device which shall respond to the command. At last the command itself follows.

| S | S | T | A4 | A3 | A2 | A1 | A0 | C5 | C4 | C3 | C2 | C1 | C0 |

Some important addresses and commands:

Address:	Device:	Command:	
0	TV1	09	Numbers 09 (channel select)
1	TV2	12	Standby
5	VCR1	16	Master Volume +
6	VCR2	17	Master Volume -
17	Tuner	18	Brightness +
18	Audio Tape	19	Brightness -
20	CD Player	50	Fast rewind
		52	Fast run forward
		53	Play
		54	Stop
		55	Recording

There are integrated decoder circuits which have inputs to select the device address and parallel outputs activated by the commands. Since this is comp. robotics the devices you wish to control will have a microcontroller on board which can do all the decoding. Here is an input

routine I have written for the 8052 microcontroller family to receive RC5 codes. My cousin has written a similar routine for the RECS80 code which i will try to make available also. Perhaps we can start a collection of such routines and archive them somewhere.

; Inte ; written by d	======================================
\$MOD52	
INPUT EQU LF EQU CR EQU SPC EQU RB0 EQU RB1 EQU DSEG ORG	<pre>P3.2 ; Port3,Bit2 is used as input. The demodulated signal ; with active low level is connected to this pin OAH ; Linefeed ODH ; Carriage return 20H ; Space 000H ; Select Register Bank 0 008H ; Select Register Bank 1poke to PSW to use ; This is internal data memory 20H ; Bit adressable memory</pre>
FLAGS: DS	1
CONTROL BIT	FLAGS.0 ; toggles with every new keystroke
NEW BIT	FLAGS.1 ; Bit set when a new command has been received
COMMAND: DS SUBAD: DS BUFFER: DS STACK: DS	<pre>1 ; Received command byte 1 ; Device subaddress 30 ; Buffer to store length of transmitted pulses 1 ; Stack begins here</pre>
;	; Code begins here
;===	===================================
ORG	00H ; Reset
JMP	MAIN
ORG	0003H ; External Interrupt0
JMP	RECEIVE
;	Output routines
; DonB4	t forget to set up the serial port and Baud rate !
N_OUT: ADD C_OUT: JNB CLR MOV RET	A,#30H ;Convert BCD number to ASCII TI,\$ ;Wait until transmission completed. TI ;Clear interrupt flag. SBUF,A ;Write out character to serial port.
BIN2BCD:	;Convert 8 bit value in Acc to 3 digit BCD
MOV	B,#100
DIV	AB
CALL	N_OUT
XCH	A,B
MOV	B,#10
DIV	AB
CALL	N_OUT

	XCH CALL RET	A,B N_OUT	
; at Po ; pin i ; a thr ; indep ; extra ; the c	rt3-Bit n buffe eshold endent cted fi ontrol	2. Stores the er. Analyzes t between short of CPU speed. com the bit st bit which tog icating that a	red by the first high to low transition length of all pulses occuring at this he timing of the startbits to calculate and long pulses. This routine is The device address and command are ream. Two flags are set upon exit, gles with every new keystroke and the new command has been received.
RECEIVE:			
REC:	PUSH MOV PUSH MOV MOV	PSW PSW,#RB1 ACC R0,#BUFFER A,#0	; save current registerset
REC0:	INC	A,#0 A	; Measure duration of low-level
	NOP NOP NOP		; Delay
	NOP JZ JNB MOV INC	TIMEOUT INPUT,REC0 @R0,A R0	; End of transmission if duration exeeds 256 counts
REC1:	MOV INC	A,#0 A	; Measure duration of high-level
	NOP NOP NOP NOP		; Delay
TEMPOLITY -	JZ JB MOV INC JMP	TIMEOUT INPUT,REC1 @R0,A R0 REC	; End of transmission
TIMEOUT:	MOV INC ADD	A,BUFFER RO A,BUFFER+1	; calculate threshold between short and long pulses ; length of first low-pulse ; plus length of first high-pulse
	CLR RRC MOV CLR	C A R1,A C	; divided by two
	RRC ADD	A A,R1	; plus half of the time
	MOV	R5,A	; yields threshold
DECODE:	MOV MOV MOV INC CLR	R0,#BUFFER R1,#1 R2,#13 A,@R0 R0 C	; initial value ; Number of bits to decode
	SUBB	A,R5	; compare length with threshold
	MOV CPL RLC	A,#0 C A	; short=1
	JNZ INC	NOSKIP RO	; if short skip over next pulse

bit

NOSKIP:	XRL	A,R1	; new bit is calculated by XOR with previous
	MOV	R1,A	; Store new bit
	RRC	А	
	MOV	A,R3	; Store new Bit in R3/R4 by rotating
	RLC	A	
	MOV	R3,A	
	MOV RLC	A,R4 A	
	MOV	A R4,A	
	DJNZ	R1, A R2, DECODE	
	MOV	A,R3	
	ANL		; extract command from R3
	MOV	COMMAND, A	
	MOV	A,R3	
	RLC	A	; do some rotating to extract
	XCH	A,R4	
	RLC	A A D4	;device address
	XCH RLC	A,R4 A	
	XCH	A A,R4	
	RLC	A	
	CLR	CONTROL	
	JNB	ACC.5,TZ	; Check control bit
	SETB	CONTROL	
TZ:	ANL		; mask device address
	MOV	SUBAD, A	
	POP POP	ACC PSW	; Restore old registerset
	SETB	NEW	; Set flag to indicate the new command
	RETI	IND W	, bet itag to matcate the new command
; code ; progr ; has b ; are p ; When	to init am does been rec printed a stand	ialize the ser n't do that for eeived. Then th separated by s aby command (12	ution starts here. Don't forget to add ial port and Baud rate if your monitor r you. The Main loop waits until a command e control bit, subaddress and command byte paces. Leading zeroes are not suppressed. ) has been received, the main loop is returns to the monitor.
MAIN:	MOV	TCON, #00H	; MAKE SURE TIMERS ARE SHUT DOWN.
	MOV	PSW, #RBO	; Select register bank 0
	MOV SETB	SP,STACK EXO	; Enable external Interrupt0
	CLR	ITO	; triggered by a high to low transition
	SETB	EA	
	CLR	NEW	
LOOP:	JNB	NEW,LOOP	; Wait until a command has been received
	MOV	A,#CR	
	CALL	C_OUT	; Ouput carriage return and linefeed
	MOV CALL	A,#LF C_OUT	
	MOV	A, FLAGS	
	ANL	A,#00000001B	
	CALL	BIN2BCD	; Output control Bit
	MOV	A,#SPC	
	CALL	C_OUT	
	MOV	A, SUBAD	
	CALL MOV	BIN2BCD A,#SPC	; Output subaddress
	CALL	C_OUT	


MOV CALL MOV CLR	A, COMMAND BIN2BCD A, COMMAND C	; Output command
SUBB	С А,#0СН	; compare for standby command
CLR	NEW	, compare for scanasy command
JNZ	LOOP	; go on receiving
CLR	EX0	; stop receiving
CLR	EA	; and
JMP	8000H	; return to monitor which has its entry point at 8000H
END		

Also see http://www.awi-bremerhaven.de/~cdodge/PCIR/
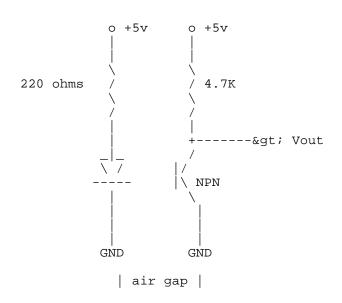
### 7. IR 'slotted switch' sensor

(From Paul Hitchcock)

There is a type of detector known as a "slotted switch" that consists of a phototransistor/LED pair mounted on a solid frame with a small air gap between the two elements. A typical circuit might be:



When the air gap is unobstructed, the transistor saturates, pulling Vout to ground; when the gap is blocked, the transistor cuts off and Vout is +5 volts.

Please see document for document author. [Feedback Form] | [mailto]. The most recent version is available on the WWW server <u>http://www.repairfag.org/ [Copyright] [Disclaimer]</u>