


# Circuit provides visual verification of IR pulses

Michael J Gambuzza, General Electric Measurement and Control Solutions, Billerica, MA


 You can test an IR (infrared) link with a circuit that converts an IR-generated photocurrent to an amplified current that drives a standard LED. This approach provides a visual feedback to indicate that the transmitter is working. The circuit can be enclosed in a small plastic or metal box and requires just a 9V transistor battery for operation. Diode  $D_1$  is a basic Everlight (www.everlight.com) PD333-3C/H0/L2 or equivalent IR photodiode in a T1¼ package.

You can configure amplifier  $IC_{1A}$  as a photovoltaic amplifier. When the IR-light energy impinges on photodiode  $D_1$ , it generates a small photocurrent that tries to pull the inverting input negative. Meanwhile, the output of  $IC_{1A}$  goes positive, maintaining the virtual-ground node on Pin 2 of the amplifier at 0V. The transfer function for the circuit is  $V_{OUT} = I \times R_1$ . If you set the gain high,  $IC_{1A}$  goes to the power-supply rail when the circuit detects light. Analog Devices' (www.analog.com) AD823AR JFET-input amplifier directly drives the LED through a 750Ω current-limiting resistor.  $C_1$  compensates the amplifier, preventing it from oscillating due to capacitive load from  $D_1$  and the input parasitic capacitance.

If the output of  $IC_1$  oscillates, you may need to increase the value of  $C_1$ .

You can determine the value of  $C_1$  by using the following equation for a 45° phase margin:  $C_1 = \sqrt{(C_D / 2\pi R_1 F_C)}$ , where  $F_C$  is the unity-gain-crossover frequency of  $IC_{1A}$ —typically, 16 MHz for the AD823—and  $C_D$  is  $D_1$ 's 0V junction

capacitance, including any parasitic capacitance on that node. Adjust  $R_1$  for optimum gain. For testing, the remote-control transmitter window should be as close as possible to photodiode  $D_1$  for maximum signal transfer. **EDN**

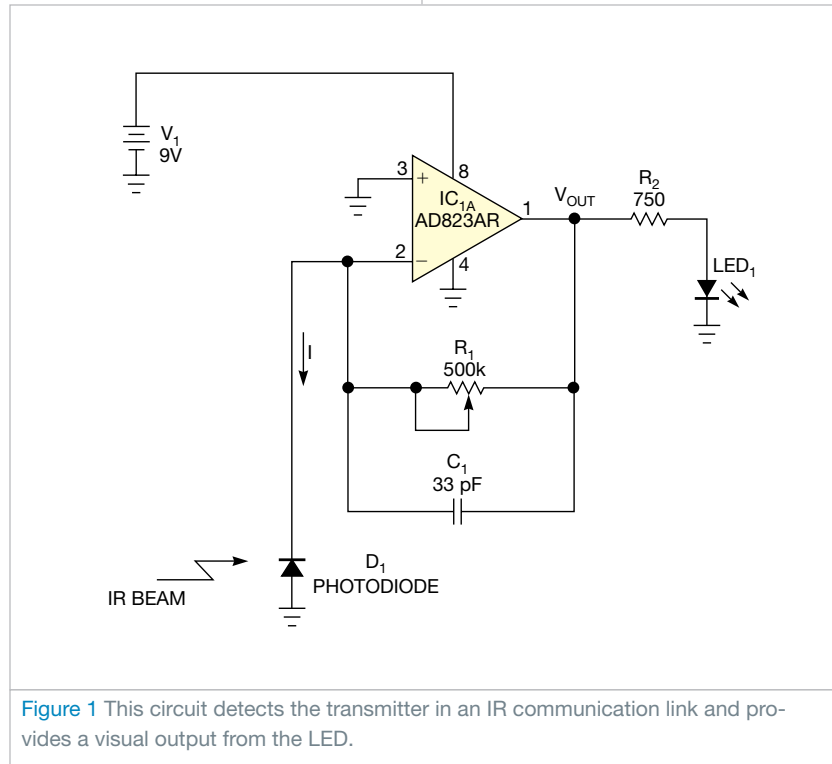

**Figure 1** This circuit detects the transmitter in an IR communication link and provides a visual output from the LED.