



Three coupled astables

This circuit produces three symmetrical square waves at 120° to each other. By inverting these, outputs at 60° can be produced. Three comparators from the MC3302P are used, and the device can

be operated from 4 to 12 volts. With the component values shown, output frequency is approximately 17Hz.

L. J. Bell,
Evesham,
Worcs.