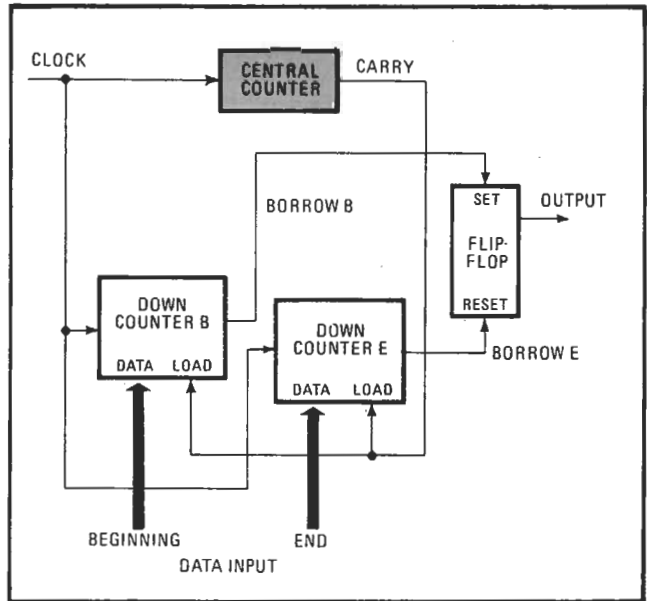


Digital pulser provides programmed width, position


by Marian Stofka
Bratislava, Czechoslovakia

The job of testing a digital circuit design often requires a pulse generator whose start and stop times are controlled by a precise and programmable amount. With a central counter and two programmable down counters, this design (Fig. 1) accomplishes this task and has a resolution that is a function of the counters' capacity. Two digital words at data input port determine the turn-on and -off times of the output pulse.


Whenever the central counter reaches an overflow state, a carry pulse is generated at its output. At this point, the two down counters B and E are programmed with the input data, which carries the information concerning the output pulse. When counter B reaches the value of zero, a pulse generated at its borrow output sets the flip-flop, thus initiating the start of the output pulse. Similarly, when counter E reaches zero, a borrow pulse at its output resets the flip-flop, thereby giving the desired width of the output pulse.



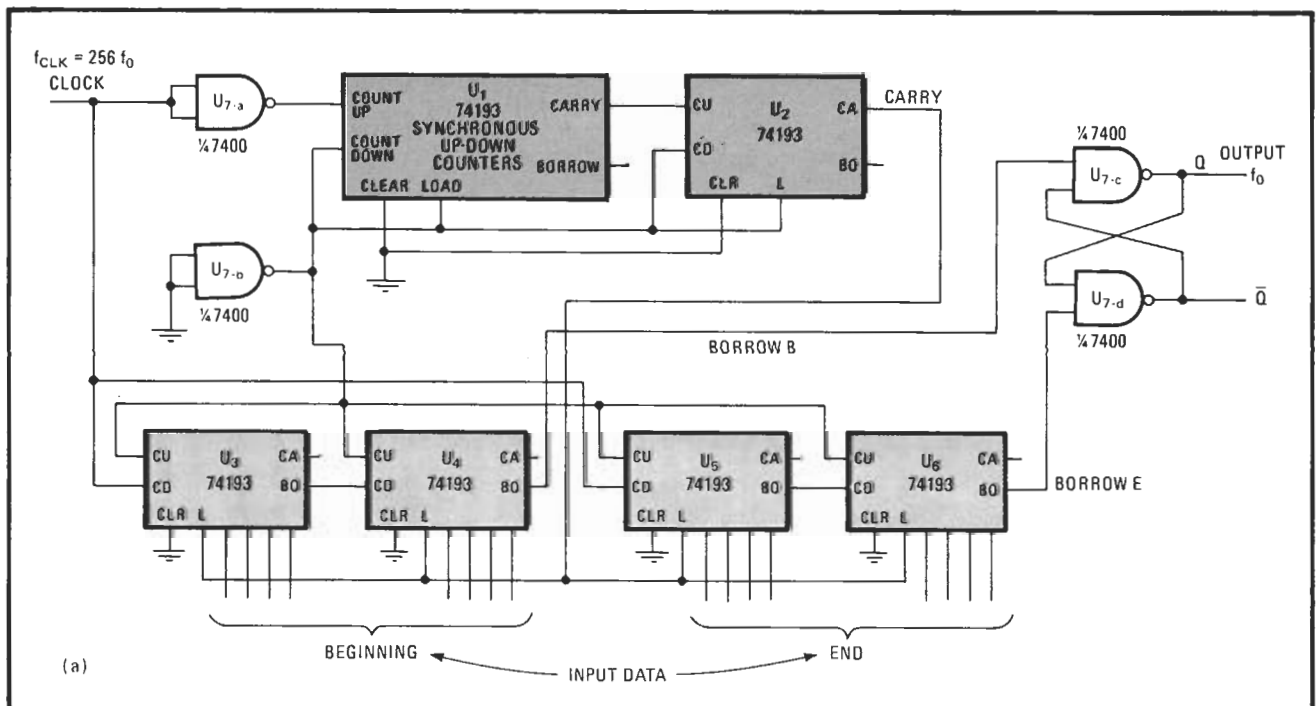1. Selectable edges. This pulse generator produces a pulse having a defined width and position within a given period and with a resolution given by the capacity of the counters. Two digital words serving as a data input determine the start and stop times of the output pulse. The borrow pulse generated by counter B sets the output flip-flop, while the borrow E pulse resets it.



(a)

 

(b)

2. Hardware. The fundamental pulser is realized by incorporating six 4-bit programmable counters U_1 - U_6 and a NAND gate chip U_7 (a). The 256 selectable start and stop edges of the output pulse are programmed by the two 8-bit words functioning as data input. Counters U_1 - U_2 function as the central counter, while U_3 - U_6 simulate down counters B and E. The various pulses generated by the circuit are shown in (b).

The counters employed may be binary or binary-coded decimal. For the binary counters used in this setup, the start and stop times can be resolved to within $2\pi/16^k$ radians, where k is the number of 4-bit chip counters cascaded within the fundamental down counter.

The hardware realization (Fig. 2a) uses two 4-bit

programmable counter chips to form the basic down counter and has a resolution of one part in 256. Two 8-bit words form the input data that program the output pulse's 256 edge positions. The timing diagram (Fig. 2b) illustrates the relationship between the clock, input data, and output pulse. \square
