

YOU Can Build This VLF to HF Loop Receiving Antenna

Part 3 of 3.

Linearizing a nonlinear world: We would like the loop's tuned frequency to linearly track the coarse tuning control. If the loop tunes from 2.00 to 7.00 MHz, we would like the same number of degrees of revolution of the tuning knob to cover 2.00-3.00 MHz as it takes to cover 6.00-7.00 MHz.

If we were using a mechanical variable capacitor, we would use one with plates cut for "straight line frequency." A varactor equivalent of these ingeniously shaped capacitor plates, unfortunately, isn't available. So, how do we approximate straight-line frequency tuning with potentiometer and a varactor diode?

The resonant frequency of an LC tuned circuit is given by:

$$f = \frac{1}{2\pi\sqrt{LC}} \quad [4]$$

where:

f is the frequency in Hertz
L is the inductance in henrys
C is the capacitance in farads

In the loop tuner, C consists of the capacitance of varactor diodes D1-D4, the turn-to-turn distributed capacitance of the loop windings, and strays. (We'll call both of these last two items together C_{stray}).

Equation 5 provides a good fit for the capacitance versus voltage relationship for the MVAM-109 diodes that I used over the range 0.5 volts through 10 volts:

$$C = 8.5 + 447.6e^{\frac{v-v_0}{k}} \quad [5]$$

where:

C is capacitance in pF

$v_0 = 1.24$

$k = 2.698$

v is the applied voltage, in volts

If we assume that L is in μH , C is in pF, and f is in MHz, and then substitute Equation [5] into [4], we get [6], the tuning frequency f in MHz as a function of tuning voltage v.

$$f_{\text{MHz}} = \frac{159.16}{\sqrt{L(C_{\text{stray}} + 8.5 + 447.6e^{\frac{v-v_0}{k}})}}$$

At first glance, equation [6] doesn't look particularly linear. However, it turns out that it isn't too far away from a straight-line relationship, as can be seen in the error plot.

To see if the linearity could be improved, I modeled the behavior of the circuit using an Excel® spreadsheet and experimented with various values of resistance between the wiper on R11 to +12 V or to ground, based upon the 3-turn air loop of 9.3 μH inductance. An excellent tutorial on using resistors to customize pot responses can be found at R.G. Keen's Web page "The Secret Life of Pots," [http://www.

geofex.com/Article_Folders/potsecrets/potsecret.htm].

A single 3.3k ohm resistor to ground from R11's wiper reduced the tuning error significantly.

Parts availability

A few of the parts may prove difficult to find:

- Varactor diodes D1-D4. I used Motorola MVAM-109 diodes, now unfortunately obsolete. The NTE-618 is a substitute and is carried by major parts houses such as Mouser Electronics, 1000 North Main Street Mansfield, TX 76063; 1-800-346-6873; [http://www.mouser.com]; part number 526-NTE618.

- BN 43-202 binocular core and FR-7 1/2-61 ferrite rod. I found these at Ocean State Electronics, 6 Industrial Drive, P.O. Box 1458, Westerly RI 02891; 401-596-3080; (fax) 401-596-3590; [http://www.oselectronics.com].

- Surplus loopstick. Ocean State Electronics lists an inexpensive 3-1/2-inch, 1/2-inch-diameter loopstick, part number LA-540. I purchased several of these some months ago and measured the inductance as 1140 μH with the supplied coil of approximately 105

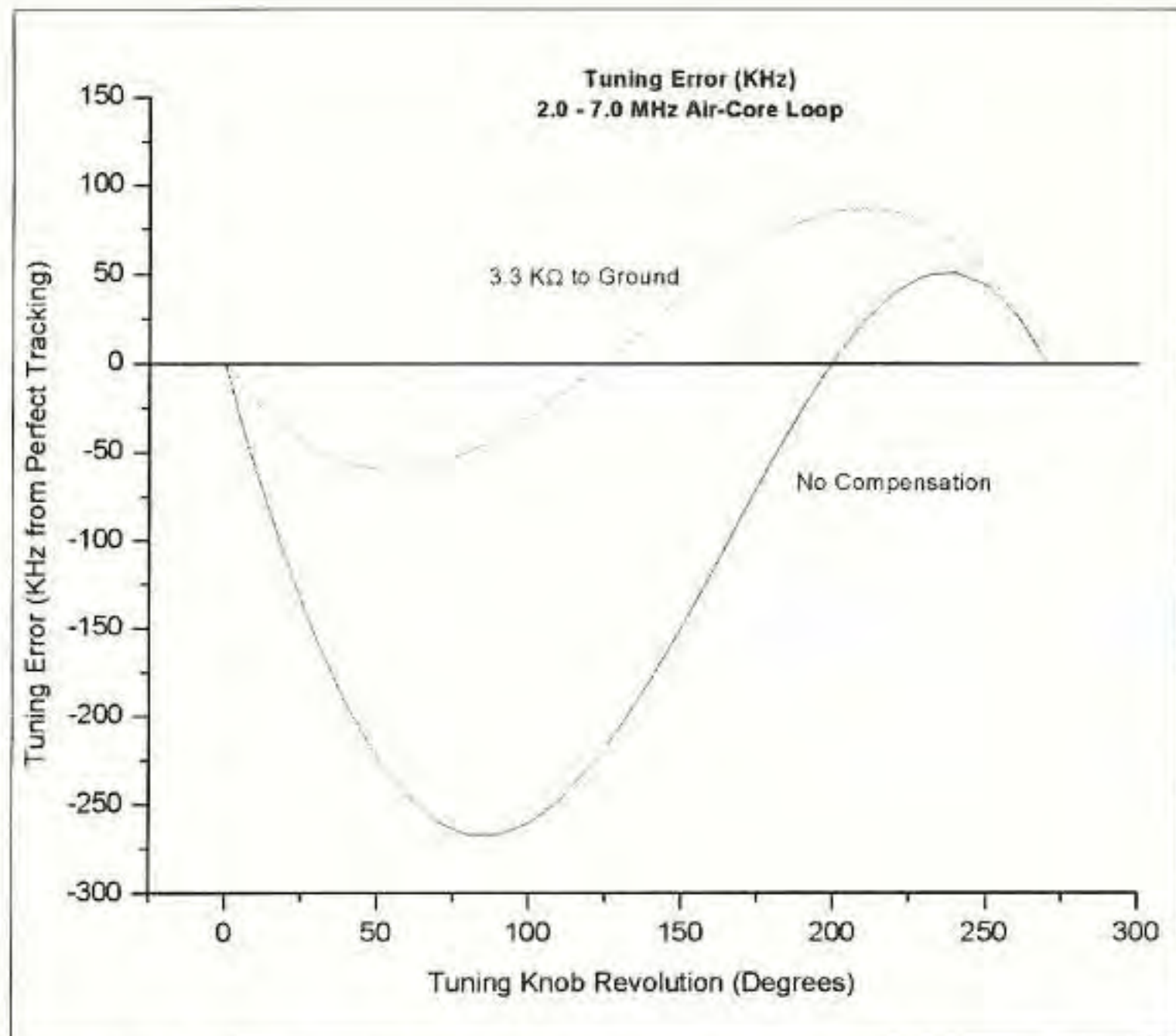


Fig. 10. Tuning error with and without compensation resistor.

turns. The approximate tuning range with the tuner is then 97 kHz to 765 kHz, using low and high modes. It would be possible, of course, to remove sufficient turns to move up resonance. (The LA-540 loopstick is not the one referred to in the text.)

- Q-Dope. Ocean State Electronics carries this product.

- Relay K1 is an Omron model G5V-2-H1 with a 12-volt coil. This relay plugs into a 14-pin DIP socket and has contacts optimized for switching low-level signals. Mouser's part number is 653-G5V-2-H1-DC12. Most major supply houses carry Omron relays.

- Printed circuit board. A printed circuit board is available for this project from Far Circuits, 18N640 Field Court, Dundee IL 60118; voice/fax 847-836-9148; [http://www.cl.ais.net/farcir/].

References

Antenna Engineering Handbook, 2nd Edition, Richard C. Johnson & Henry Jasik, eds., McGraw Hill, New York NY, 1984.

Antennas, 2nd Edition, John D. Kraus, McGraw Hill, New York NY, 1988.

The ARRL Antenna Book, R. Dean Straw, ed., American Radio Relay League, Newington CT, 1994.

Ferromagnetic Core Design & Application Handbook, M.F. "Doug"

DeMaw, MFJ Publishing Co., Inc., Starkville MS, 1996.

Joe Carr's Loop Antenna Handbook, Joseph J. Carr, Universal Radio Research, Reynoldsburg OH, 1999.

TRANSMITTER LOCATION

New fixed site direction finders provide 2 degree accuracy, and include software for triangulation from a central control site. Mobile versions also available covering 50MHz to 1 GHz

Doppler Systems Inc.

PO Box 2780 Carefree, AZ 85377
Tel: (480) 488-9755 Fax: (480) 488-1295
www.dopsys.com

European Marketing Director Denis Egan
PO Box 2, Seaton, Devon EX12 2YS England
Tel & Fax: 44 1297 62 56 90



A GREAT gift idea for yourself, your ham friend(s), or your child's school library

is a subscription to 73 Magazine ... only \$24.97!
Call 800-274-7373 or write to 70 Hancock Rd., Peterborough NH 03458

Reprints
of
73 Magazine articles
Only \$3.00 Each!
Call 800-274-7373

Back Issues
of
73 Magazine
Only \$5.00 Each!
Call 800-274-7373

Amplifiers, ATU Down Converters & Hard to Find Parts

LINEAR AMPLIFIERS

HF Amplifiers
PC board and complete parts list for HF amplifiers described in the Motorola Application Notes and Engineering Bulletins:

AN779H (20W)	AN 758 (300W)
AN779L (20W)	AR313 (300W)
AN 762 (140W)	EB27A (300W)
EB63 (140W)	EB104 (600W)
AR305 (300W)	AR347 (1000W)

2 Meter Amplifiers
(144-148 MHz)
(Kit or Wired and Tested)

35W - Model 335A,	\$79.95/\$109.95
75W - Model 875A,	\$119.95/\$159.95

HARD TO FIND PARTS

- RF Power Transistors
- Broadband HF Transformers
- Chip Caps - Kemet/ATC
- Metalclad Mica Caps - Unelco/Semco
- ARCO/SPRAGUE Trimmer Capacitors

We can get you virtually any RF transistor!
Call us for "strange" hard to find parts!
DIGITAL FREQUENCY READOUT
For older analog transceivers
TK-1 (Wired and Tested) \$149.95

ATU Down Converters

(Kit or Wired and Tested)

Model ATV-3 (420-450)	(Ga AS - FET) \$49.95/\$69.95
Model ATV-4 (902-926)	(GaAS - FET) \$59.95/\$79.95

For detailed information and prices call or write for our free catalog!

Phone
(937) 426-8600
FAX
(937) 429-3811

CCI Communication Concepts Inc.

508 Millstone Drive • Beavercreek, Ohio 45434-5840
e-mail: cci.dayton@pobox.com
www.communication-concepts.com

ADDITIONAL ITEMS

Heat Sink Material
Model 99 Heat Sink (6.5" x 12" x 1.6"), \$24
CHS-8 Copper Spreader (8" x 6" x 3/8"), \$24
Low Pass Filters (up to 300W)
for harmonics \$12.95
Specify 10M, 15M, 20M, 40M, 80M or 160M
HF Splitters and Combiners up to 2KW