

The Dual-Combo Field-Strength and Source Dip Meter

Versatile test instruments for all your RF projects.

by Martin Beck WB0ESV

Most field-strength meters described in ham literature are coil-capacitor tanks with a diode and a meter. These FSMs are useful, but not sensitive enough for many jobs where the RF is not very strong. I frequently need something better, so I designed the device described here.

The most notable feature of this FSM is that instead of a DC amplifier, it uses an RF amplifier: a grounded-gate FET. After RF amplification, the signal is capacitively coupled to a diode voltage doubler whose output is fed to a 200 μ A meter. For those who want the ultimate in sensitivity, a simple bipolar DC amplifier can follow the diode doubler.

More than 20 years ago I used such a system, but it was all bipolar. I took it to the annual Field Day operation of the W6LIE radio club. During a break in operation, I noted that my FSM's meter was reading up and down, but no local signal was being generated. I determined that the FSM was reading 15 meter *received* energy being re-radiated from a 15 meter yagi at about 40 or 50 feet up!

Construction Details

The device shown in Figure 1 uses three "tricks." First, the FSM uses the same plug-in coils as the source dipper described later in this article. Second, the dipper uses the FSM's meter. Third, switch S1 not only switches the meter from the FSM to the dipper, but also turns on the power for the FSM's FET when in the FSM meter position. The FSM uses two extra plug-in hairpin loop coils to extend its range a little bit.

Note that in Figure 1 the 365 pF air variable capacitor C1 is not shown. This was for the sake of clarity. C1 is on the opposite side of the board. Two bolts hold it to the board. Any broadcast capacitor will do (from a "junkie" AM radio, for example)—just use one section. It does not have to be bolted to the board, but a short heavy lead should be run from its frame to the board. A thin brass strip $\frac{1}{4}$ -inch or wider is good for this. You can often drill and tap a couple of holes for mounting it to the board.

Note that in Figure 1, J2, J3, J4, and J5, as

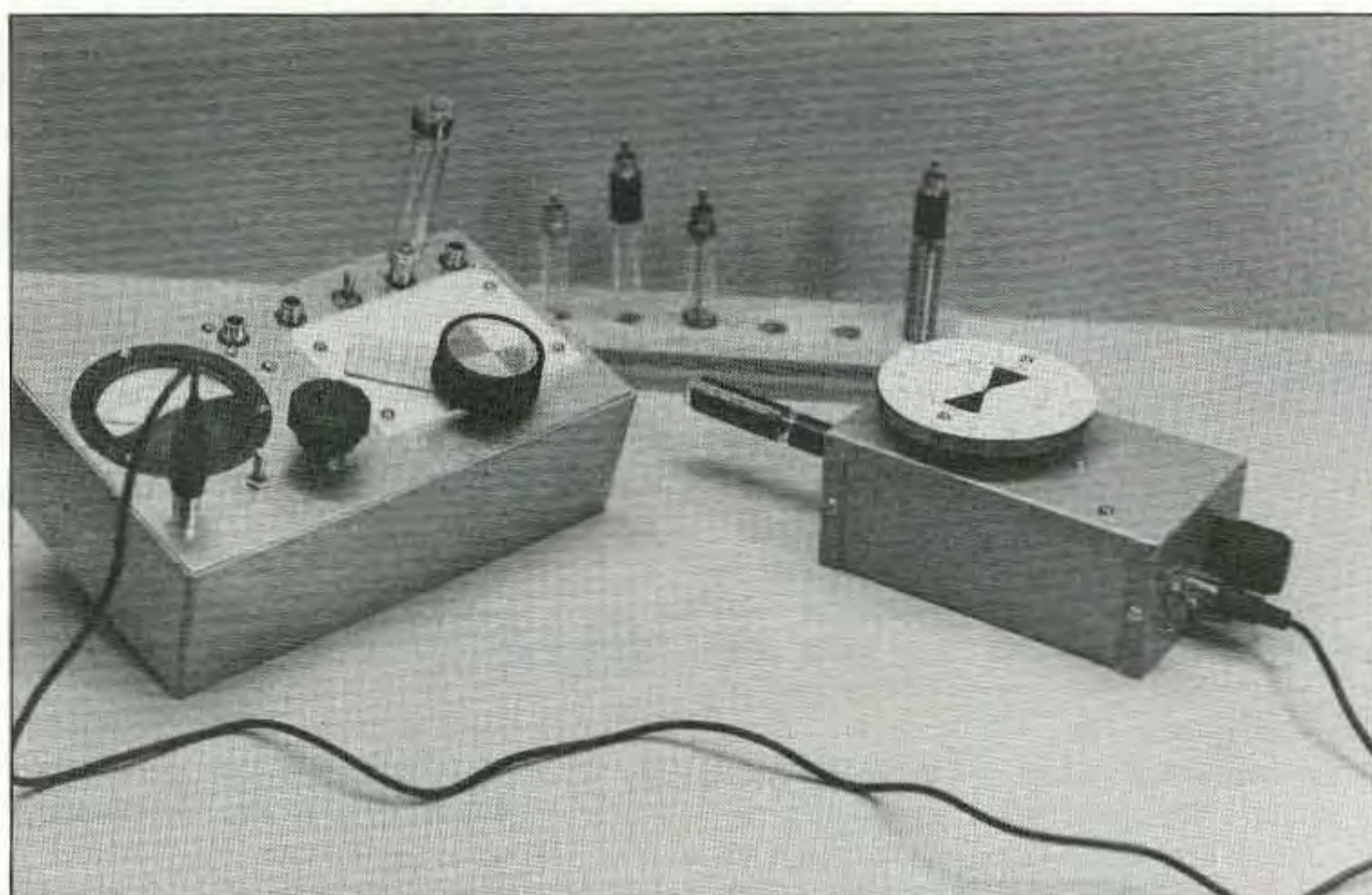


Photo A. The field-strength meter (left) and the source dip meter (right).

well as S2, are mounted on a plastic strip. This is because these phono jacks must have both "sides" (i.e., both sheath and center pin) above ground. The plastic strip is bolted to the inside of the metal face plate and 0.375-inch holes are punched in the face plate to completely clear the phono jacks. The switch just went along for the ride, as it could have been mounted on the metal face plate.

Except for the meter, C1, and the RF choke, I bought all the parts at Radio Shack. The RF choke came out of an AM radio. Anything from 1 to 2.5 mH will do. The chassis box is known to Radio Shack as a "project box," and is about $7\frac{1}{2}$ " L x $4\frac{1}{4}$ " W x 2.375" deep. A metal chassis box could also be used. The entire FSM is built on the metal face plate. Simply turn the plate upside down on the box and you will have a convenient holder while you do the work.

For a dial, I used a piece of typing paper held down by a piece of thin, clear plastic. Since the FSM uses the source dipper's plug-in coils, you need an RF source for calibrating the dial. Some signal generators will

work. Other options are the use of a friend's dipper or, if you want only the amateur bands, transmit into a dummy load and hold the field-strength meter nearby. As a last resort, you can wind a second set of plug-in coils for the FSM and calibrate it with the source dipper.

Since both the source dipper and the FSM use the same meter, I opted for a 200 μ A job. You can use a Radio Shack 50 μ A meter (now discontinued), but it is so highly damped that its response is too slow to suit me when using it with the dipper. It does work, but a less highly damped 200 μ A meter is better.

Note that most of the circuit is built using phenolic terminal strips. A printed circuit could be equally good.

In Figure 1 you can see that there are both a low band (J2 coil and J3 antenna) and a high band (J5 coil and J4 antenna). Since brass strips are used in conjunction with J4-J5, the inductance is lower, and the FSM's range can be extended. Only the two hairpin loops are used in the high band section. Either antenna can be a two-to-three-foot "spike."

"b" mark the beginning and end of the coil itself. Hole "a" is drilled about a 1/4 inch from the top end of the coil form in each case. See the chart in Figure 5 for the dimensions for each coil.

Next, mount an RCA phono plug in the end of each form. Use only the Radio Shack plug (RS# 274-339) with the metal shield. Remove the shield and toss it. Next, dab some epoxy on the threads of the plug and place it securely into the end of the coil form with the ground lug sticking through the hole in the side of the form as shown in Figure 5.

After the epoxy has set up, you're ready to wind the coils according to the chart in Figure 5. First, route the wire down the center of the coil form, through the center conductor of the phono plug, and solder it in place. Figure 6 shows the winding procedure. The last turn passes through the holes marked "b" and pulled down to point "c" and soldered in place on the phono plug's shield lug. Be sure to cut off the excess grounding lug. Being careful not to short the lug to the center pin, push the lug in a bit until it is about flush with the outside of the tube. It can be pried in and out several times without breaking. Once the coil winding is adjusted to the range you want, you can slip some heat-shrink tubing over the lower (plug) end, or for that matter, over the entire coil. Once the wire is fed through holes B-B, pulled tight and bent down to the plug's ground lug, the coil will not unravel. The dipper coils are all close-wound. You should use the #28 enameled wire for the lowest band's coil, but you can substitute #22 enameled wire for the #21 I

Field Strength Meter Parts List

Q1	MPF102 FET (RS# 276-2062)
D1,D2	1N914 diode
S1,S2	SPDT switches
R1	10k panel mount potentiometer
R2	270 ohm resistor
J1-J5	RCA phono jacks (RS# 274-346)
RFC	1 to 2.5 mH RF choke (Antique Electronic Supply #PC-1535B)
TB1,TB2,TB3	2-terminal strips
TB4	4-terminal strip
BT1	9-volt battery
L1	4 turns #20 bare wire with center tap (3/8" diameter by 1/2" length)
L2	1/4" wide brass strips mounted as shown in Figure 1
M1	200 µA panel meter
C1	365 pF variable capacitor (from AM broadcast radio or Antique Electronics Supply #CV-230)
C2	0.001 disc ceramic capacitor
C3,C4,C5	0.01 disc ceramic capacitor
Misc.	Case, mounting hardware, a 7/8" W x 4 7/8" L Acrylite support plate (1/8" thick) and a 2" W x 4" L piece of single-sided PC board material for mounting components

Source Dip Meter Parts List

Q1	MPF102 FET (RS# 276-2062)
RFC	2.5 mH RF choke (Antique Electronic Supply #PC-1535B)
C1	Dual section 150 pF variable capacitor (Antique Electronic Supply #CV-900 or #CV-240)
C2,C3	100 pF ceramic disc capacitor
C4	0.01 µF ceramic disc capacitor
4	insulated standoffs
J1,J2	RCA phono jacks, RS# 274-346
R1	100k resistor
R2	10k potentiometer
R3	150 ohm resistor
S1	SPST switch
BT1	9-volt battery with clip
6	RCA phono plugs (for coils), RS# 274-339
Misc.	Battery clip, PC board material for mounting components (1 3/4" W x 3 1/2" L), small plastic block (1.5" x 1.5") to support J2. 1/2 inch diameter Acrylite tubing for the coil forms. Lengths of #28, #22 and #20 wire for the coils.
Source:	C1 and the RF choke for both the Field Strength Meter and the Source Dip Meter are available from Antique Electronic Supply, 6221 S. Maple Ave., Tempe AZ 85283. Phone (602) 820-5411.

Measure Up With Coaxial Dynamics Model 83000A RF Peak Reading Wattmeter

Take a PEAK with Coaxial Dynamics "NEW" Model 83000A, designed to measure both FWD/RFL power in CW and FM systems simply and quickly. Then with a "FLIP" of a switch, measure "PEAK POWER" in most AM, SSB or pulse systems. Our Model 83000A features a complete selection of plug-in-elements plus a 2 year warranty. This makes the Model 83000A an investment worth looking at. So go ahead, take a "PEAK", you'll like "WATT" you see!

Contact us for your nearest authorized Coaxial Dynamics representative or distributor in our world-wide sales network.



**COAXIAL
DYNAMICS,
INC.**

15210 Industrial Parkway
Cleveland, Ohio 44135
216-267-2233
1-800-COAXIAL
Fax: 216-267-3142

Service and Dependability . . . a Part of Every Product



used (because I had it). Note that, except for the lowest band coil, a few extra turns should be used as it is easier to remove than add turns when adjusting frequency. Be sure that when the coils are finished, there is overlap of the ranges. For example, the lowest frequency of coil C should be lower than the highest frequency of coil B. I always try to keep all of an amateur band on one range, to avoid having to plug and unplug coils.

My dipper is stable, easy to use, and gets more use than my old 110V Millen dipper. The source dipper has its own "power supply" and can go anywhere. Once you have one, you will wonder how you ever got along without it.

One note: Make sure you use the proper size of Acrylite tubing (1/2" o.d.) that will mate with the phono plugs. For the location of an Acrylite distributor, you can call Cyro Industries at (800) 223-2976.

If you can't find a source of the tubing, I can supply a full set of pre-cut and drilled coil forms with phono plugs permanently installed (send to address at end of article). These forms are suitable for many other purposes than these two projects. The package includes a pre-cut and drilled acrylite plate with the coil's jack permanently installed. The set is \$39.95, including postage. If you can do your own drilling and epoxying-in of the phono plugs, the set of coil form parts is \$29.95, including postage.

Contact Martin Beck WB0ESV at 1637 Hood, Wichita KS 67203.