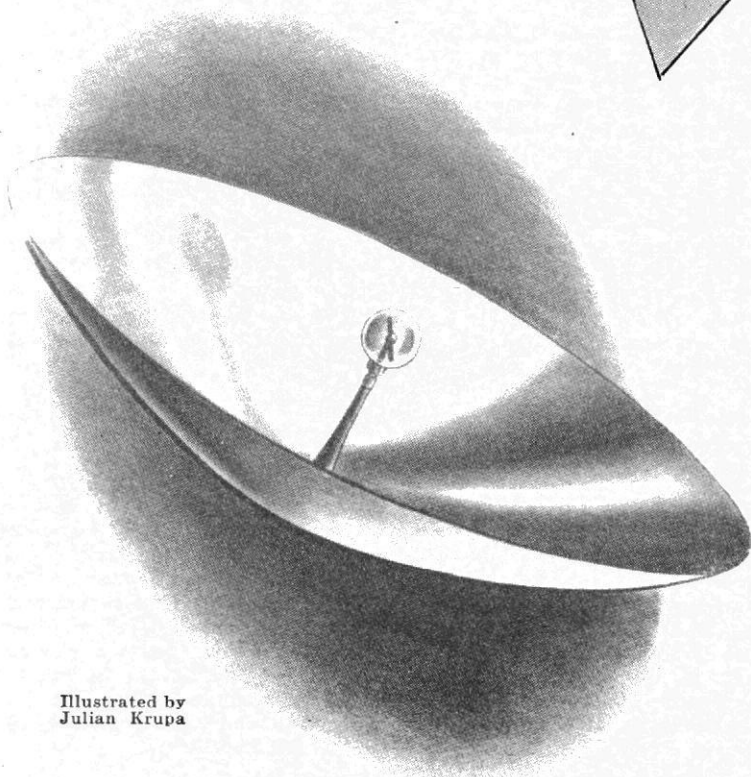


# Practical


# RADAR



Illustrated by  
Julian Krupa

By **JORDAN McQUAY**

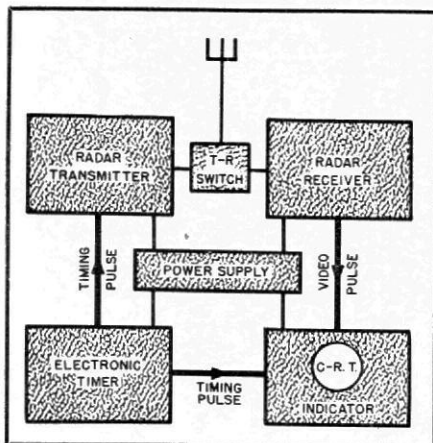**Part 5. The design of radar receivers capable of detecting weak echo signals. Conventional u.h.f. tubes, circuits, and design techniques are used throughout.**



A CONSTANT barrage of r.f. pulses from a radar set scans the air and land and sea, searching for targets in light or darkness, in any kind of weather.

The pulses travel at the speed of light until they strike a target, when the r.f. energy is reflected or reradiated at equal speed in all directions from the surface of the target. Some of this reflected energy returns to the radar set in the form of *echoes* which are picked up by the radar receiving antenna.

The receiver takes every weak echo from the antenna, amplifies it, detects the echo envelope, and then feeds the

Fig. 1. Basic block diagram of a radar set.

rectified signal to the indicator unit of the radar set.

Once the echo signals are received from targets, determination of the ranges and directions of the targets are based on the facts that radio-frequency energy travels at a constant velocity (about 186,000 miles-per-second) and that the antenna set of a radar set is movable and highly directional.

The range or distance to a target can be found by multiplying the velocity by one-half the time a single pulse requires to complete a round-trip cycle, known as a radar cycle. This *time* is measured electronically by the cathode-ray oscilloscope and immediately translated in terms of *distance*—in yards or miles.

The physical position of the antenna system then gives us two angular measurements, the azimuth or bearing, and the elevation angle of the target.

Knowing the range or distance, azimuth, and angle of elevation, we can locate accurately the position of any object in space or on land or water.

The reception and detection of echoes from distant targets is an important job in the over-all function of a complete radar set (Fig. 1).

Because reflections from any target are scattered at random in all directions, the few echoes that return to the radar set are very weak. Yet these signals must be accepted by the receiver and amplified sufficiently so they can be observed as visual signals on the time base of a cathode-ray oscilloscope.

This ability of the receiver to detect and amplify extremely weak echo signals is a measure of the effectiveness of the radar equipment; the weaker the acceptable echo signal, the greater the workable range of the radar set.

Radar receivers employing, for the most part, conventional types of u.h.f. tubes and circuits require a fairly wide bandwidth input, at the same operating frequency as the radar transmitter. Except in this one respect, the radar receiver needn't differ greatly from other u.h.f. receivers. Therefore, much of the published and known theory of u.h.f. receiver operation is applicable to radar receivers.

### The Superheterodyne

A radar receiver must supply considerable amplification, with inherent stability and extreme sensitivity. For this purpose a superheterodyne circuit logically offers itself.

Special types of high-frequency tubes with low interelectrode capacitances are used in the r.f., local oscillator, and i.f. stages. And a large number of i.f. amplification stages may be expected in a radar receiver. These and other u.h.f. refinements give stability of operation at ultra-high frequencies, as well as a high degree of sensitivity. Even when the receiver employs as many as six or eight stages of i.f. amplification, there is considerable stabilization.

The block diagram of a basic su-

perheterodyne receiver suitable for radar is shown in Fig 2.

It functions much in the conventional manner, with some important exceptions. The input to the receiver is broadly tuned with provisions for changing the input bandwidth; the intermediate frequency is measured in megacycles and the output of the receiver is a video signal containing a wide range of component frequencies.

A number of other circuit conditions must be considered in addition, if the radar receiver operates at ultra-high frequencies. High amplification by any one r.f. stage is seldom possible and there are considerable losses in the process of conversion to an intermediate frequency. The shortness of interconnecting leads becomes important. Interlocking of amplifier and local oscillator tuning becomes more difficult to avoid. All r.f. and i.f. circuit elements must be well shielded. Tuned sections of transmission lines are often used as "tank" circuits, and special types of u.h.f. tubes must be used in the r.f., local oscillator, and i.f. stages of the receiver.

In general, as the frequency of operation is increased, the physical structure and electrical design of radar superheterodyne circuits becomes more radically altered.

All of this is necessary to preserve the shape of the reflected echoes, while they are being detected and amplified.

It's a big job for the radar receiver. Often the simple diagram (Fig. 2) may become quite complicated, as shown in Fig. 4, where as many as 20 or 25 separate and distinct stages compose the complete receiver.

But regardless of the total number of stages in a radar superheterodyne, the receiver can be conveniently divided into five principal parts; the radio-frequency amplifier stages, the mixer or frequency conversion stage, the i.f. amplifier stages, the (second) detector stage, and the video amplifier stages.

#### Problems of Noise

Like other u.h.f. receivers, the radar receiver is faced with the eternal problem of noise disturbances generated within the circuits of the receiver itself. If it were not for this problem, any number of amplification stages could be used to increase the amplitude of the echo signal, no matter how weak, by any desired amount. These noise disturbances actually

### GLOSSARY OF RADAR TERMS

**Antenna array**—A symmetrical arrangement of dipoles with directional characteristics.

**Antenna reflector**—See reflector.

**Antenna switch**—See T-R switch.

**Azimuth**—Bearing or angular direction relative to true north.

**Beam width**—The width in azimuth of the pulsed r.f. energy beam.

**Bearing**—See Azimuth.

**Blocking oscillator**—Tuned-grid, tuned plate r.f. oscillator in which the grid circuit controls the pulse duration.

**Carrier frequency**—The ultra-high frequency at which a radar transmitter operates.

**Cathode follower**—Distortionless, impedance-matching, isolating stage.

**Charged line**—A pulse-shaping network which reflects a steep-sided rectangular pulse of a duration determined by the electrical constants of the line.

**Clamping circuit**—A circuit which holds either the positive or negative amplitude extreme of a wave form to a given reference level of voltage.

**Crystal mixer**—Mixing two frequencies by using the non-linear characteristics of a crystal.

**Cut-off limiting**—Limiting action of an amplifier when operated beyond the point of plate current cut-off.

**D.C. restorer**—See clamping circuit.

**Delay circuit**—Network or circuit which introduces a time or phase delay of a wave form.

**Differentiator circuit**—A short time constant (RC) circuit and amplifier which produces an output voltage with an amplitude proportional to the rate of change of the input voltage. A circuit used to sharpen a wave form. Sometimes called a peaking circuit.

**Dipole**—A half-wave, center-fed radiating element.

**Duty cycle**—The fraction of a complete radar cycle during which energy is transmitted.

**Echo**—That part of the r.f. pulse reflected back to the radar set by a target.

**Electronic timer**—The component of a radar set that originates the pulse recurrence frequency, and synchronizes the operation of other components with the radiation of r.f. pulses by the transmitter.

**Elevation angle**—The angle of the target with respect to the radar set and the horizontal plane of the earth.

**Envelope**—The general outline of a wave form.

**Gate**—A rectangular wave used to switch a circuit on or off electronically during certain portions of the radar operating cycle.

**Grass**—Static or noise appearing as intermittent, minute interruptions of the oscilloscope time base.

**Ground return**—That part of the r.f. pulse reflected by the ground surrounding the radar set.

(Continued on page 149)

are random, minute voltage variations due to any of several circuit conditions—usually associated with radio-frequency amplifier stages of the receiver.

The effect of these noise voltages depends not so much upon their individual amplitudes, but upon the power relation between the echo signal and the collective noise. If the amplitude of the noise voltages is not less than the amplitude of the echo signal, the echo cannot be recognized at the output of the receiver.

For this reason, the noise voltages must be kept as low as possible; i.e., the signal-to-noise ratio must be kept high. The lower the noise level, the weaker the acceptable echoes—and the greater will be the working distance of the radar set. Thus, internal noise in the early stages of the receiver directly affects the useful range of the equipment.

There are three different kinds of noise disturbances in the r.f. section

of a receiver; noise due to thermal agitation, noise due to shot effect, and hum or induced noises.


Thermal agitation—the random motion of electrons in a conductor—is caused primarily by either high conductor resistance, or high operating temperature.

Shot effect—the irregular emission of electrons by the cathode of the r.f. amplifier tubes—is caused by low filament operating temperatures, resulting in a low space charge within the tube.

Stray electrostatic or electromagnetic fields often induce hum and other extraneous noises into a u.h.f. circuit. This is a form of modulation and generally exists when units of the r.f. stages are not properly shielded.

While it has not been possible to eliminate the noise disturbances caused by these three effects, most of them have been minimized by improved u.h.f. design and the use of special tubes.

Fig. 2. Basic block diagram of radar superheterodyne receiver.

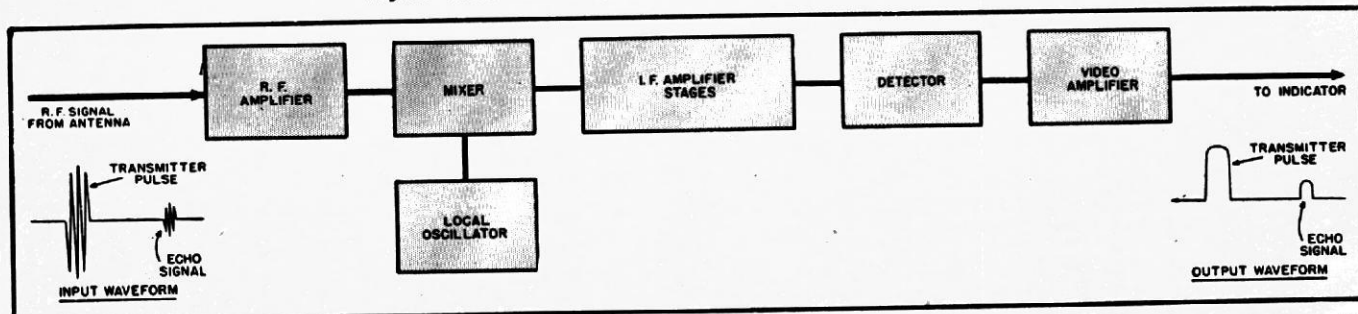



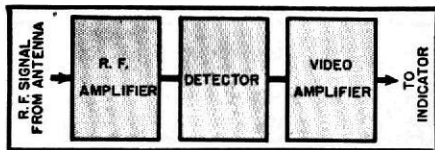


Fig. 3. Basic block diagram of superregenerative receiver.

Atmospheric "noise," or static, is another contributing factor to the sensitivity of the radar superheterodyne. A fairly wide input bandwidth would be required by most receivers, since the video output of the receiver must contain a wide range of frequencies, *i.e.*, be rich in harmonics, for faithful reproduction of the echo pulse. This wide bandwidth admits a greater amount of spurious external "noise" and atmospherics, which usually must be contended with unless some form of *variable* input bandwidth is used in the first r.f. stage of the receiver.

Considerable noise may be minimized or even eliminated by dividing the superheterodyne receiver *physically* so that the r.f. stages and mixer are located near the antenna system, and the i.f. and video stages are located elsewhere, near the main components of the radar equipment.

Parts of the receiver may often be distributed throughout the radar set so that their physical identity becomes lost. However, for purposes of our discussion we will assume the receiver to be a complete component, consisting of the r.f. amplifier, frequency conversion, i.f. amplifier, and video amplifier stages.

### R.F. Amplification

Probably most radar superheterodyne receivers use one or more stages of r.f. amplification, but at extremely high frequencies of operation this may be difficult.

However, we can assume that at least one stage of r.f. amplification is generally used—sometimes two or three stages—providing a considerable degree of pre-selection.

Because of noise disturbances, screen grid tubes are impracticable for r.f. amplification in radar superheterodynes. Inductive reactance of the cathode leads causes degeneration in the circuits associated with such tubes.

Grounded-grid triodes offer advantages as r.f. amplifiers at the lower frequencies of radar operation. If the input signal is applied to the cathode, the plate-to-grid capacitance of the tube then acts only as a plate load, instead of the conventional feedback circuit. This absence of plate-to-grid capacitance is due to the shielding action of the grounded grid.

At higher frequencies the Light-house tube has found considerable use as an efficient r.f. amplifier. But in the extremely high ranges, r.f. amplifier stages are seldom used in superheterodynes.

All of the u.h.f. circuit techniques discussed earlier in this series on "Practical Radar" can be applied to this stage of the receiver. Every piece of connecting wire, no matter how short, acts as some portion of a transmission line. Lumped inductance and capacitance are of far less importance than distributed inductance and capacitance, and coaxial cables or wave guides are used to transfer r.f. energy over any appreciable distance in the set.

Resonant circuits of the r.f. stages are of the fixed tuned type; that is, the stages are adjusted to a given frequency of operation, depending upon the carrier frequency of the radar transmitter. Tuning can be accomplished by variable condensers.

R.f. chokes used in the plate and filament leads of the r.f. amplifier tubes prevent leakage of the signal into the power supply. Because of the high operating frequencies involved, low values of inductance are required. The chokes may be formed from the interconnecting leads which supply voltages to the different tube elements, a few turns being sufficient for this purpose.

Every portion of the r.f. amplifier stage must be well shielded, and the complete stage also shielded from the rest of the superheterodyne.

These, and many other "trick" u.h.f. techniques, could be employed in radar receivers, in an effort to supply as much undistorted r.f. amplification as possible to the echo signal before it is passed to the frequency conversion stage of the radar superheterodyne.

### Frequency Conversion

Mixing or frequency conversion

could be accomplished in a radar receiver by means of a separate local oscillator in a somewhat conventional circuit. However, it should be noted that the output of this mixing stage, the intermediate frequency, needs to be considerably higher than in the usual u.h.f. superheterodynes.

At the lower operating frequencies of the r.f. spectrum, any of several types of high-frequency tubes can be used as the "mixer" with a stable local oscillator supplying the mixing frequency.

Link coupling between the mixer and local oscillator, and between the mixer and the first i.f. amplifier stage, would obtain the optimum degree of energy transfer between these stages. This method of coupling prevents interaction between the circuits due to heavy loading, such as would occur with other types of coupling.

Radio-frequency chokes would be as efficient in the power leads to the mixer stage as in the r.f. amplifier stages previously described.

The local oscillator might use any type of stable oscillatory circuit, and the tuning can be adjusted over a slight range of frequencies. The local-oscillator frequency may be slightly higher or lower than the r.f. signal, by an amount which represents the "difference" or intermediate frequency.


Frequency conversion at the higher operating frequencies of the u.h.f. spectrum becomes much more difficult and requires something of a new philosophy of "mixing."

One type of local oscillator capable of generating a high frequency for mixing purposes is known as the Klystron tube [Sperry] functioning in a very simple circuit. Also known as a reflex Klystron, this tube can generate radio waves of very short length.

The Klystron tube consists essentially of a cathode, a control grid, a repeller electrode, and a resonant cavity. The tube operates on the velocity-modulation principle, in which the transit time of electrons between the resonator and the repeller is utilized. Oscillations take place within the resonant cavity when properly phased electrons pass between the resonator grids. This phasing can be affected by the accelerating voltage

(Continued on page 151)

Fig. 4. Detailed block diagram of radar superheterodyne receiver.

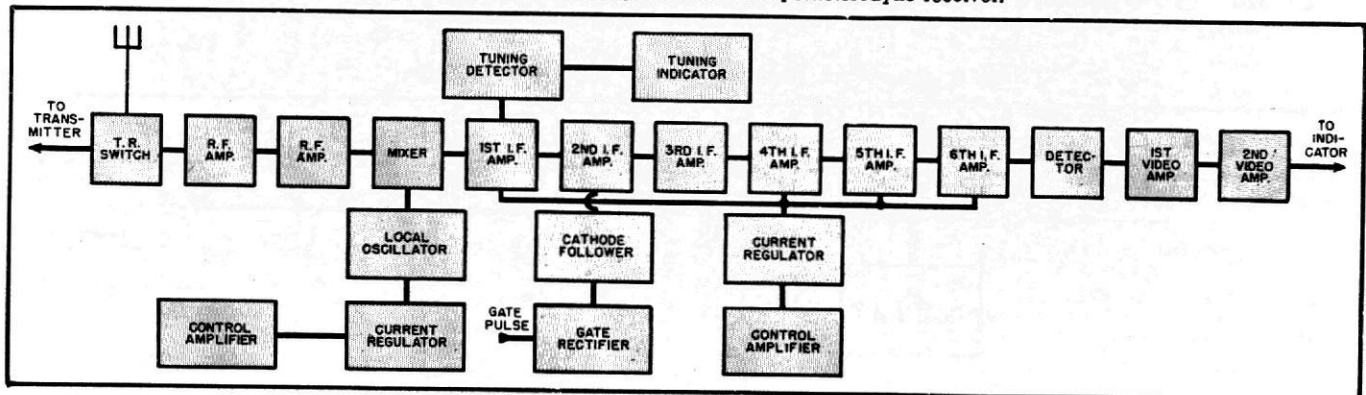

**Practical Radar**  
(Continued from page 46)

of the electrons, the voltage of the reflector, or the resonant frequency of the cavity. Thus, any one of these interrelated variables can be used to tune and adjust the Klystron for operation at any desired local-oscillator frequency.

**I.F. Amplification**

The large amount of gain required in a radar receiver is obtained by considerable amplification of the intermediate frequency, thus requiring a large number of i.f. amplifier stages.

The intermediate frequency may be quite high, while some radar receivers function with a considerably lower i.f. signal. An important factor governing the choice of intermediate frequency is the bandwidth of the circuits.

The width of the frequency channel passed by the i.f. amplifier is determined by the spectrum range of the returning echo signal. Since reception of the signal is of the double-sideband variety, this region allows for sufficient uniform amplification of all video frequencies.

The frequency bandwidth must be fairly wide to pass all of the component frequencies contained in the received r.f. signal. To fix the bandwidth within acceptable limits, "damping" resistors could be used in the i.f. circuits.

The sensitivity as well as the selectivity of the entire set will suffer if the bandwidth of the i.f. amplifier is too wide. Losses in the i.f. amplifier stages can be made almost negligible by using very close coupling between the primary and secondary windings of i.f. transformers.

In order to vary this coupling, the physical location of the primary winding can be changed with respect to the secondary winding. This coupling adjustment is particularly critical in the first stage of i.f. amplification.

The first i.f. stage should be operated with the lowest possible noise level, in an effort to obtain as high a signal-to-noise ratio as possible.

Following stages of i.f. amplification may be primarily straight i.f. amplifiers, operating under similar but not so exacting conditions as the first stages. All i.f. stages are double-tuned.

Since gain values as high as 100 db. can be expected from the combined stages of i.f. amplification, tendencies toward regeneration must be carefully controlled by filters and proper shielding.

Lead shielding and filters can also prevent the receiver from being over-sensitive to strong external r.f. and a.f. fields.

Although the radar receiver is protected by the T-R switch (Fig. 1) from transmitter power surges, a small signal is permitted to "leak through" the receiver in order to register as a

# SOUND VALUES at TERMINAL RADIO


**DE LUXE  
20 WATT AMPLIFIERS  
No. 6419**

- 2—HIZ MIKE INPUTS
- 2—PHONO INPUTS with Fader Controls
- 1—Master Gain Control
- DUAL TONE CONTROL for Bass and Treble
- Illuminated Panel
- 4-8 or 500 OHM OUTPUT
- 2—65Q7
- 1—6SJ7
- 1—6SC7
- 2—666G
- 1—523

NET PRICE WITH TUBES  
**\$43<sup>59</sup>**  
F.O.B. N.Y.



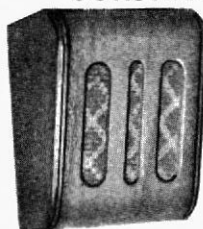**WALNUT FINISH WALL BAFFLES REINFORCED CONSTRUCTION**




- SPECIAL PRICES:**
- For 5" Speaker.. \$1.74
  - For 6" Speaker.. 2.45
  - For 8" Speaker.. 3.01
  - For 10" Speaker.. 3.48
  - For 12" Speaker.. 4.53

NO PRIORITY REQUIRED

**UTAH PUBLIC ADDRESS SPEAKERS**


Model	Watts	Diam.	Price
8P	7	8"	\$3.38
10P	9	10"	5.43
12P	10	12"	6.61
E12P	13	12"	9.40
G12P	17	12"	14.25
GS12P	20	12"	20.43
H12P	22	12"	25.28

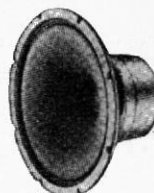

NO PRIORITY REQUIRED  
OTHER SIZES AND MODELS IN STOCK

**STEEL UTILITY CABINET**

Size 19x12x10" for 8 3/4x19" Panel

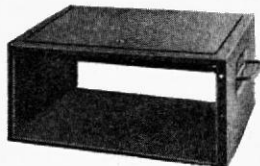

- Top door with Snap lock
- Heavy duty construction
- Black crackle finish
- Special Price while they last only \$3.98
- Steel Panel ..... .88
- Steel Chassis 11x17x2..... 1.35

NO PRIORITY REQUIRED.

**HEAVY DUTY POWER CONTROLS  
STANDARD BRANDS—NEW STOCK**

- 50 WATT
- 16 Ohms
- 32 Ohms
- 50 Ohms
- 150 Ohms
- 250 Ohms
- 300 Ohms



ANY SIZE  
**\$1.82**

- 25 WATT
- 6 Ohms
- 100 Ohms
- 250 Ohms

ANY SIZE  
**\$1.63**

- 5000 Ohms 1.92

NO PRIORITY REQUIRED

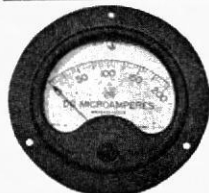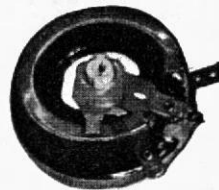

**DE JUR MICROAMP METERS  
BRAND NEW STOCK**

- 0-200 Micro-Amp
- 3 Inch Diameter
- No Priority Required

PRICE ONLY  
**\$7.95**  
R.N. 10

## Terminal Radio Corporation

65 CORTLANDT STREET, NEW YORK 7, N. Y. Telephone WOrth 2-4115




**WAR SURPLUS BARGAINS**

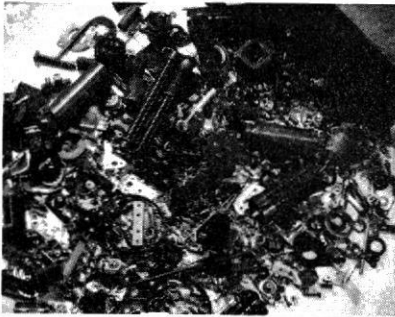**WAR SURPLUS BARGAINS**

**BIG SAVINGS**  
Hundreds of specials  
for **RADIO SERVICEMEN**

- CATHODE RAY TUBES
- POWER & TRANSMITTING TUBES
- HEADPHONES, etc.
- HARD-TO-FIND TEST METERS



**7 LB. RADIO PARTS ASSORTMENT**

A "gold mine" for the radio serviceman. Hundreds of valuable radio parts, including rivets, soldering lugs, sockets, coils, resistors, condensers, switches, transformers, etc. An amazing value. Money-back guarantee.

**K130R — FULL 7 POUNDS ONLY \$179**

War Surplus Bargain Book  
Page after page of war surplus  
and other bargains for the radio  
serviceman; also specials for  
home, shop and outdoors.  
**IT'S FREE! WRITE TO-DAY**

**FREE CATALOG**

**STARK'S** Dept. RR-10 509 So. STATE STREET  
CHICAGO 5, ILLINOIS

For the Finest  
in  
Sound Equipment  
Watch ...

**NEWCOMB**

... the sound of quality

Announcements of special interest to discriminating buyers of sound equipment may be expected in the near future. Send us your address to receive these mailings as they become available.

*Newcomb*  
**AUDIO PRODUCTS CO.**  
Manufacturers Since 1938  
2815 So. Mill Street, Dept. F  
Los Angeles 7, California

strong pulse—or "transmitter" pulse—at the beginning of the time base of the indicator oscilloscope. This r.f. signal directly from the radar transmitter may have a blocking effect each time the pulse passes through the receiver. To counteract this possibility, a gate pulse could be applied to the second i.f. amplifier stage.

The gate pulse consists of a rectangular voltage wave controlled by the electronic timer. The wave would be applied to one or more of the i.f. stages and could either bias the tube(s) to cut-off, or completely remove the plate voltage during the time the transmitter is pulsing. This, in effect, is a protective device to prevent the i.f. stages from overloading due to the extremely powerful input pulses from the transmitter.

After the desired degree of amplification has been obtained by the i.f. stages of the radar receiver, the signal is detected—probably by means of a conventional diode—and the rectified output is then applied to the video stages of amplification.

**Video Amplification**

An energizing voltage of from 50 to 200 volts peak with a bandwidth of about three megacycles is required by most cathode-ray tube circuits. It is the purpose of the video stages of amplification to supply this wide range of frequencies at the desired voltage amplitudes.

Video-frequency amplifiers are usually resistance-coupled with a characteristically almost-flat gain response over the entire range of frequency operation, about three megacycles.

Video-frequency amplifiers have been developed which supply from 30 db. to 50 db. of gain per stage with bandwidths as great as two megacycles. Use of the same circuits for bandwidths of about three megacycles, lowers the amount of stage gain to about 25-35 db.

Some means of limiting the amplitude of the video output may be provided, to prevent defocusing of the cathode-ray tube due to strong signals. The output signal from the video amplifier is usually a negative-going pulse, applied to the grid of the cathode-ray tube. A positive-going pulse would be applied to the cathode of the indicator tube.

The type of cathode ray oscilloscope used by the radar set would not normally influence the nature of the output from the video amplifier stage or stages.

**Superregenerative Receiver**

Another type of receiver offering radar possibilities is the superregenerative receiver (Fig. 3).

A superregenerative oscillator forms the basis of this type of receiver. Superregeneration takes place when oscillations are started and stopped at an r.f. rate which is low in comparison with the frequency of the generated voltage. This is accomplished by means of a quench oscillator.

**12 WEEKS SHOP TRAINING** TRAIN FOR YOUR PLACE IN **ELECTRICITY**  
*All Finance Your Training*

At Coyne you "Learn by Doing" on real machinery and equipment. Trained Electrical men needed now. Electricity offers you opportunities for the best jobs today, and a real peace-time future. Don't let the opportunities of peace-time catch you unprepared. Get your electrical training now.

**EARN WHILE LEARNING, JOB HELP AFTER GRADUATION**

The place to get your electrical training is at Coyne. We have been training men and young men for 46 years — by the famous "Learn by Doing" method in the great Chicago shops of Coyne. Many do part time work to help out with expenses. Free lifetime employment service when you graduate. Right now I'm including extra training in Industrial Electronics and Electric Refrigeration at no extra cost. Send coupon now for Free Book and details. No obligation; no salesman will call. I send facts — then you decide. Mail coupon today. We also have facilities for men with physical disabilities whether due to war or other causes.

H. C. LEWIS, President  
COYNE ELECTRICAL SCHOOL  
500 S. Paulina St., Dept. 75-81, Chicago, 12, Ill.  
Send me your Free Electrical Book and details.  
 Send G. I. Bulletin  Physical disability.

Name .....

Address .....

City ..... State .....

**EXTRA 4 WEEKS COURSE IN INDUSTRIAL ELECTRONICS INCLUDED!**



VETERANS Coyne is equipped to train those who qualify under the G.I. Bill of Rights. Check coupon

**IF YOUR SPEED IS LESS THAN 50 W.P.M.**

**SEND TODAY FOR THIS 52 PAGE FREE BOOK**

**— FOR AMATEURS AND COMMERCIAL RADIO OPERATORS**

**CANDLER SYSTEM BOOK & FACTS**

It shows that "crack" operators rely on something besides practice to develop their high speed and proficiency; it explains the "knack" of sound-sense and sound-consciousness — the secret of speedy sending and receiving. Once you acquire these mental processes, reading code becomes almost second nature to you, just as the rhythm of a dance band becomes automatic to musician and dancer.

Champions endorse the Candler System. It is used in training Commercial Operators, Amateurs, and Radiotelegraph Specialists in Signal Corps, Airlines, Broadcast Studios, Police Inter-City Communications. Wherever the fastest, most efficient operators are found, there you will find Candler trained men.

If you want s-p-e-e-d, if you have any difficulties in operating technique, if 40-50, and more, wpm seem fantastic speeds to you—send for this revealing 52 page Book now. It's yours without cost or obligation. Simply send your name and address to—

**CANDLER SYSTEM COMPANY**  
Dept. 2-L, Box 928, DENVER, COLO., U.S.A.  
And at 121 Kingsway, London, W. C. 2, England

**BUILD YOUR OWN!**

**\*FAST-FREEZER** PLANS \$1.00

Every amateur will be proud to build this household necessity which requires no expert knowledge. Operates on 32 or 110 volts. There's fun in building and profit in using this handy freezer. Saves up to 75%.

**PLANS ARE SIMPLE**  
These 8 to 40 cubic foot sizes can be built of new or used parts. Mail \$1 bill or check for complete plans and catalog.  
**LEJAY MFG., 454 LeJay Bldg., Minneapolis 8, Minn.**



The incoming r.f. signal from the antenna is applied to the grid of the superregenerative stage. Since the tube is operated in a highly regenerative state, there will be very high amplification of the signal *during periods of oscillation.*

Because of the limiting action of the circuit, the video output doesn't depend on the strength of the input r.f. signal.

Although the sensitivity of a superregenerative receiver is very high, its lack of stability, and other disadvantages, prevents wide use in radar applications.

*(To be continued)*