

# IC provides versatile toggle functions

Louis Vlemincq,  
Belgacom, Evere, Belgium

The circuit in **Figure 1** offers not only as many as six channels in a single IC package, but also a high level of additional flexibility. The configuration of Output 1 is a "plain-vanilla" toggle. A resistive divider comprising  $R_1$  and  $R_2$  provides a midsupply bias to all the channels through resistors  $R_3$ ,  $R_6$ ,  $R_7$ ,  $R_{10}$ , and  $R_{12}$ . Because the bias voltage of  $R_1/R_2$  is within the hysteresis range of the gates, they behave as flip-flops, retaining their high or low state in a stable manner.

Debouncing capacitors  $C_2$ ,  $C_3$ ,  $C_4$ , and  $C_5$  charge to the level of the output. Pushing switch  $S_1$  inverts the output state because of the inverting action of the gate. This state remains stable because, in the first gate's circuit, for example,  $R_4$ 's value is larger than that of  $R_3$ , and  $R_4$  cannot overcome the hysteresis threshold of the gate. Only the discharge of  $C_2$  can accomplish that task. When you release the pushbutton,  $C_2$  fully charges after the debouncing delay, and the circuit is ready for another inversion.  $C_1$  provides a general power-on-reset feature to all the channels. If your circuit requires only one channel, you can directly connect  $R_1$  and  $R_2$  to the input of the gate, omitting  $R_3$ .

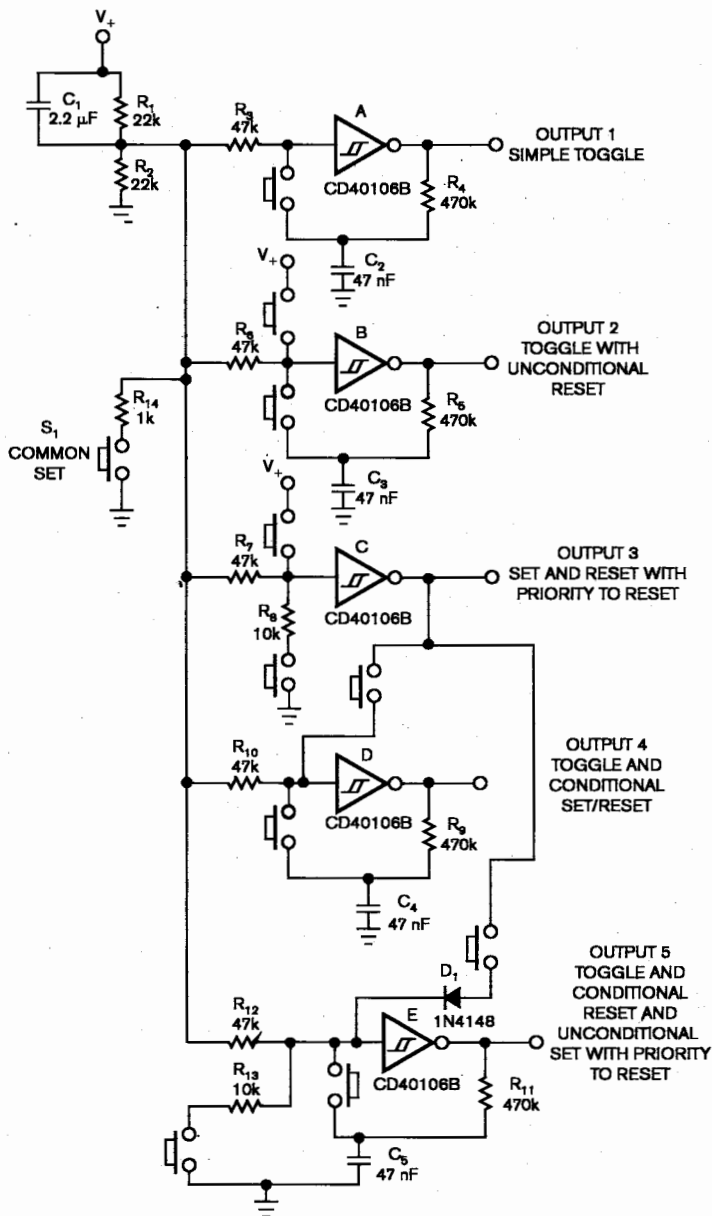


Figure 1 This circuit shows multiple Schmitt-trigger inverters functioning as a variety of set/reset toggles.

# designideas

Output 2 has the same toggle function as Output 1 but also includes a direct reset. Output 3 works only in a set/reset mode; the position of  $R_8$  determines the priority state. Output 4 also has a toggle action, but you can set or reset it to a state opposite that of Output 3. Output 5 works in a similar manner, except it allows only a condition-

al reset because of the position of  $D_1$ . Output 5 also includes a forced, non-priority set. You can mix and match all these functions, providing almost unlimited versatility.

The IC in **Figure 1** is a Fairchild Semiconductor ([www.fairchildsemi.com](http://www.fairchildsemi.com)) CD4000-series circuit, suitable for supplies of 3 to 15V, but it could also

be a 74AC14 or 74HC14 from NXP ([www.nxp.com](http://www.nxp.com)), for example. Any CMOS-input gate having a Schmitt-trigger action is suitable. You must take care to bias the inputs in the middle of their hysteresis range. HCMOS circuits would require an average bias of approximately 1.2V for a 5V supply, for example. **EDN**